


# Front-End Electronics Systems for Particle Detection and Imaging

## Circuits and Applications

- ◆ Detectors and Imagers
- ◆ It's all about charge
- ◆ Electronics
- ◆ 3 examples
  - ◆ CCDs
  - ◆ Active pixels
  - ◆ Hybrid pixels

Peter Denes  
Lawrence Berkeley National Laboratory  
Engineering Division  
Integrated Circuit Design Group Leader  
Engineering Division Deputy  
Advanced Light Source Deputy for Engineering
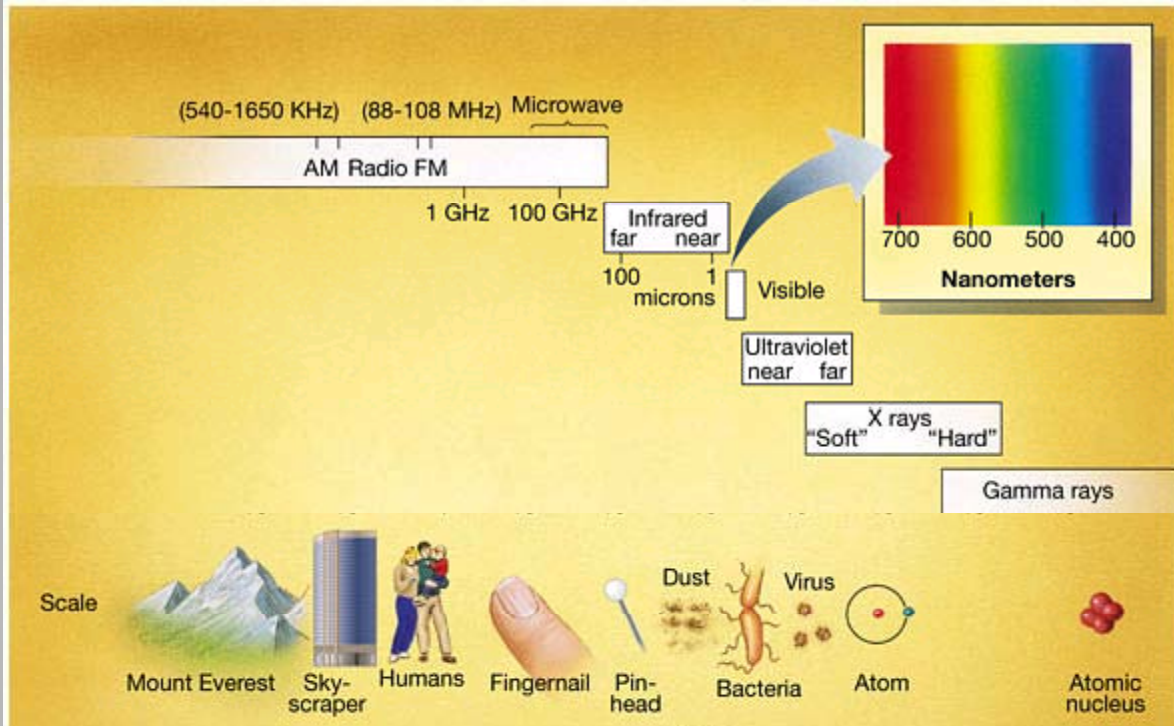
# Scientific particle detection and imaging – wide spectrum




Many objects imaged with visible light

x-rays (synchrotrons, medical)

electrons (EM)

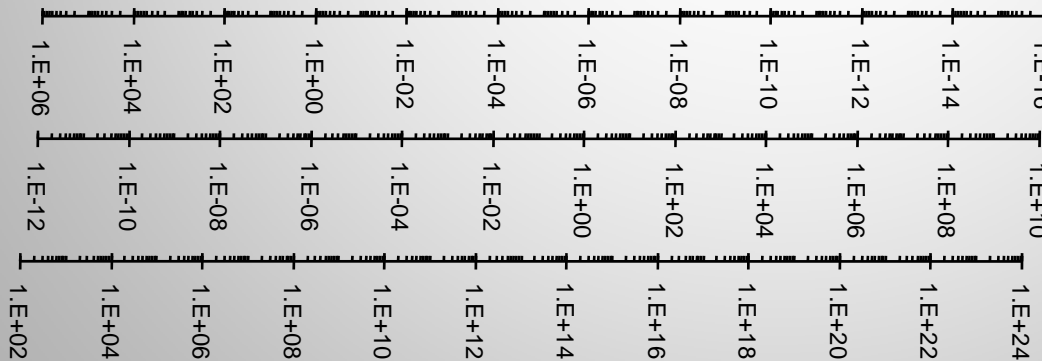and other charged particles (particle physics, ...)




$\lambda$  [m]

$E$  [eV]



$f$  [Hz]


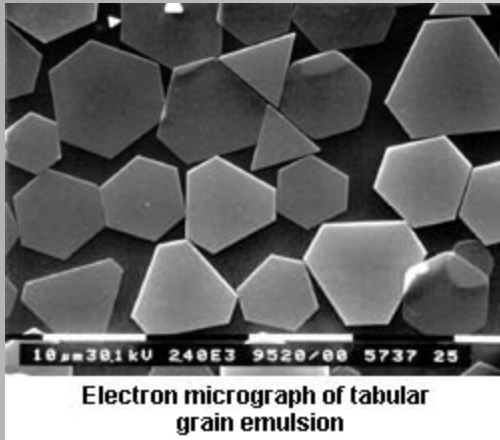
# Focus on solid state detectors, but pay homage to film



AgX + gelatin  
(emulsion)

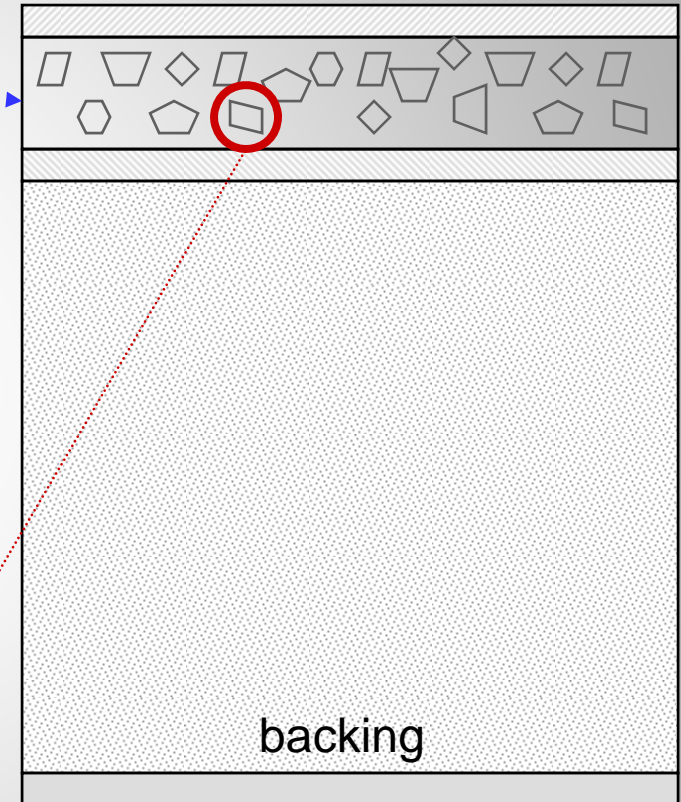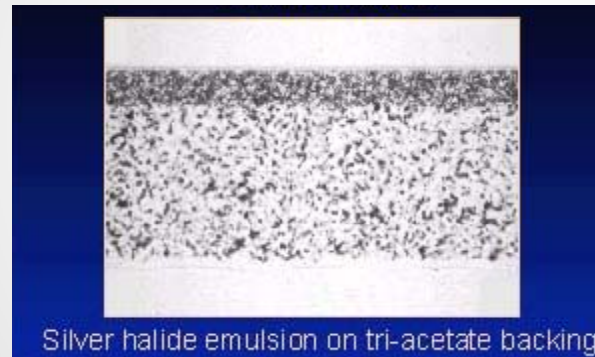


sub-micron to few micron grains  
CMOS / CCD  $\sim 7 - 10 \mu\text{m}$


# "Detection" and "Imaging"



"Particle" is  
of interest

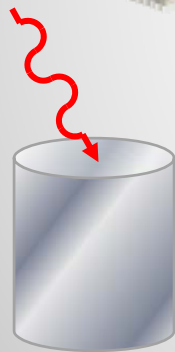

"Particle" is  
illumination

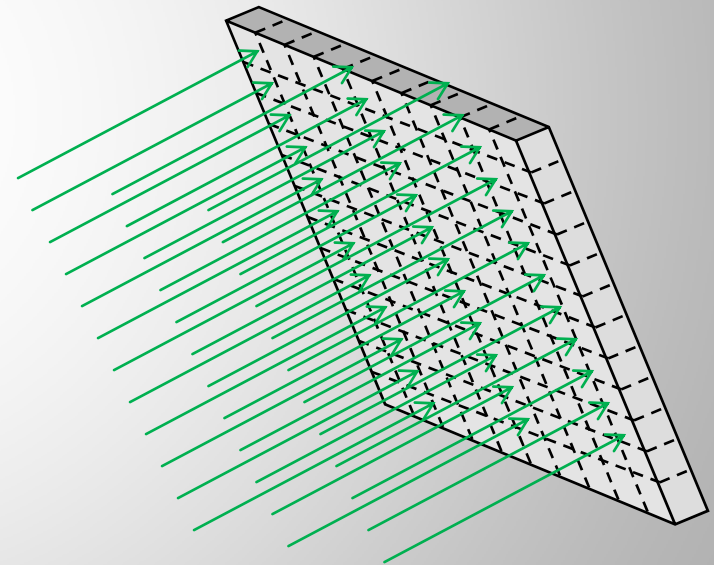

Number of particles  
per detection element  
per sampling interval

$\ll 1$

Number of particles  
per detection element  
per sampling interval

$> 1$

# What you want – what you get

Generally, we want to measure one or more of the following


1. Energy of particle, or its  $dE/dx$
2. Momentum of particle ( $\Rightarrow$  position if in a magnetic field)
3. Time of particle's passage ( $\Rightarrow$  position by TOF, or...)
4. Number of particles, or number of particles per unit area

What we end up measuring is


1. Charge [assume  $q \propto E$ ]
2. Charge [ $q(x,y)$  determines position]
3. Charge  $\rightarrow V \rightarrow V(t) > V_T$  at time  $t$
4. Charge [assume  $q(x,y) \propto N(x,y)$ ]
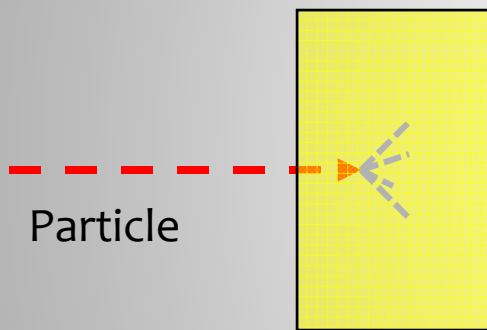
# Detector / sensor


Particle interaction in sensing/detecting medium creates charge/light/heat ...



“Sensor”  
“Detector”




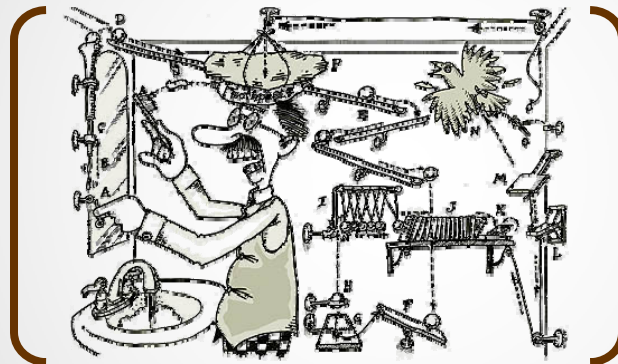


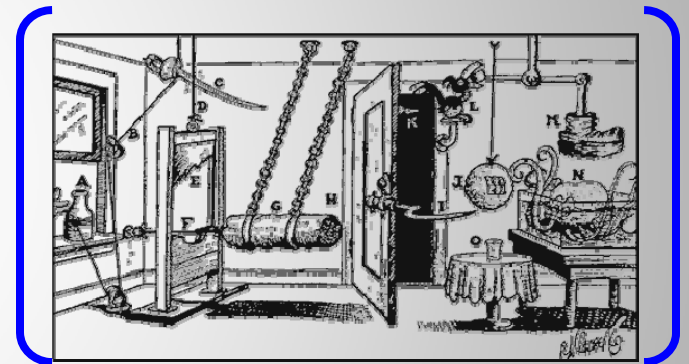“Transducer”  
(optional)  
Convert light/heat ... → charge




Charge → meaningful quantity  
**Front-end electronics**

# Different Languages

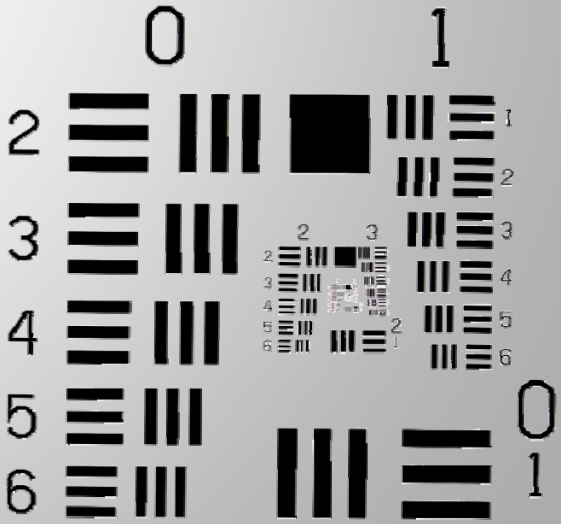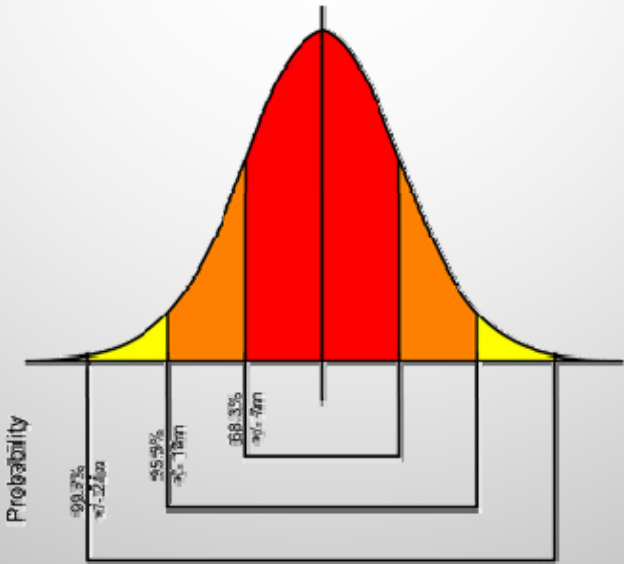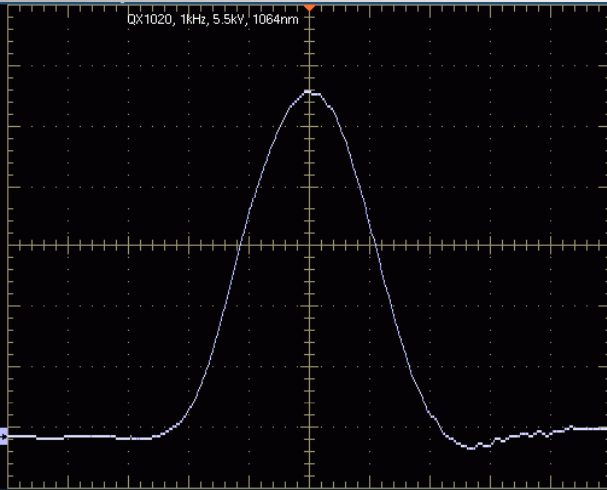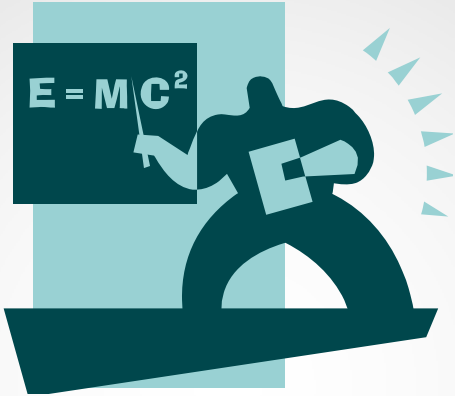

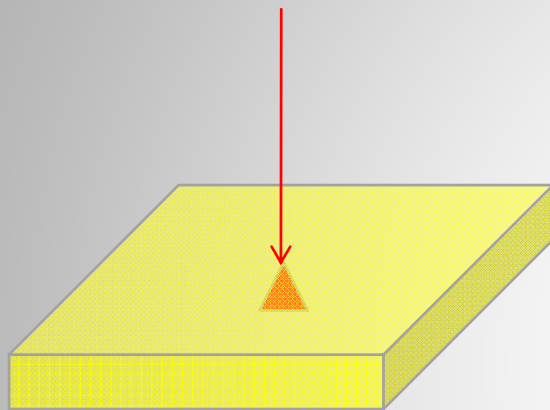
# Electronics contribution to imager "performance"

Picture "quality" defined by Detective Quantum Efficiency



$$I(x) \sim \sin \omega x$$

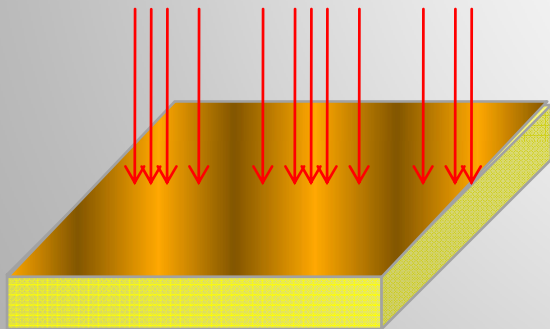

## ◆ Point Spread Function


- Image is convolution of PSF and input

## ◆ Modulation Transfer Function


- (magnitude of the) Fourier transform of PSF



# MTF

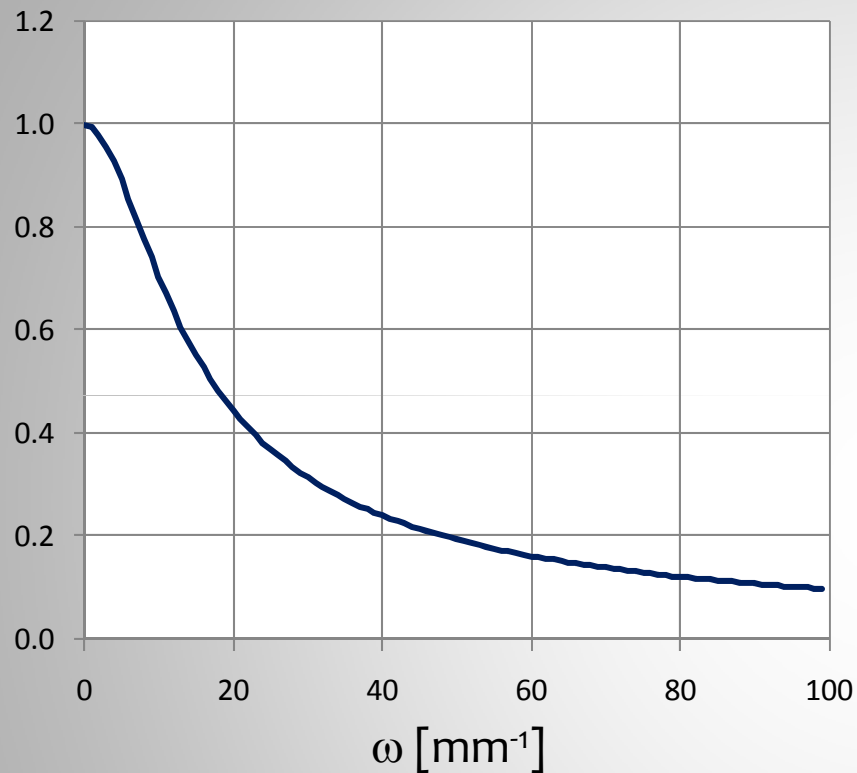

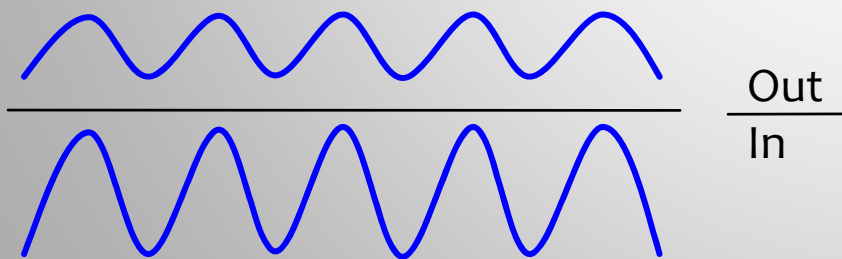- ◆ Spatial analog to (temporal) frequency response in electronics
  - “Signal processing” also possible
  - e.g. early days of Hubble Space Telescope



# DQE

- ◆ Combine notion of Quantum Efficiency (probability of detecting a particle) with spatial response (probability of detecting/quantifying  $N(x,y)$  particles)  $\rightarrow$  DQE
  - How faithfully does the detector transfer the (spatially varying) fluctuations of the input signal


- ◆ Many definitions – most common is  $DQE = \frac{(S/N)_{OUT}^2}{(S/N)_{IN}^2}$

- ◆ Example, flat field illumination (flux  $\phi$ ) of detector with certain QE

- $(S/N)_{IN} = \frac{\phi A \tau}{\sqrt{\phi A \tau}}$  (Poisson)
- $(S/N)_{OUT} = \frac{QE \times \phi A \tau}{\sqrt{QE \times \phi A \tau + \sigma_N^2}}$


for electronic noise  $\sigma_N$

# On to detectors!

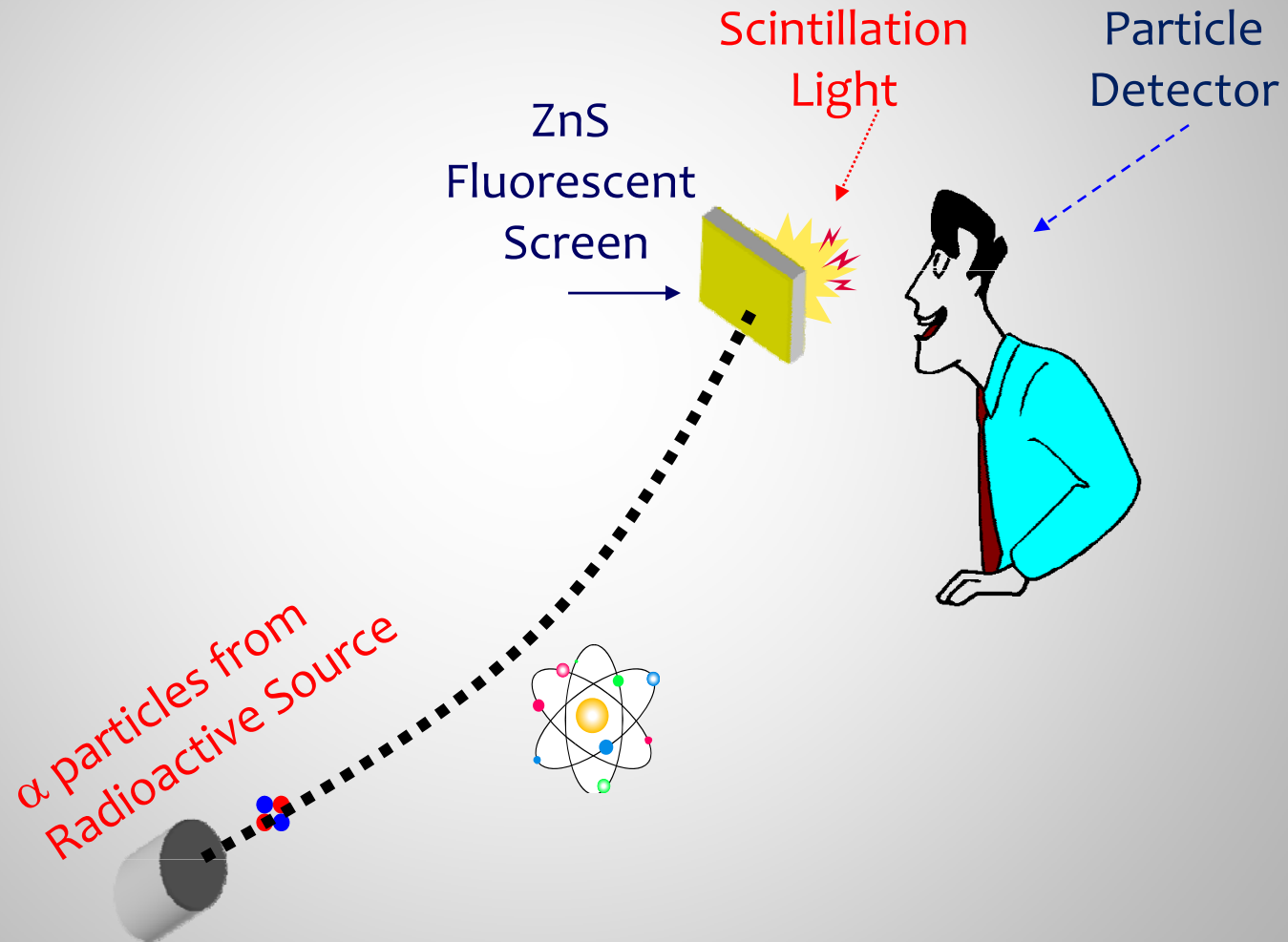

# Coincidence Experiment Cockcroft+Walton, 1932

Graduate Student ①

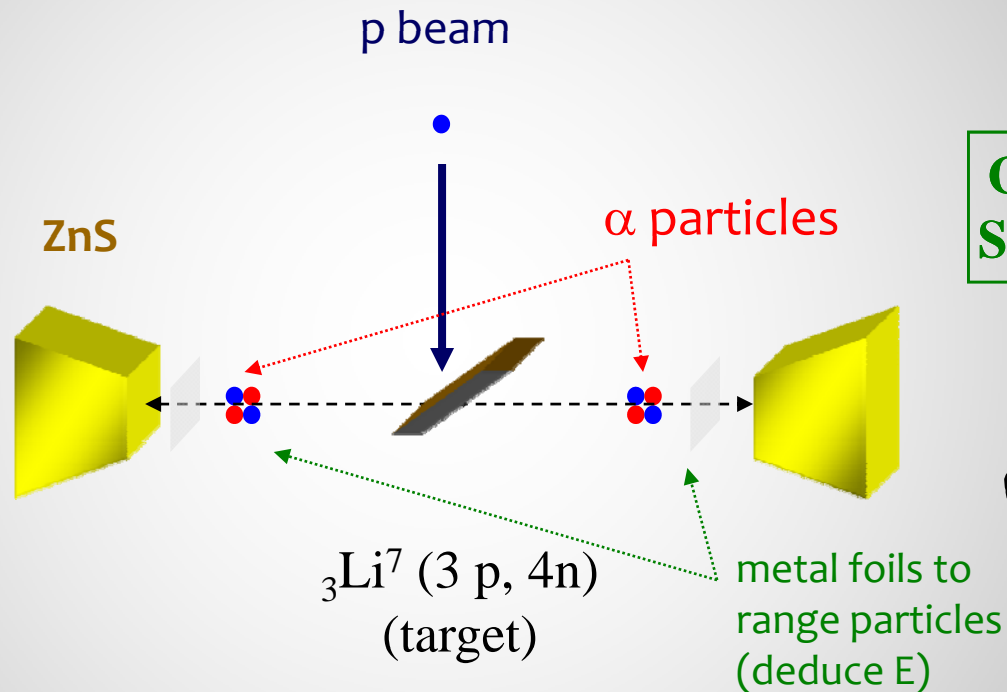

Graduate Student ②




First demonstration that  $E$  (from  $p + {}^3\text{Li}^7 \rightarrow \alpha + \alpha$ ) =  $\Delta mc^2$   
( $\Delta m$  is difference between initial and final nuclei masses)

# Coincidence Experiment
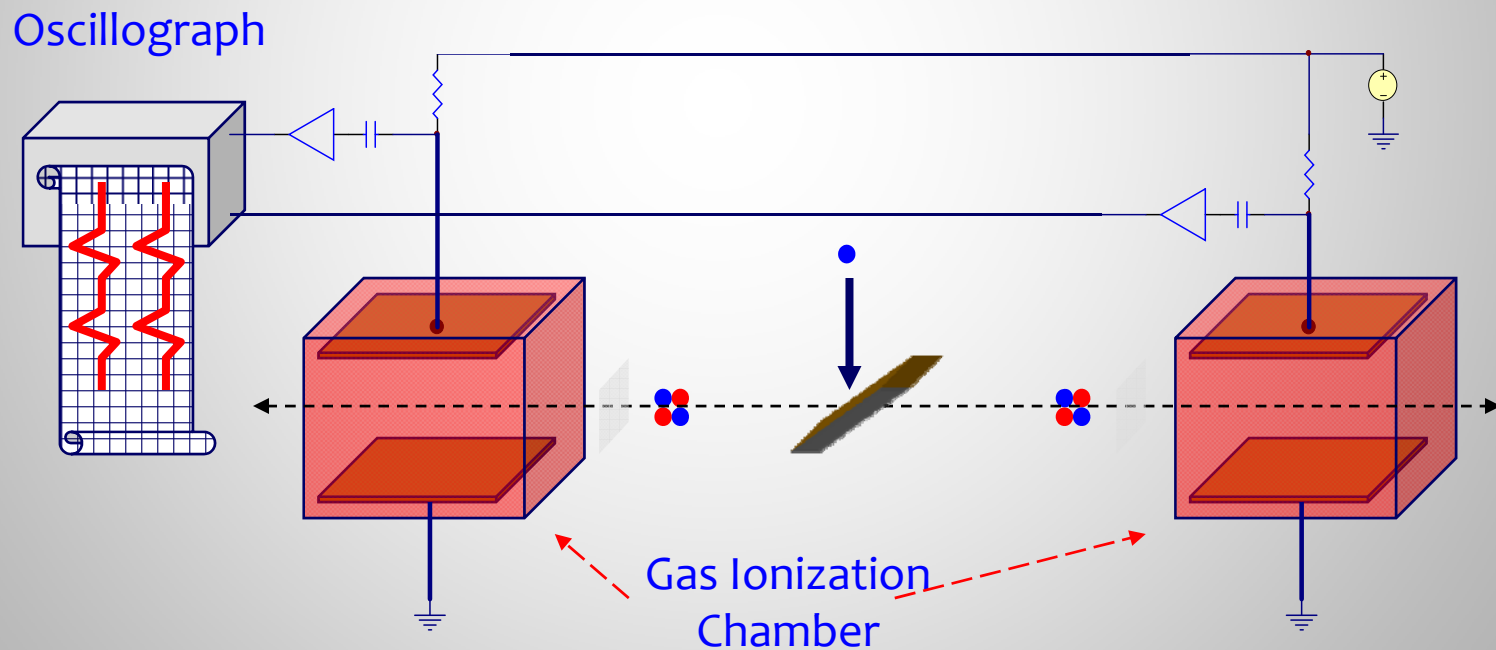
## Cockcroft+Walton - Electronic Verification


One of the last visual counting experiments  
(and one of the first electronic counting experiments)




# Electronic coincidence circuit

Bruno Rossi - 1930

Geiger tubes

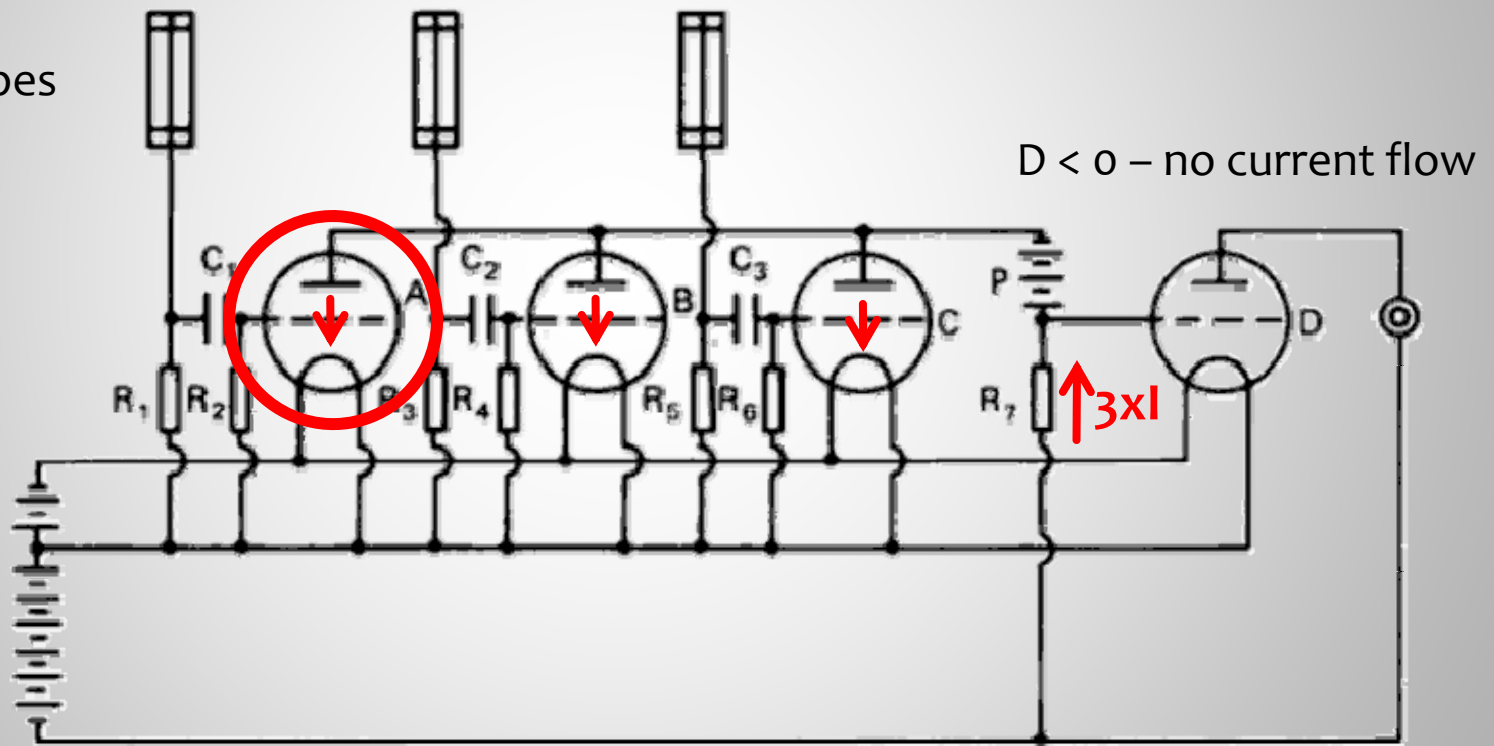

# 1906 – Lee de Forest, the Triode

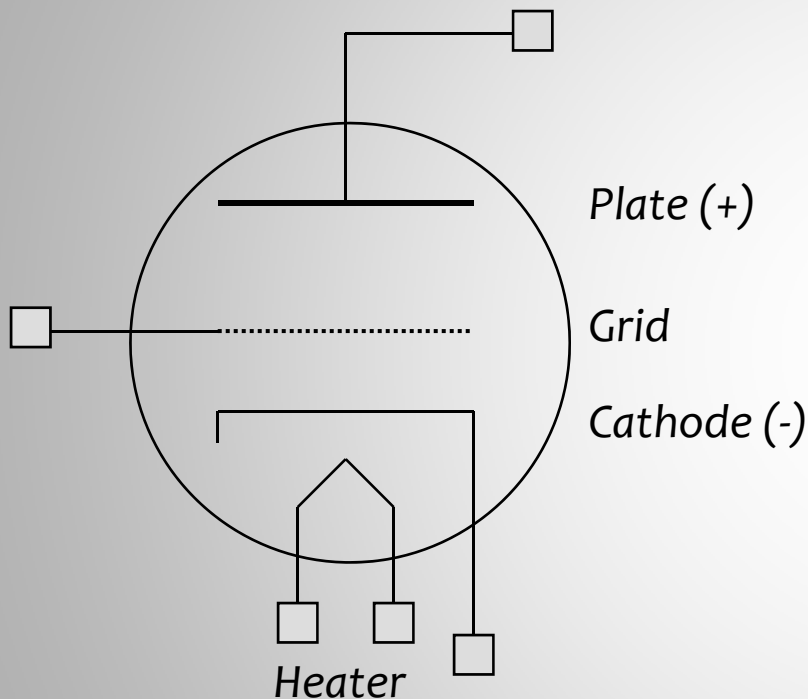

$$I \sim V_G^x$$


- ◆ Indirectly heated cathode emits electrons
- ◆ Electrons collected by positive anode (plate)
- ◆ If grid is negative, electrons are repelled (reduces or eliminates current flow)



# Electronic coincidence circuit

Bruno Rossi - 1930


Geiger tubes

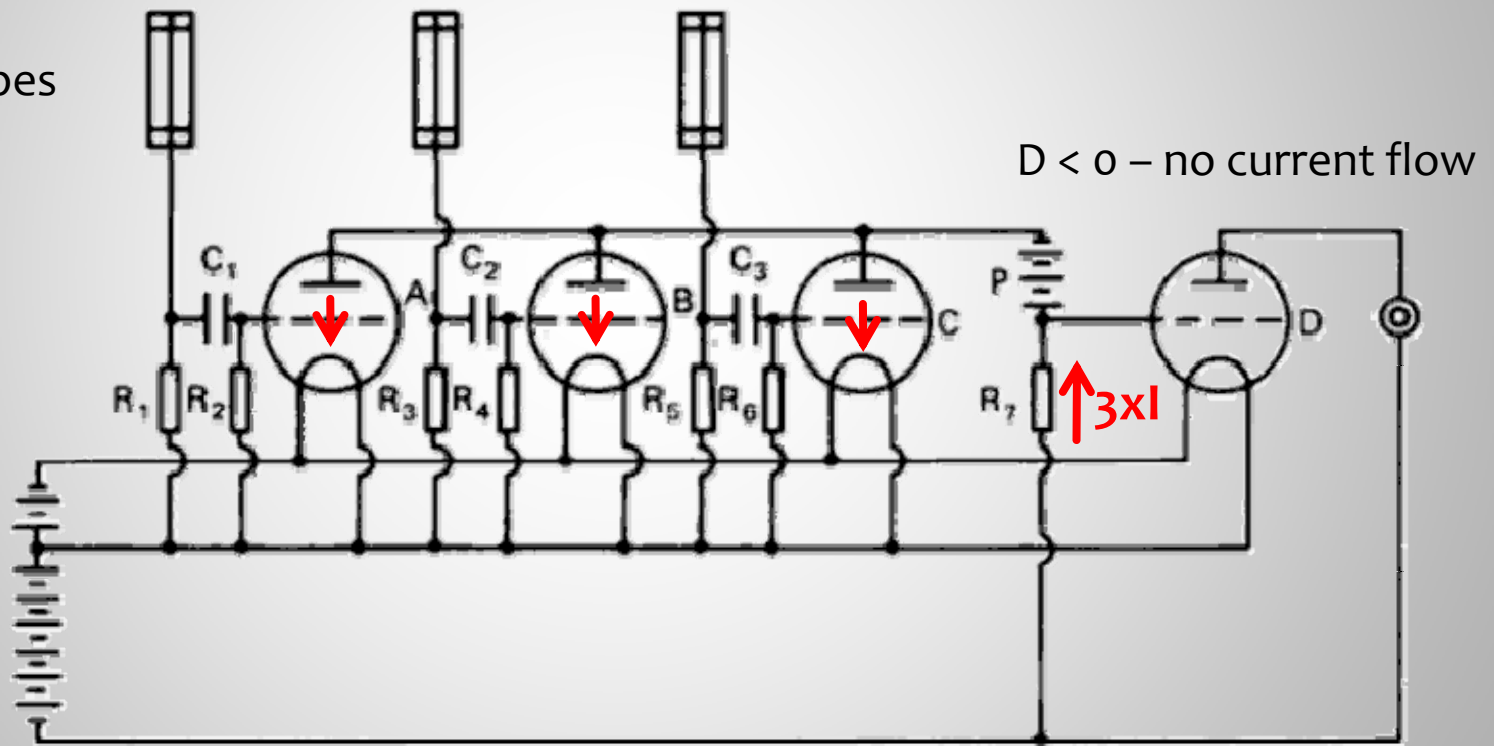




# Electronic coincidence circuit

Bruno Rossi - 1930

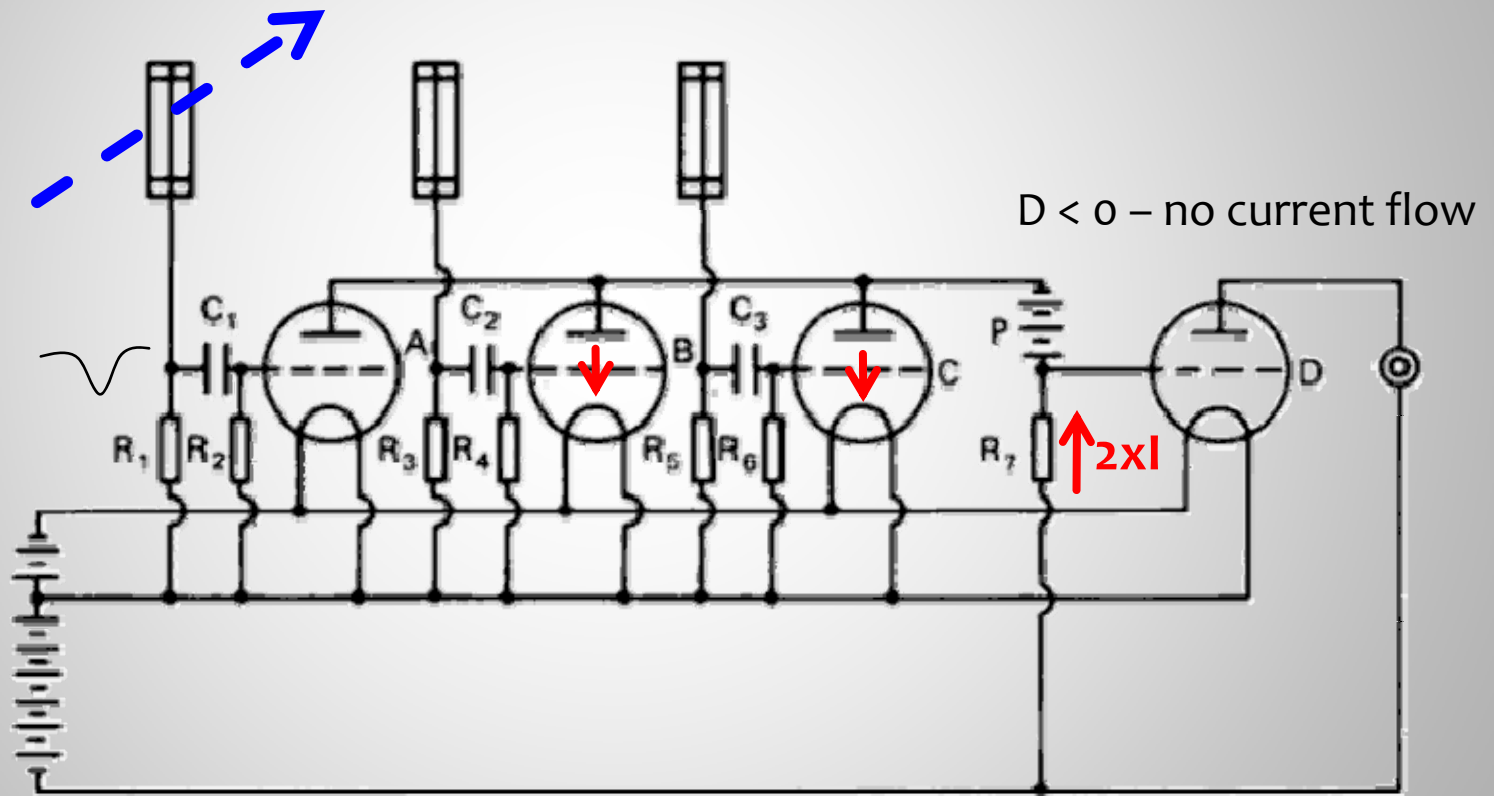


# Electronic coincidence circuit

Bruno Rossi - 1930

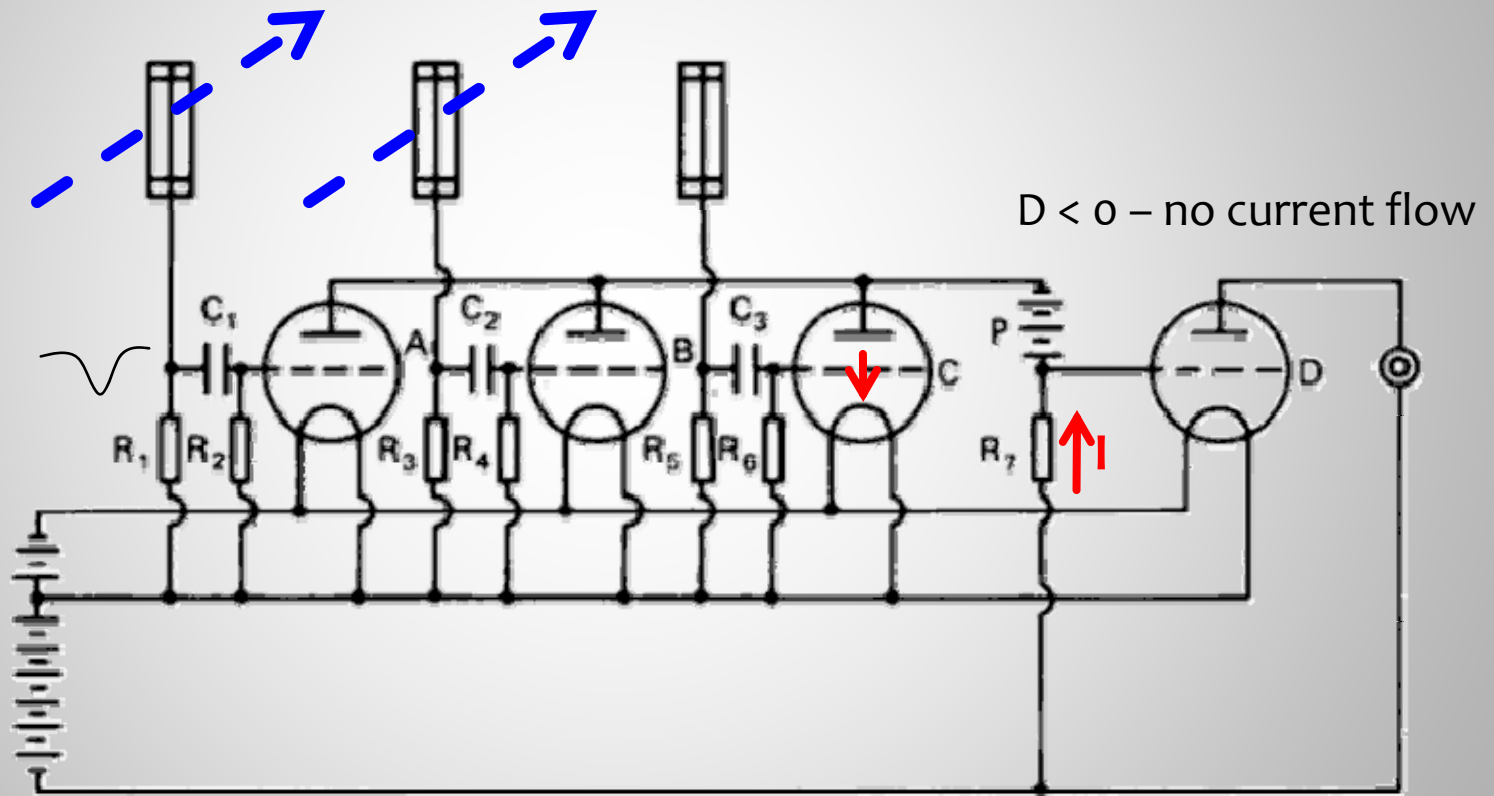


# Electronic coincidence circuit

Bruno Rossi - 1930

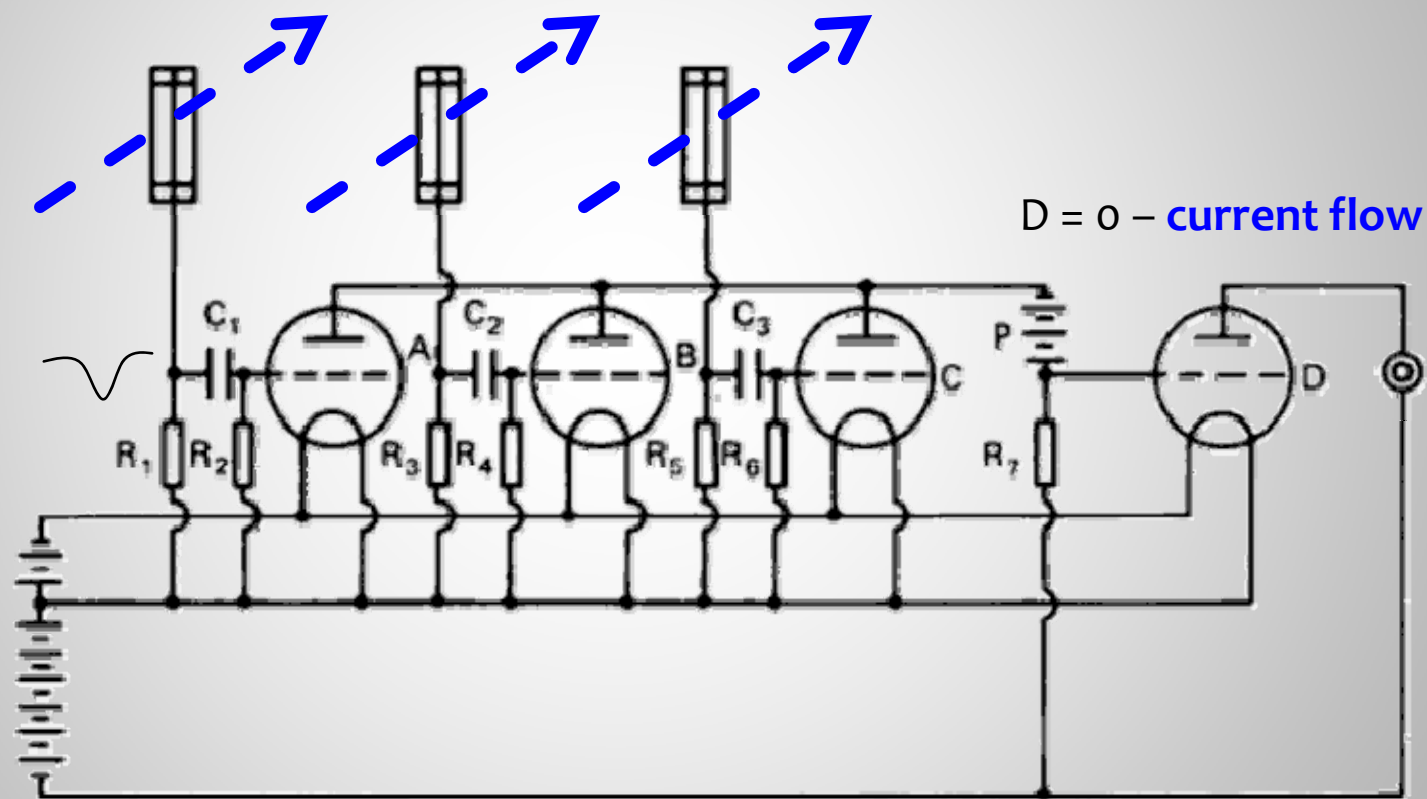

# Generic transconductor

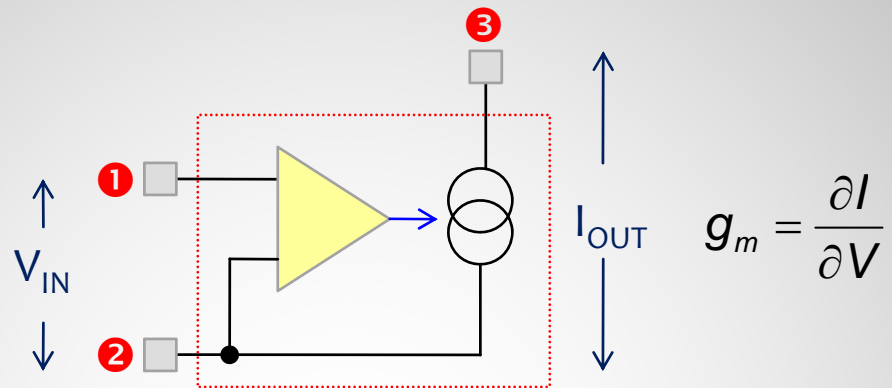


- ◆ Three terminal device
- ◆  $I_{\mathbf{3}\mathbf{2}} = f(V_{\mathbf{1}\mathbf{2}})$
- ◆ To first order,  $I_{\text{OUT}}$  independent of  $V_{\text{OUT}}$  (but not really)


# Real transconductors

- ◆ Bipolar transistor –  $\beta = I_{OUT}/I_{IN}$
- ◆ Field effect transistor –  $R_{IN} \sim \infty$


$$I \propto \exp(V_{BE})$$

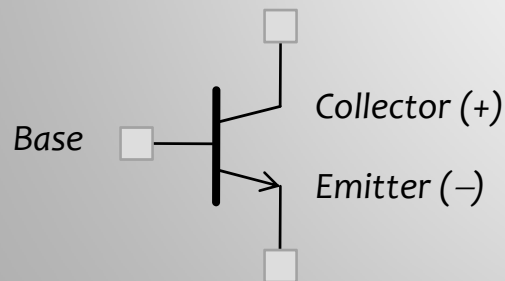


$$I \propto V_{GS}^2$$

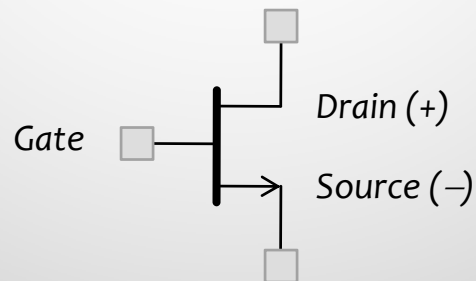

$$I \propto V_{GC}^x$$

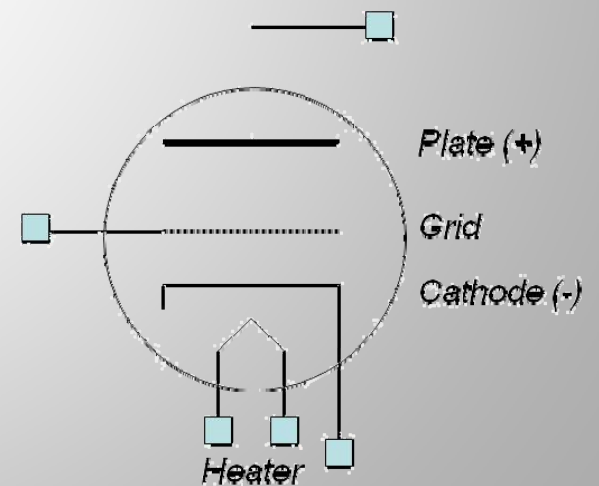

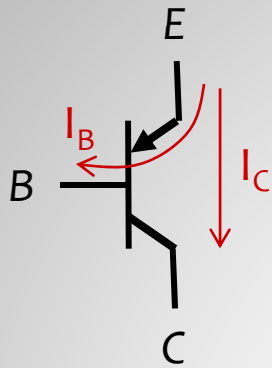
# Bipolar Junction vs. Insulated Gate Transistors





$$I_C \sim \beta I_B$$

$$I_B \sim \exp(V_{BE}/kT)$$

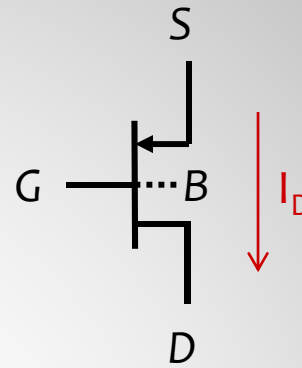



$$I_D \sim (V_{GS} - V_T)^2 \quad V_{GS} > V_T$$

$$I_D \sim 0 \quad V_{GS} < V_T$$

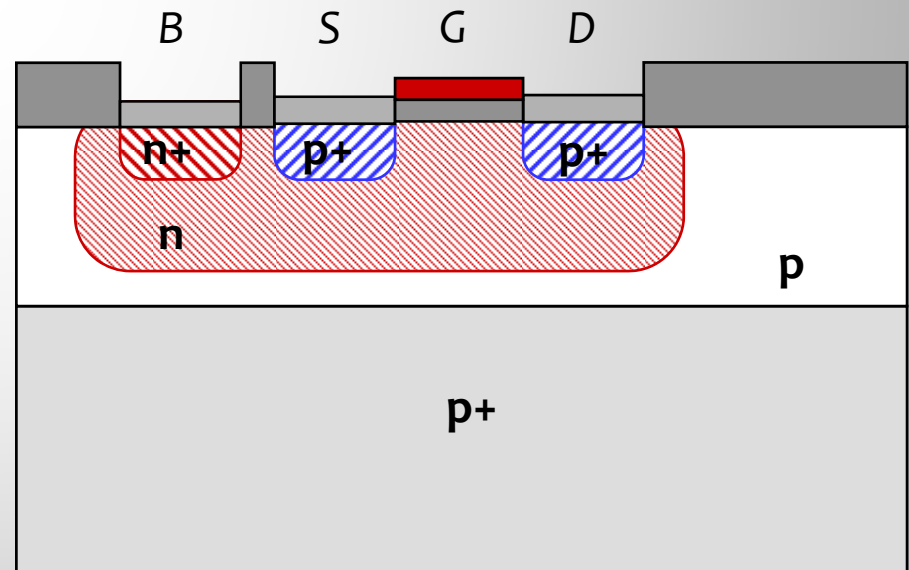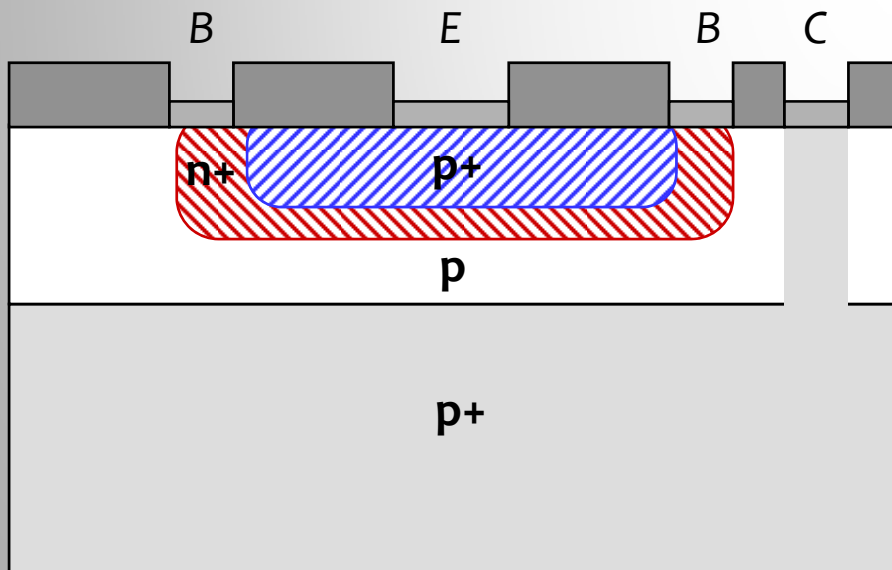

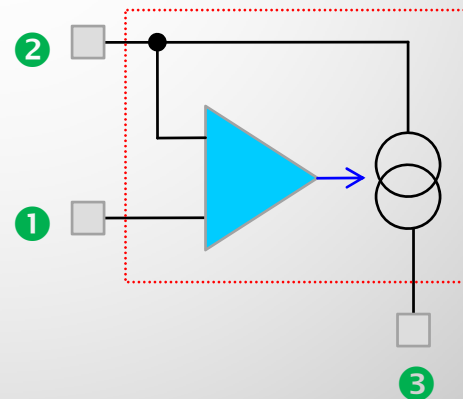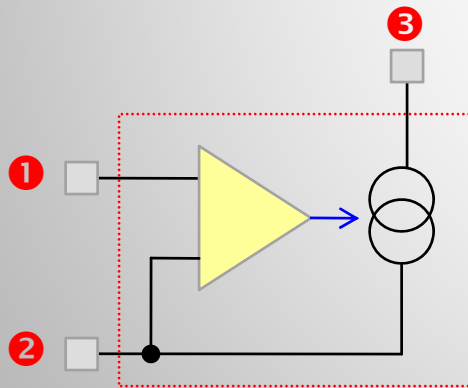
# Complementary devices

- ◆  $V_{\mathbf{1}} > V_{\mathbf{2}}$  in order to have current flow
- ◆ Complementary device has  $V_{\mathbf{1}} < V_{\mathbf{2}}$  in order to have current flow



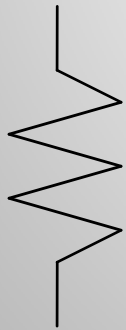
## Uses – current source

- ◆  $I_{OUT} = g_m V_{IN}$  (resistor,  $I_{OUT} = V_{OUT} / R$ )
- ◆  $I_{OUT}$  independent of  $V_{OUT}$  (for a perfect device)




$V_{IN}$

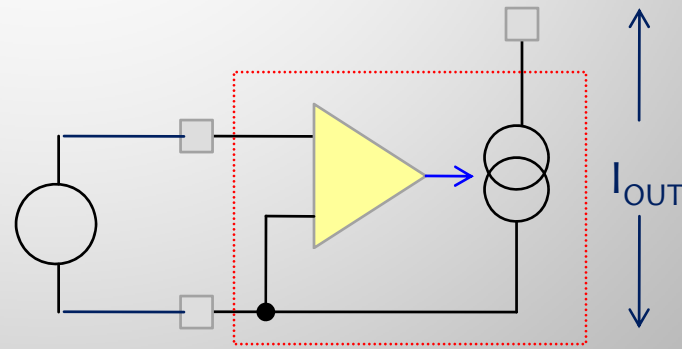



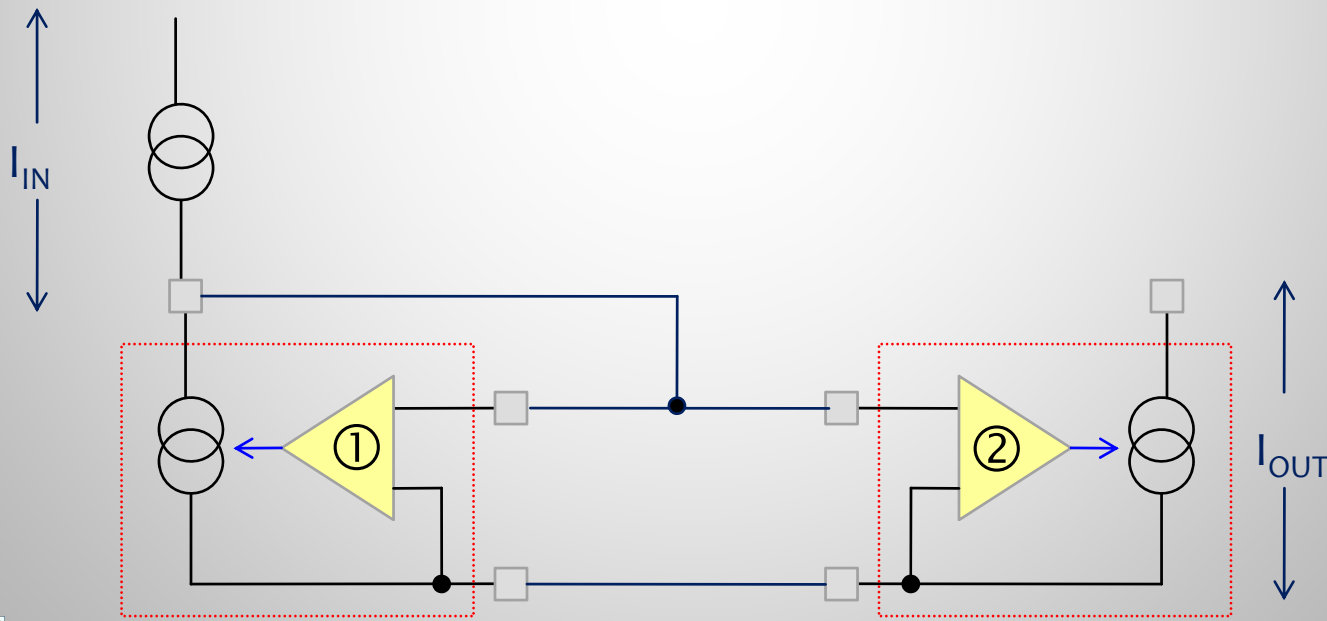
## Uses – current mirror

- ◆  $I_{IN}$  forces  $V_{IN①}$  such that  $I_{OUT①} = I_{IN}$
- ◆  $V_{IN②} = V_{IN①}$ , so that if  $② = ①$ , then  $I_{OUT②} = I_{IN}$
- ◆ (If  $② = M \times ①$ , then  $I_{OUT②} = M \times I_{IN}$ )




# Uses - preamplifier

Quiescent state



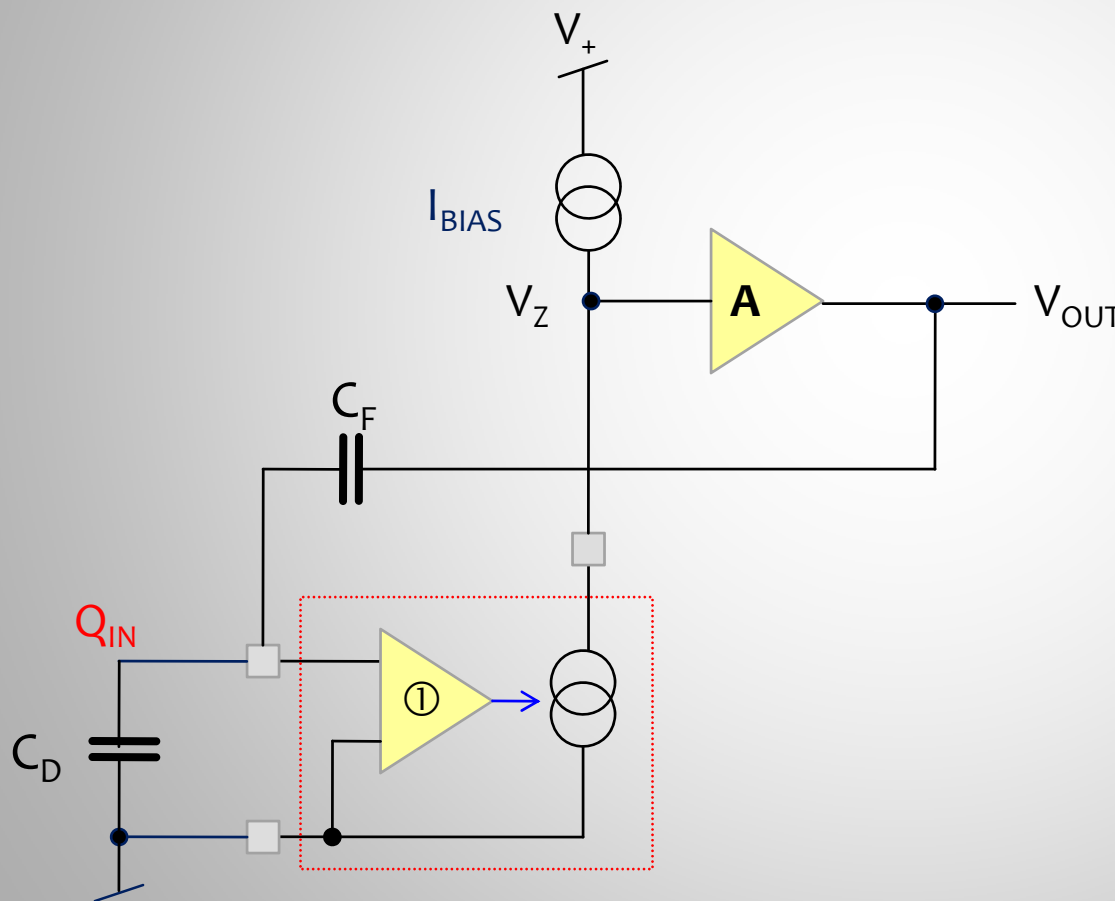


- ◆ A has high gain
- ◆  $I_{\textcircled{1}} = I_{\text{BIAS}}$  (quiescent)
  - $V_Z = V_+ / 2$
- ◆  $Q_{\text{IN}}$  arrives ( $\delta$  fn.)
  - $\Delta V_{\text{IN}} = Q_{\text{IN}} / C_D$
- ◆  $I_{\textcircled{1}} \rightarrow I_{\text{BIAS}} + g_m \Delta V_{\text{IN}}$ 
  - $V_Z \rightarrow$  rail
- ◆ Feedback current  $C_F \frac{dV_{\text{OUT}}}{dt}$  replenishes charge

# Helmuth's Example

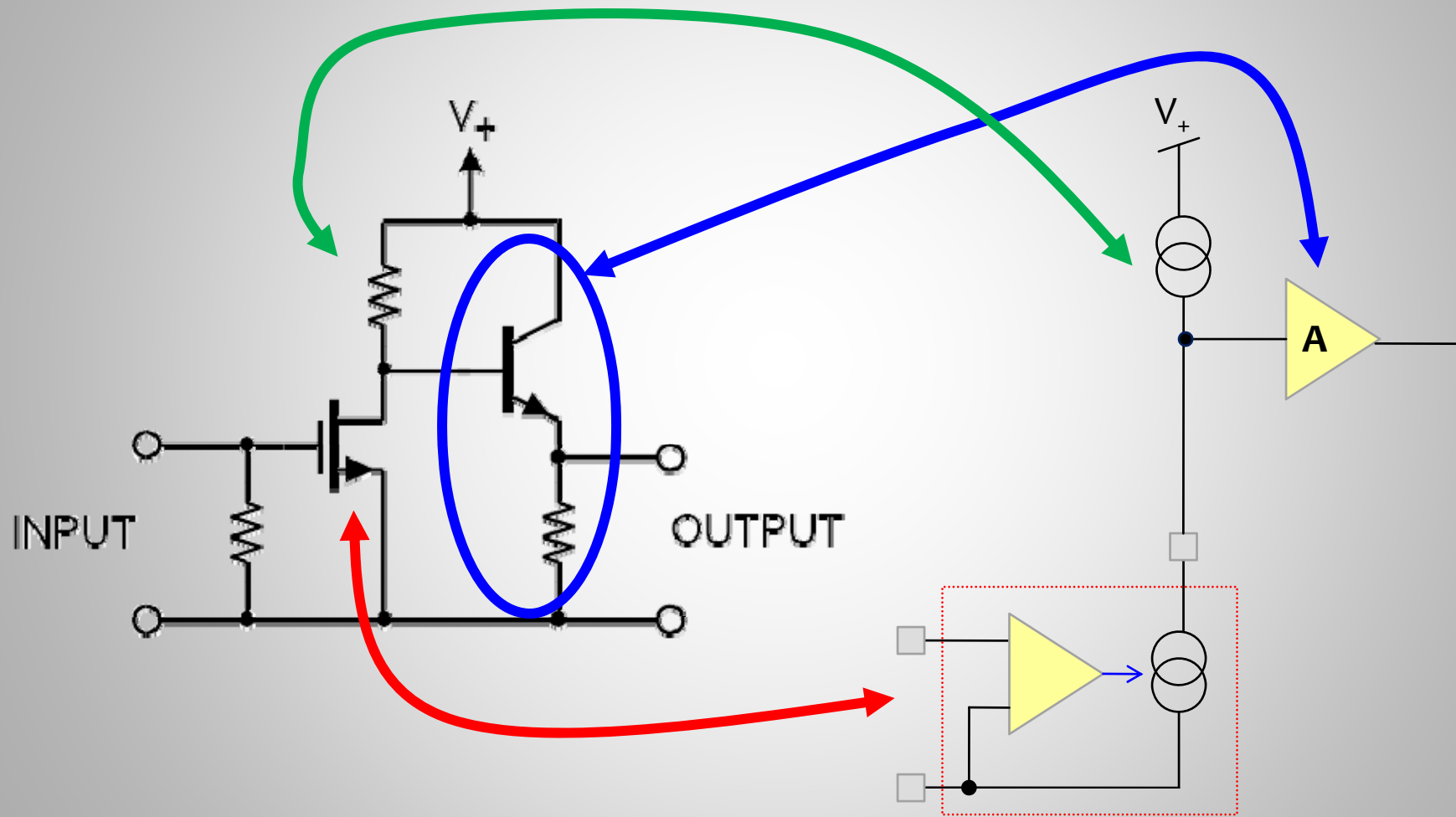

# Emitter/Source Follower

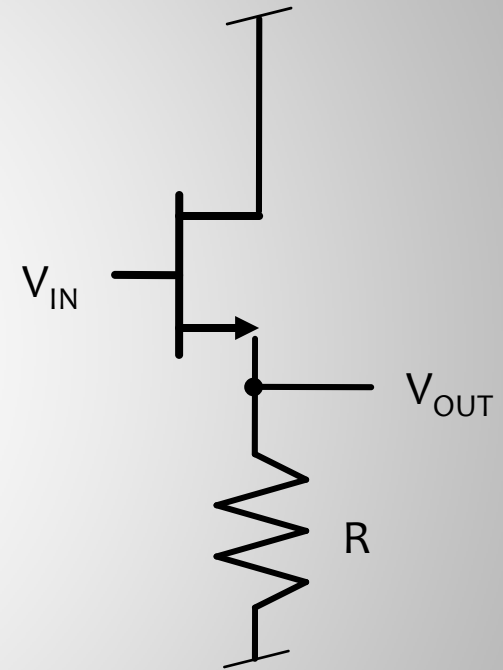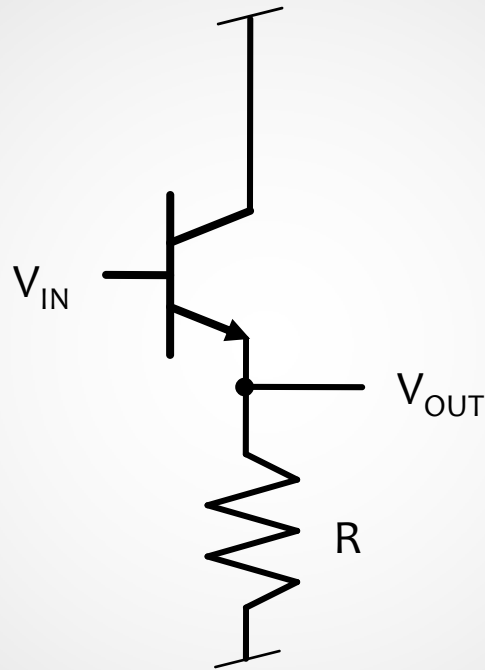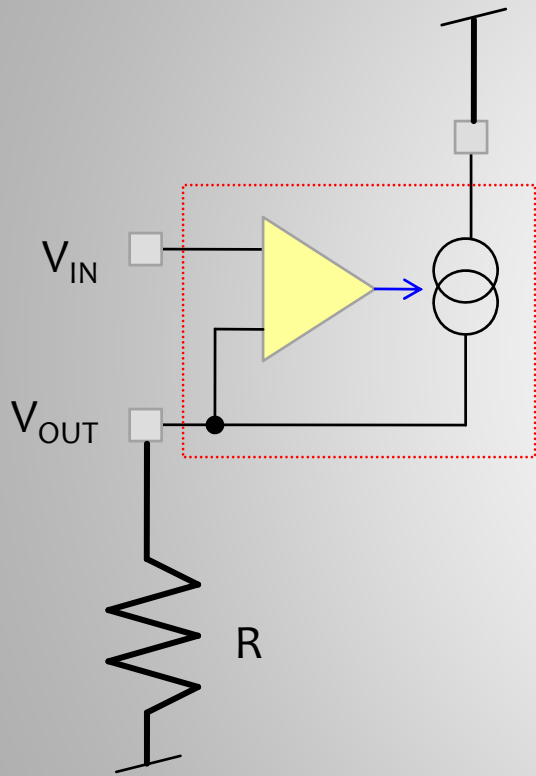



$$V_{OUT} = IR = g_m(V_{IN} - V_{OUT})R$$

$$A = \frac{g_m R}{1 + g_m R} < 1$$


# Improve

$$\Delta V_Z = R_G g_m \Delta V_{IN}$$






Maximize  $V_Z$  by making  $R_G$  big

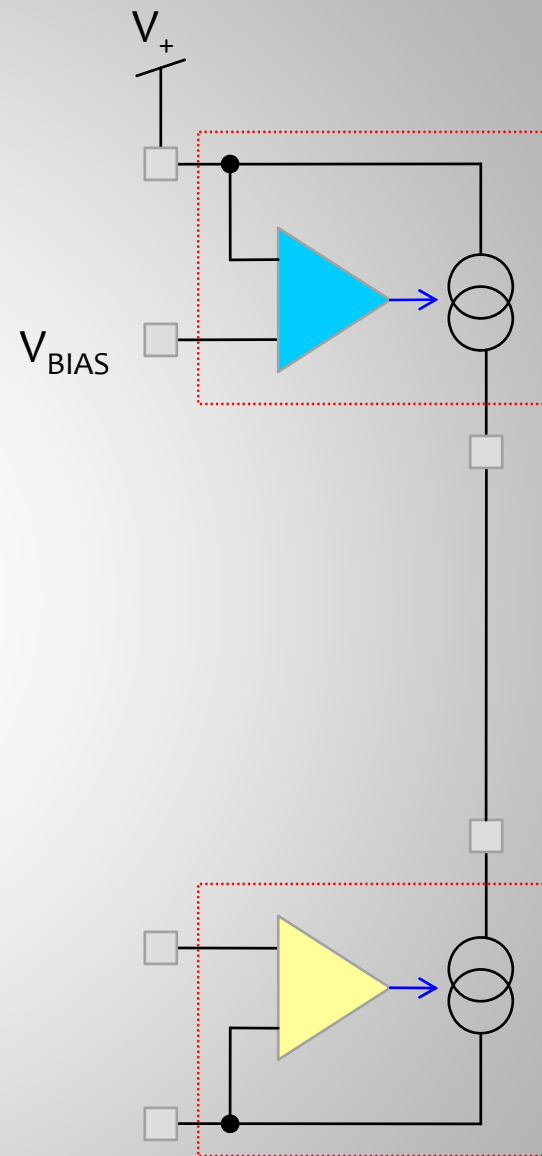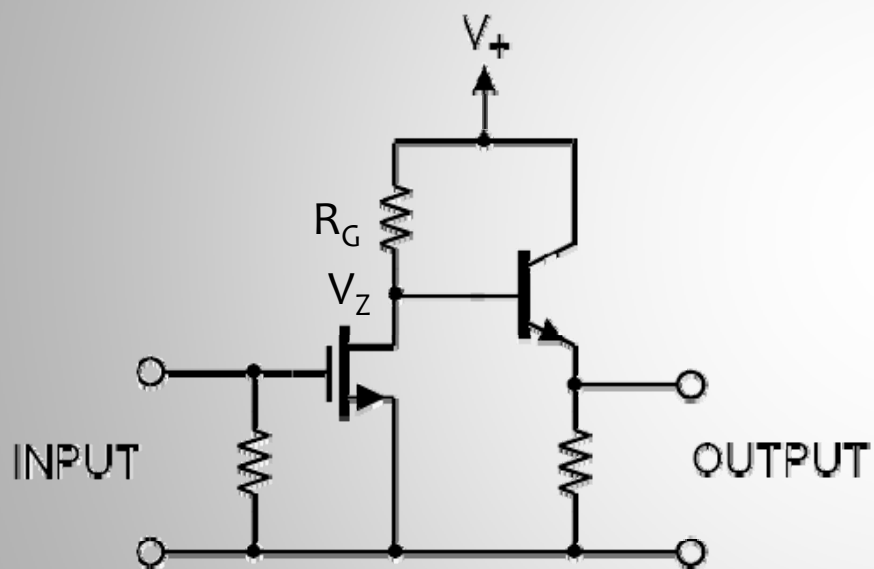

# How about this?

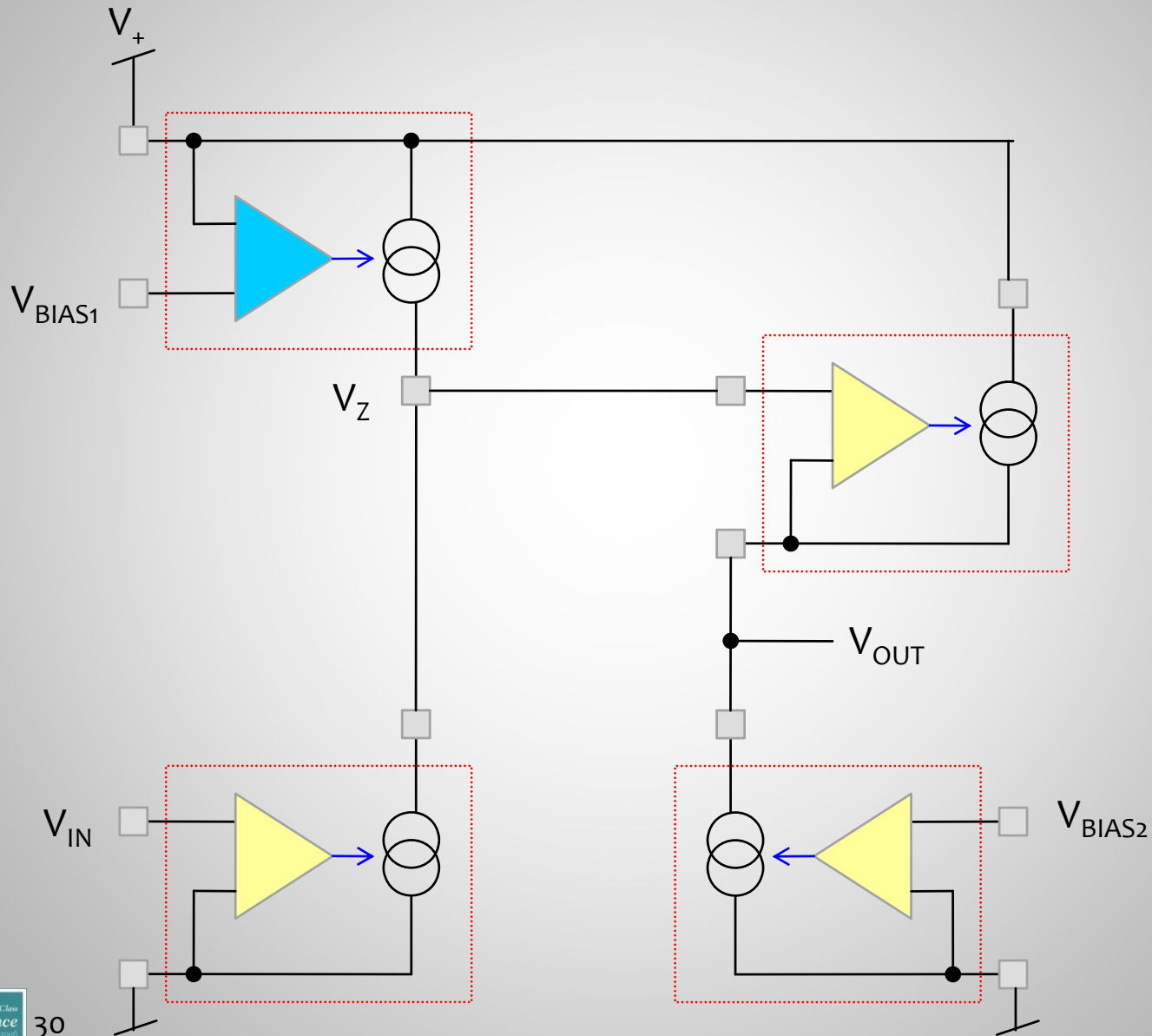

# Small problem

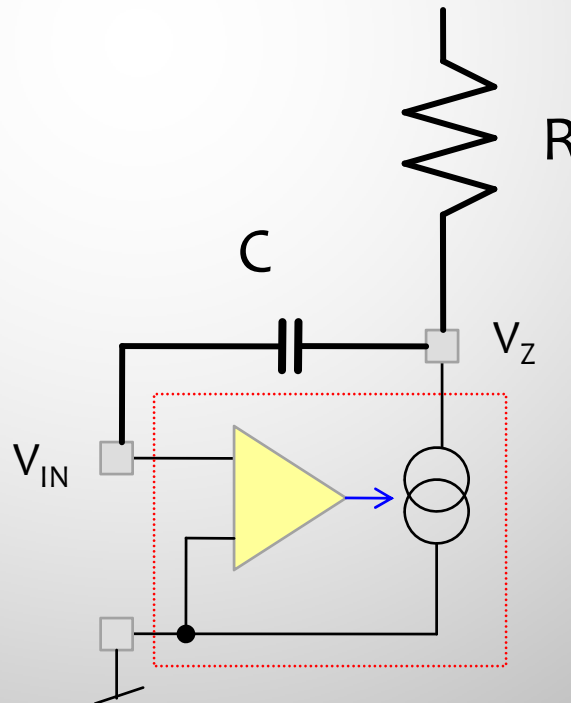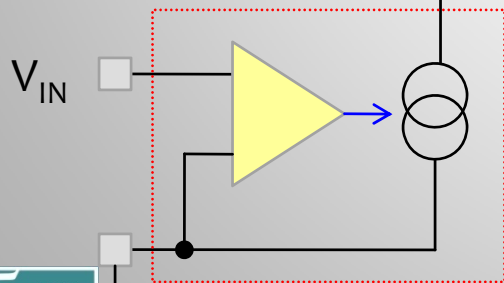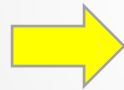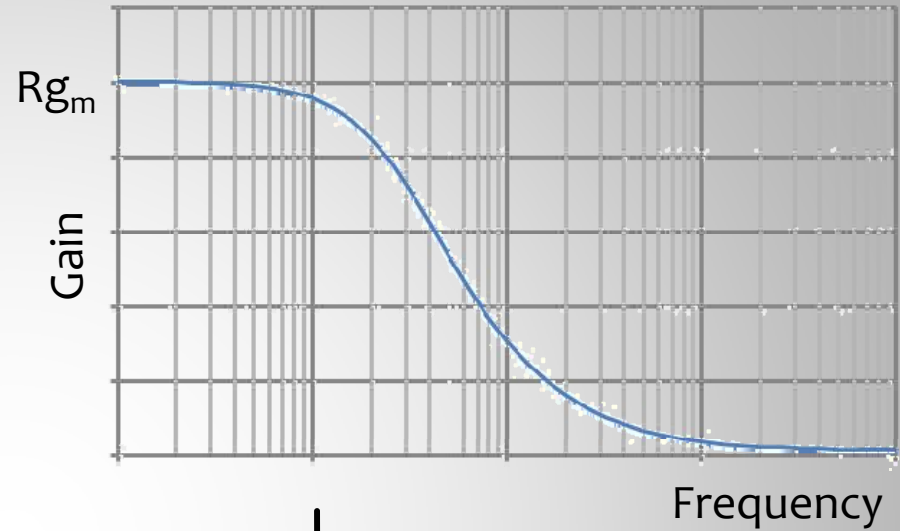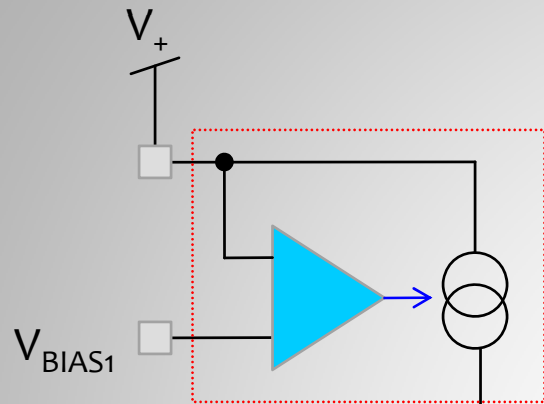

Even small  $C$   
kills gain  
(Miller effect)

# Uses - cascode


*“cascade to cathode”*

◆  $I_{\textcircled{2}} = g_m V_{\textcircled{2}}$

◆  $I_{\textcircled{1}} = I_{\textcircled{2}}$


◆  $V_{\text{OUT}\textcircled{2}} = V_{\textcircled{1}} - g_m I_{\textcircled{1}}$

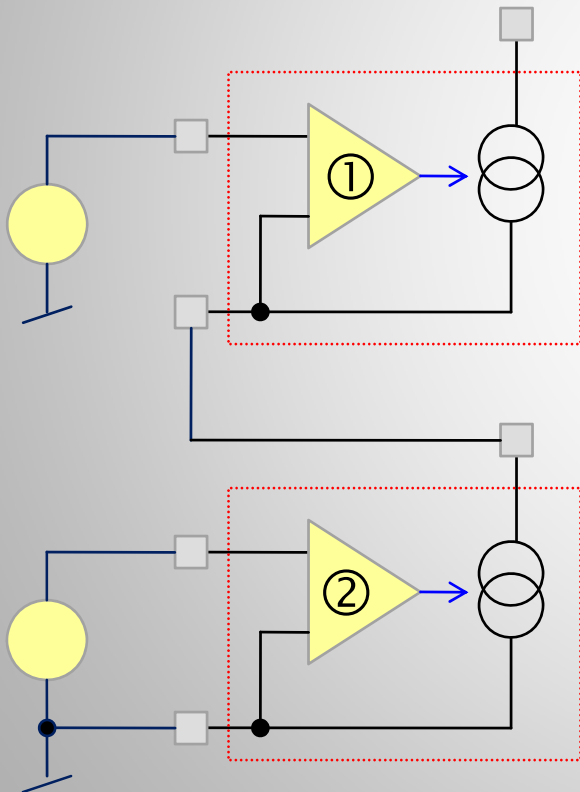◆ Output of  $\textcircled{2}$  doesn't move






# Folded cascode preamplifier

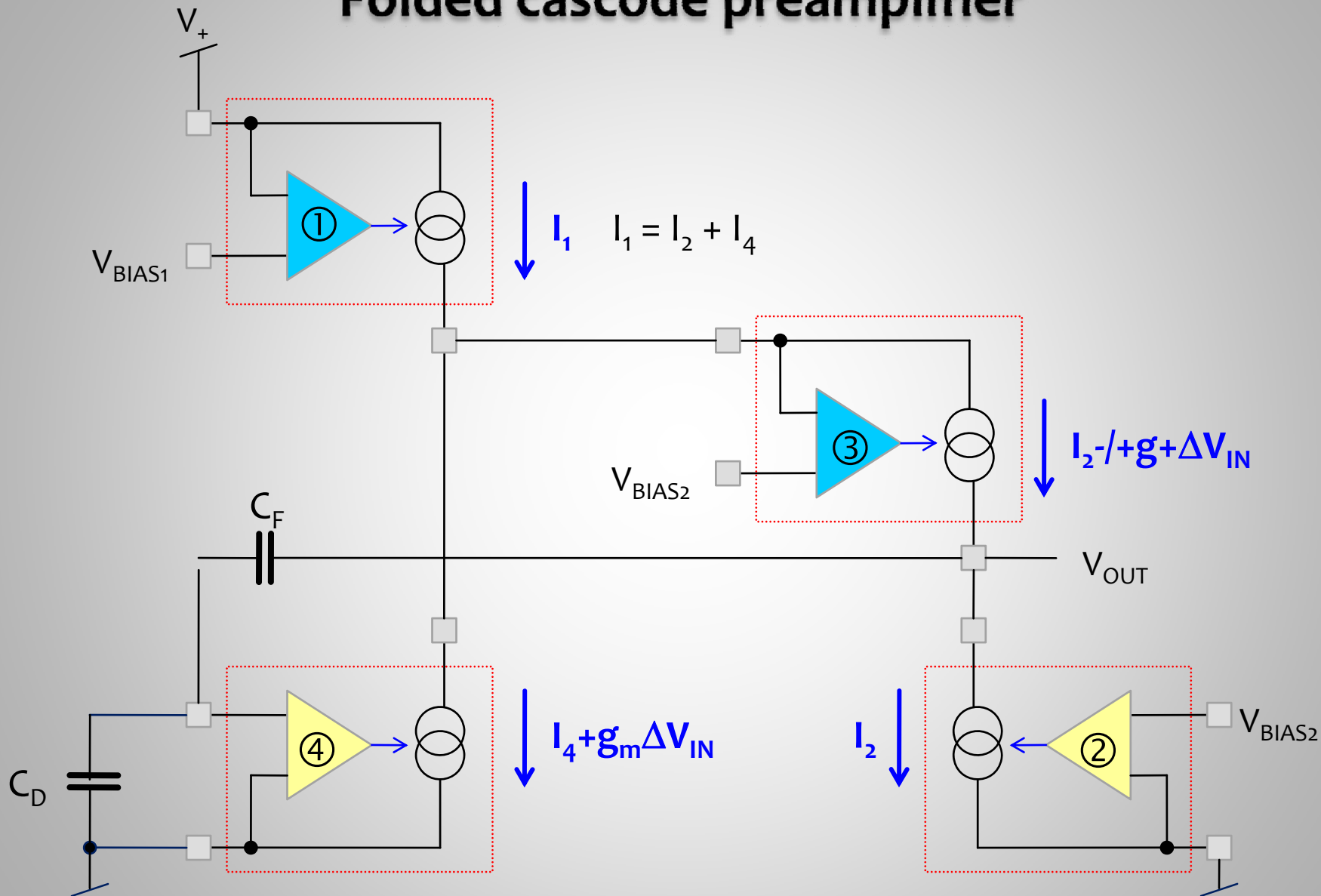

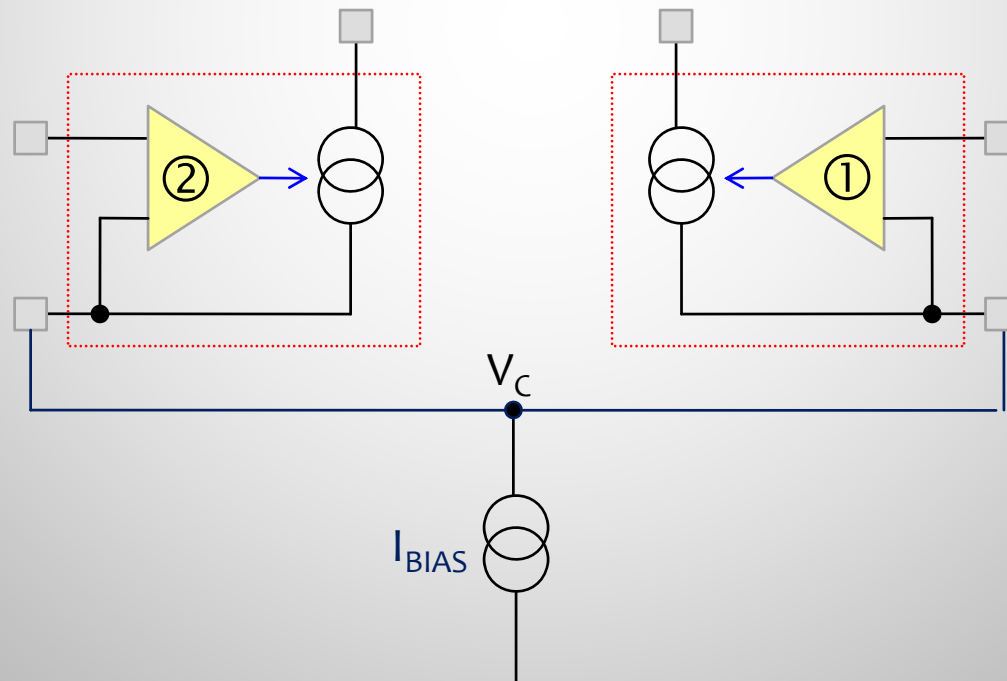
## Uses – differential stage


- ◆  $I_{\textcircled{2}} = g_m(V_{\text{IN}\textcircled{2}} - V_C)$ ,  $I_{\textcircled{1}} = g_m(V_{\text{IN}\textcircled{1}} - V_C)$
- ◆  $I_{\textcircled{1}} - I_{\textcircled{2}} = g_m(V_{\textcircled{1}} - V_{\textcircled{2}})$
- ◆  $I_{\text{BIAS}} = I_{\textcircled{1}} + I_{\textcircled{2}}$



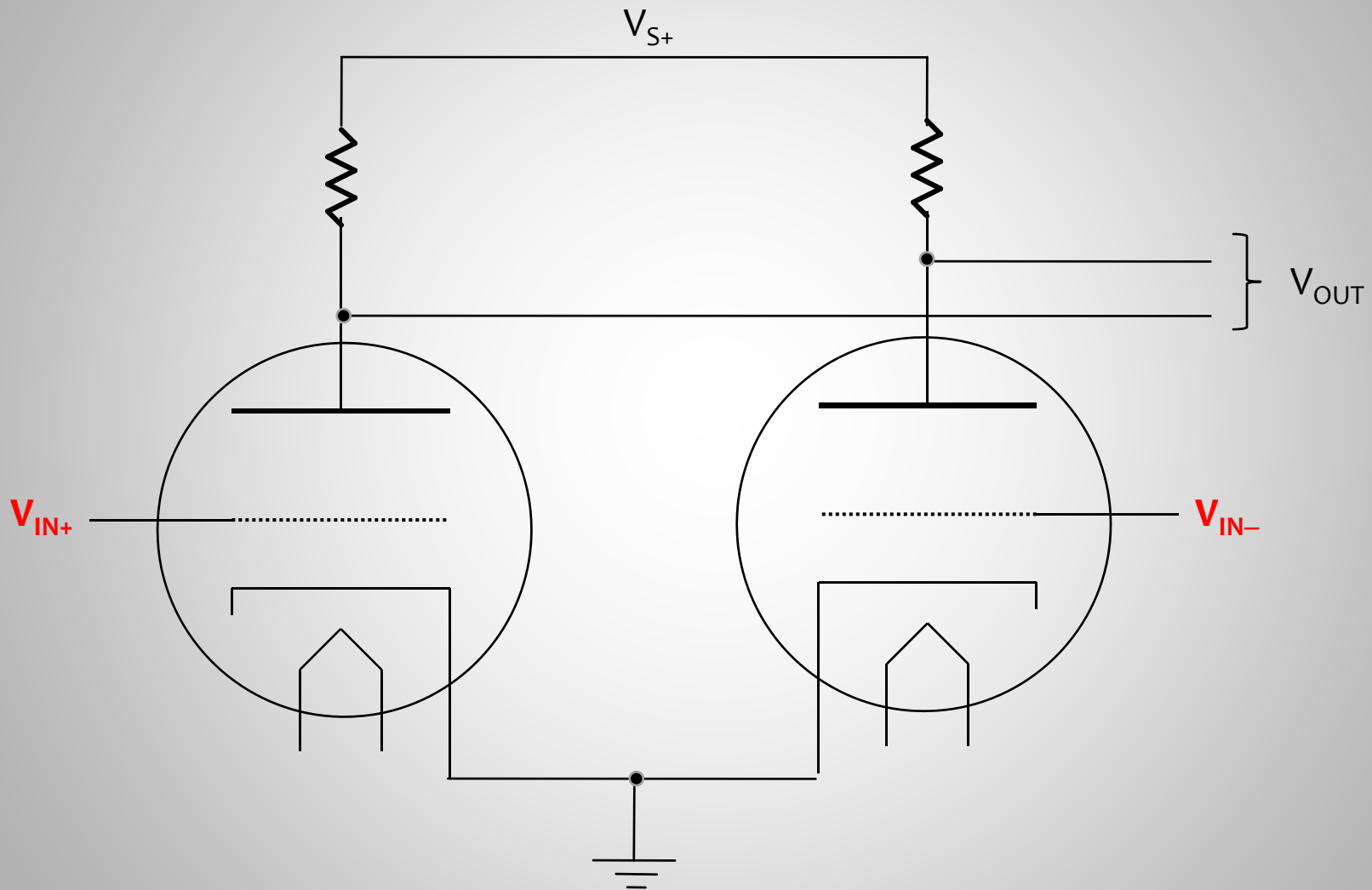
# 1938 – J.F. Toennies – The Long-Tailed Pair




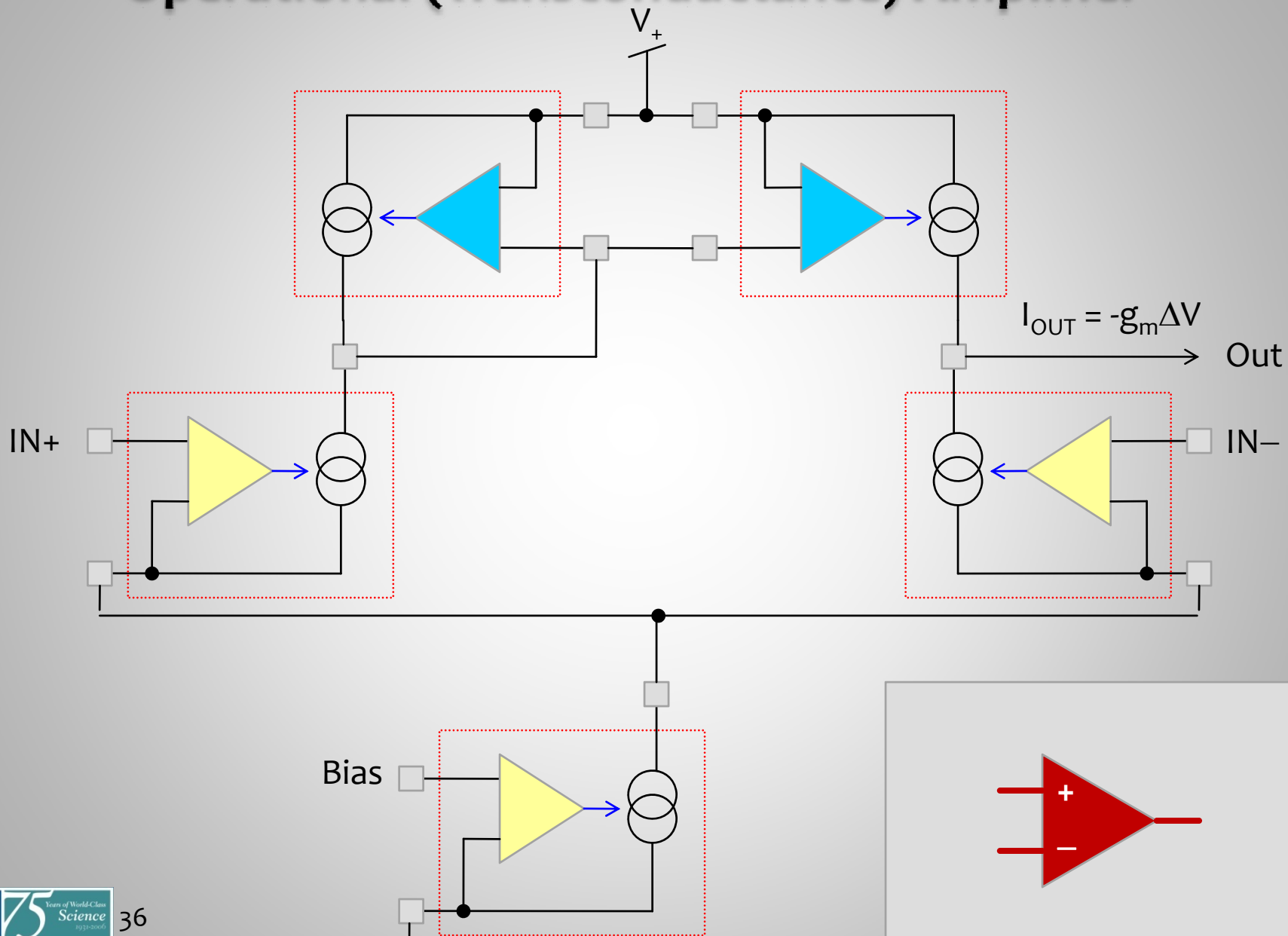
# Operational (Transconductance) Amplifier



# Rail-to-Rail OTA

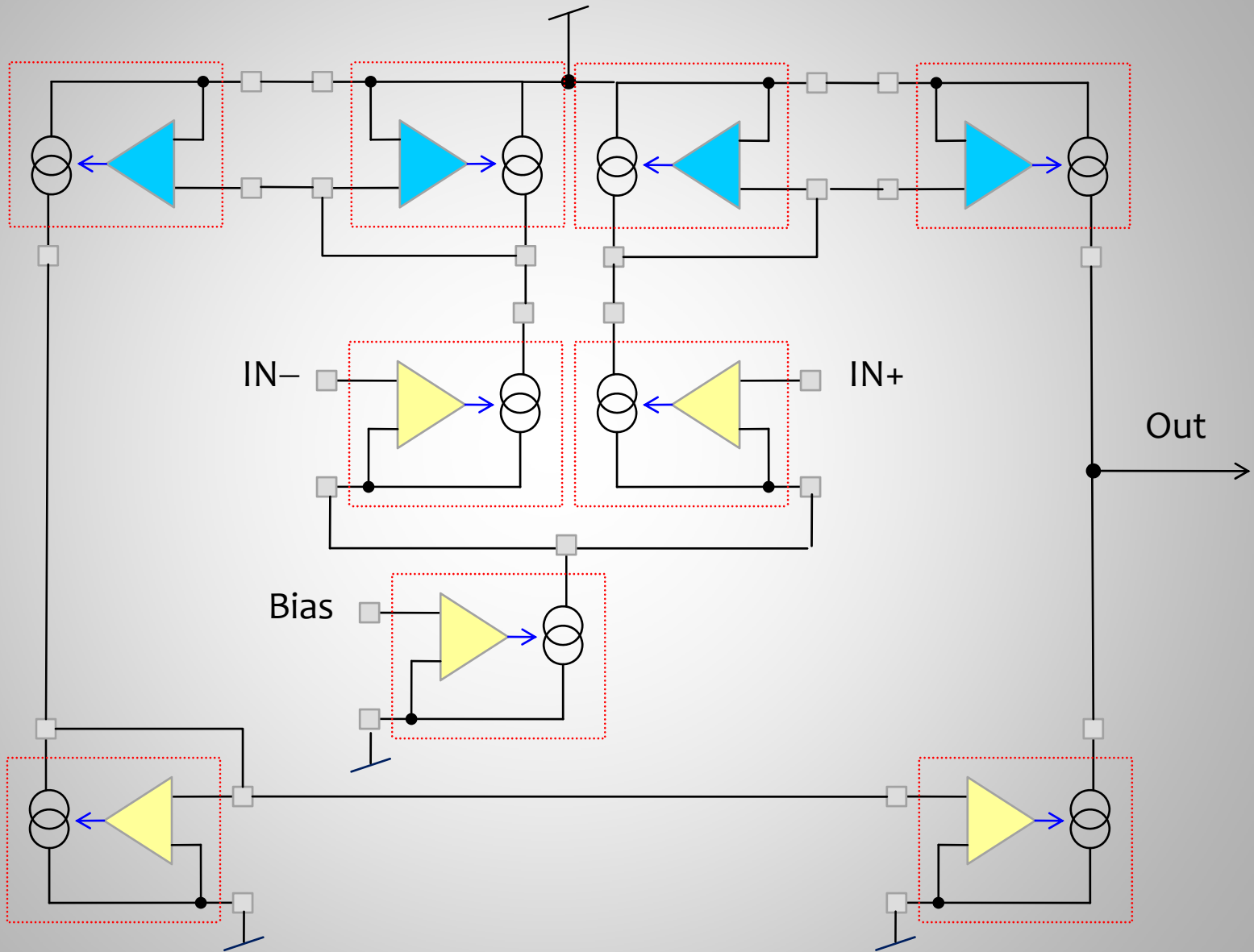


# Operational amplifier

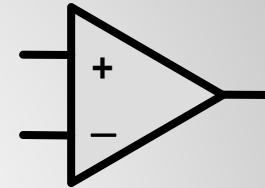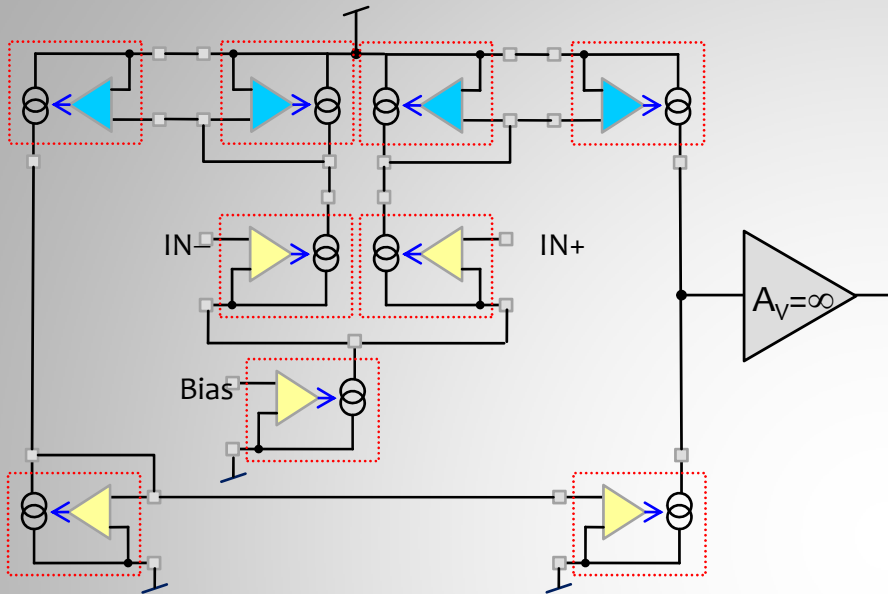


$$V_{OUT} = A_V (V_+ - V_-)$$

(Assume  $A_V = \infty$ )

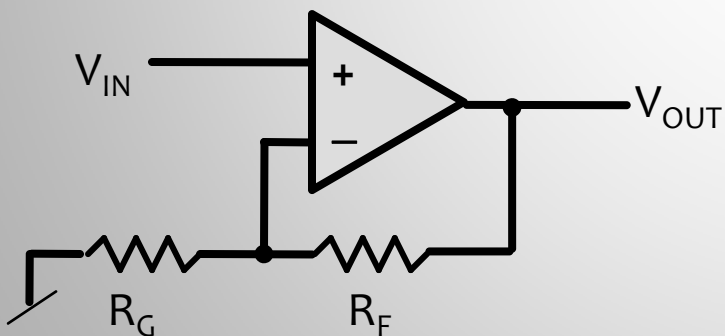



$$V_{OUT} = (1 + R_F/R_G)V_{IN}$$

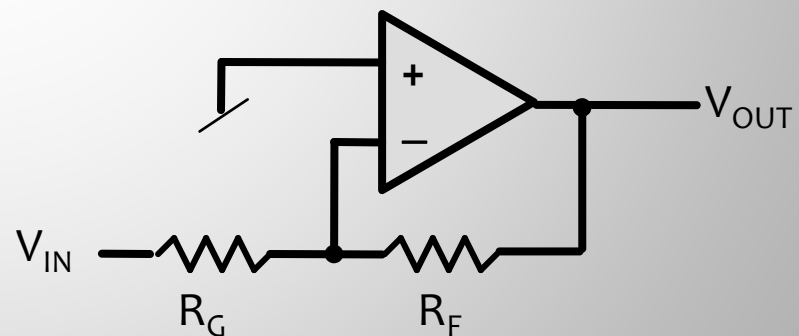


$$V_{OUT} = -(R_F/R_G)V_{IN}$$

# Uses - switch



No more “generic” transconductor

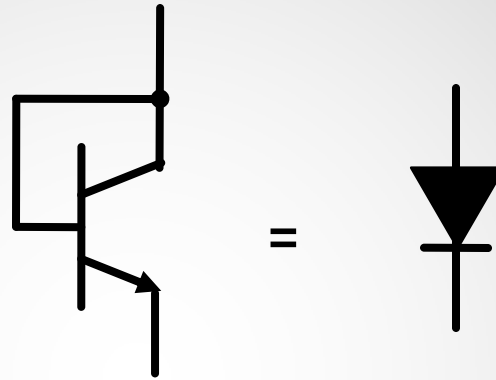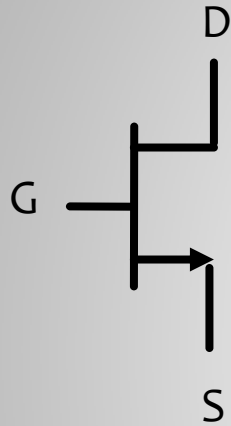
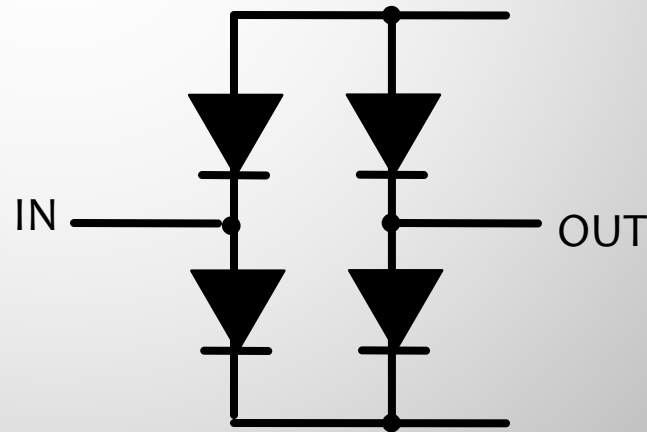
$$I_{DS} = k(V_{GS} - V_T)^2 \text{ for } V_{DS} > V_{GS} - V_T$$
$$I_{DS} = 2k(V_{GS} - V_T)V_{DS}$$
$$\rightarrow R_{DS} = V_{DS} / I_{DS}$$




# Digital logic

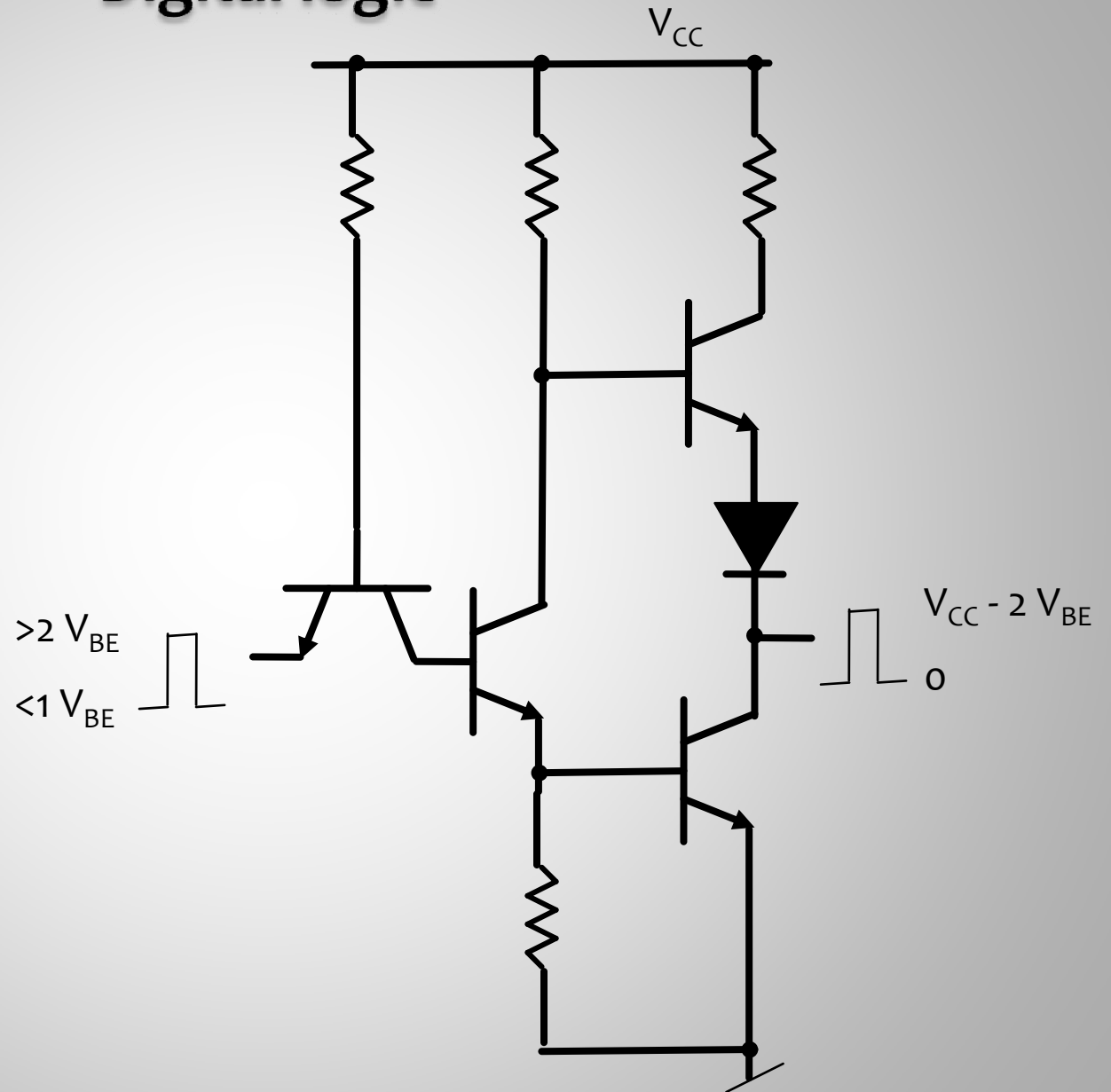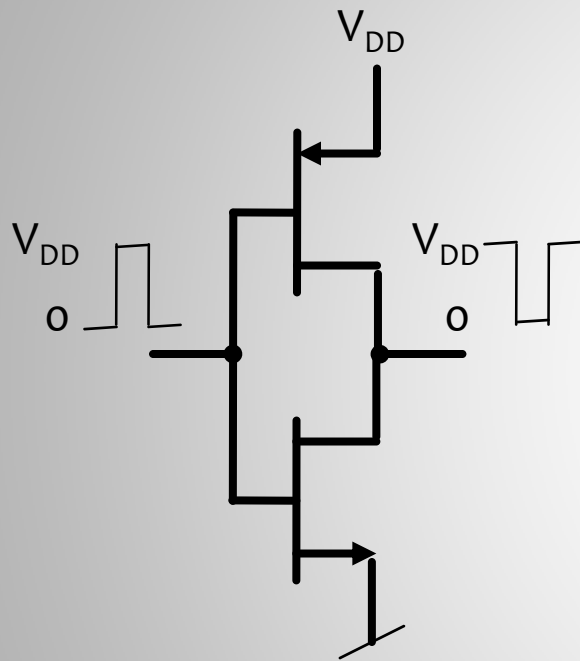




# NOR gate - TTL

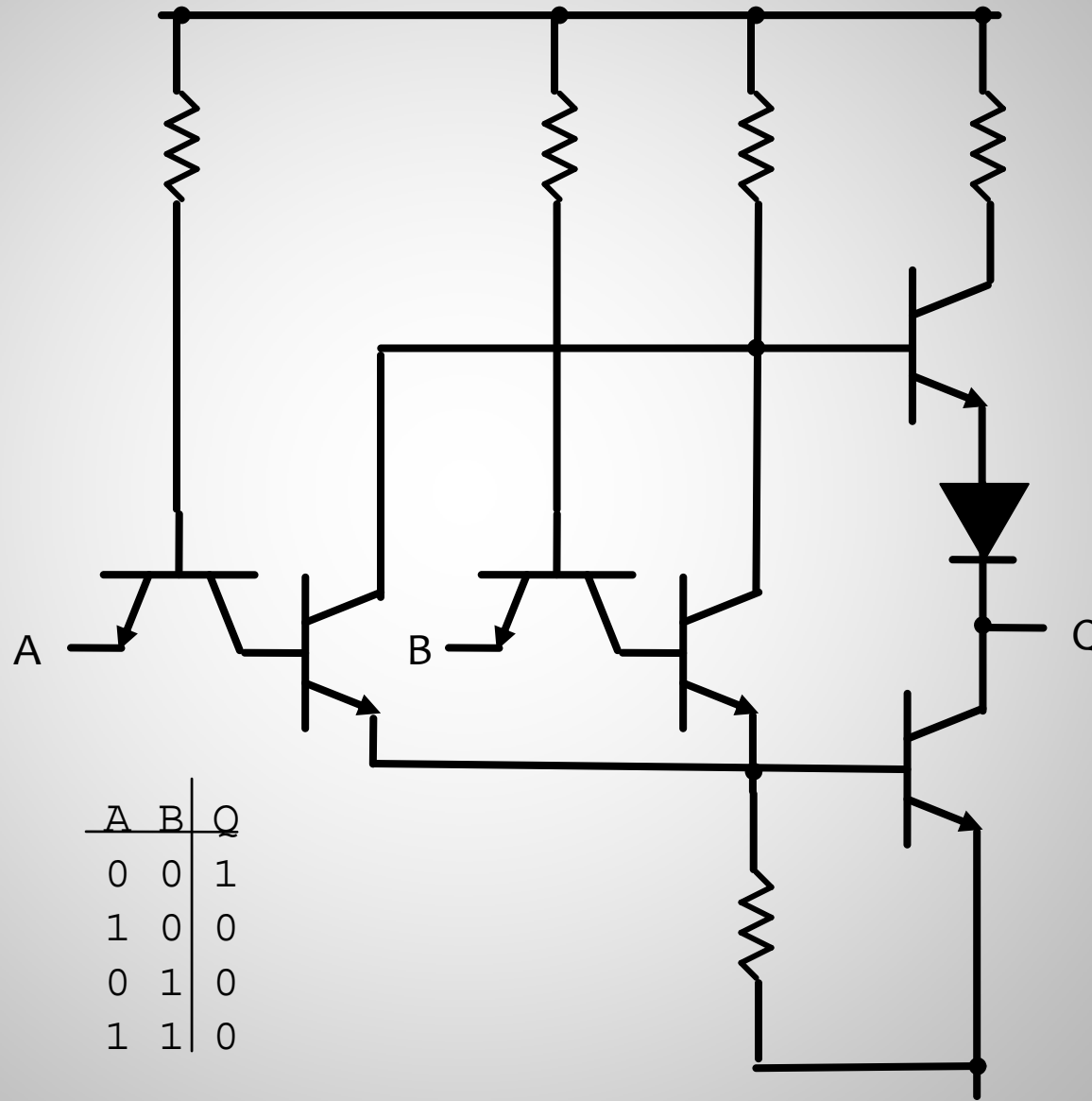


## NOR gate – ECL

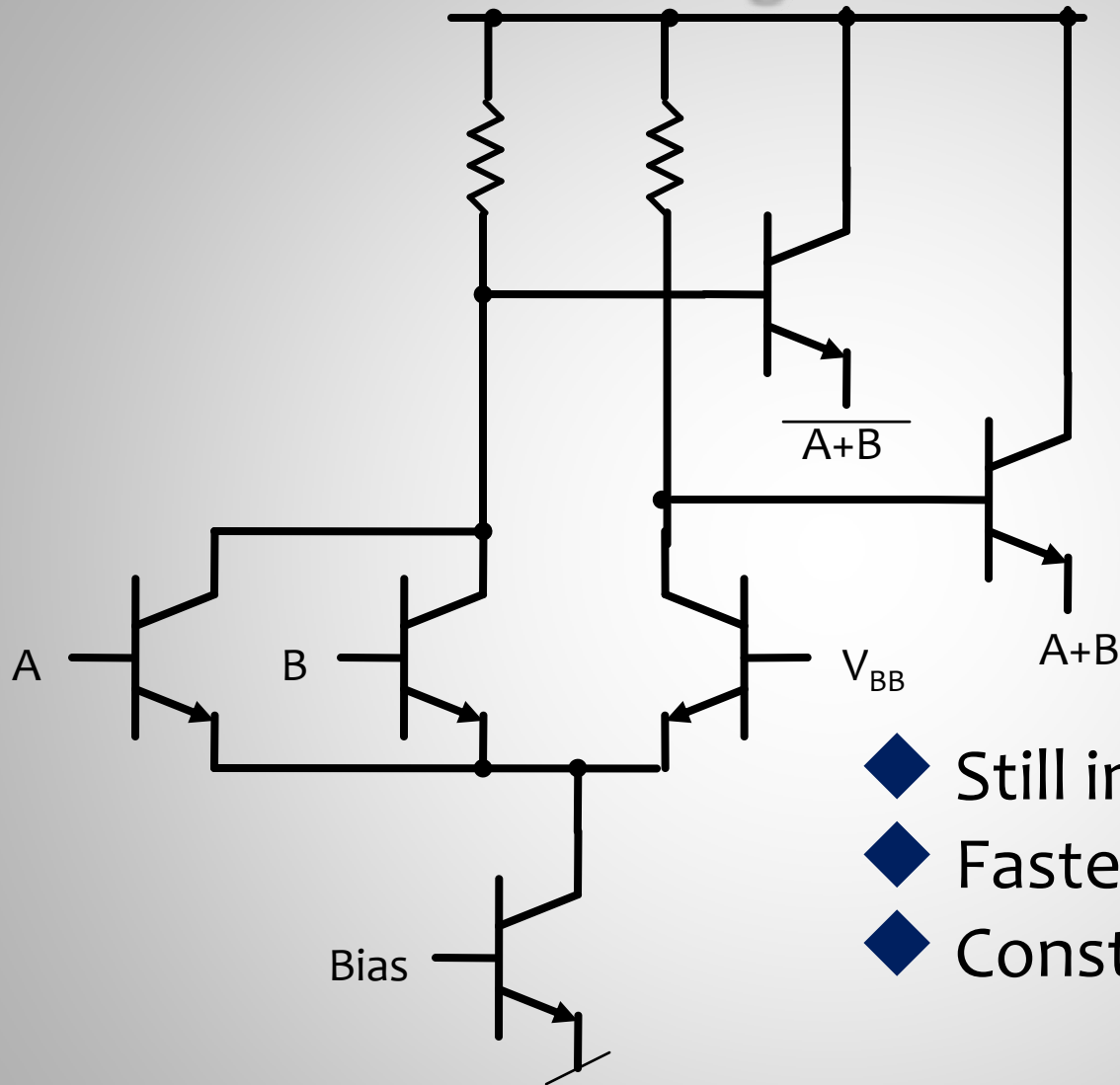

- ◆ Still in use
- ◆ Fastest logic family
- ◆ Constant current

# NOR gate - CMOS

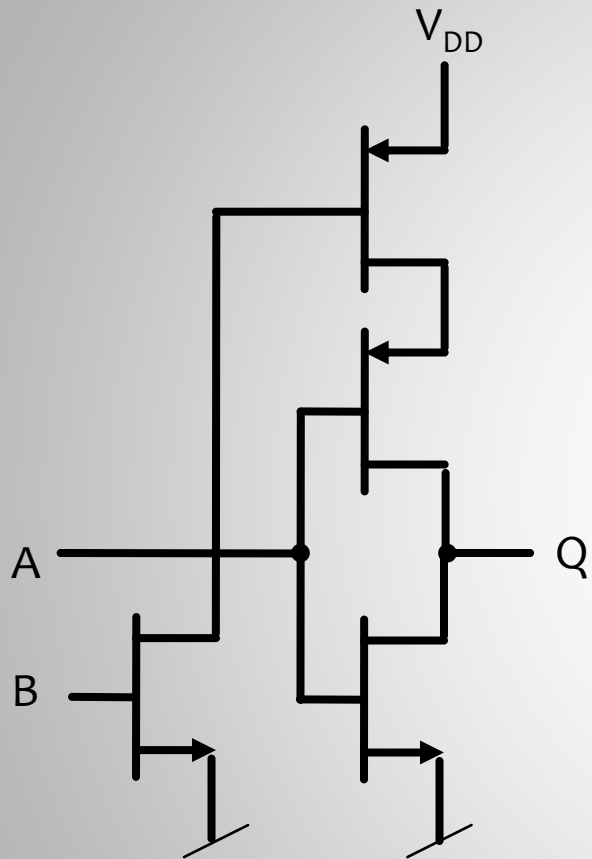

## ◆ CMOS logic dominant

- Easiest to manufacture
- No static power


## ◆ Dynamic power:

$$I \sim fCV_{DD}^2$$

## ◆ CMOS scaling


- Feature size reduction
- $V_{DD} \downarrow$
- Transistors/Area  $\uparrow$
- Microprocessor fans are a good business

# Comparator

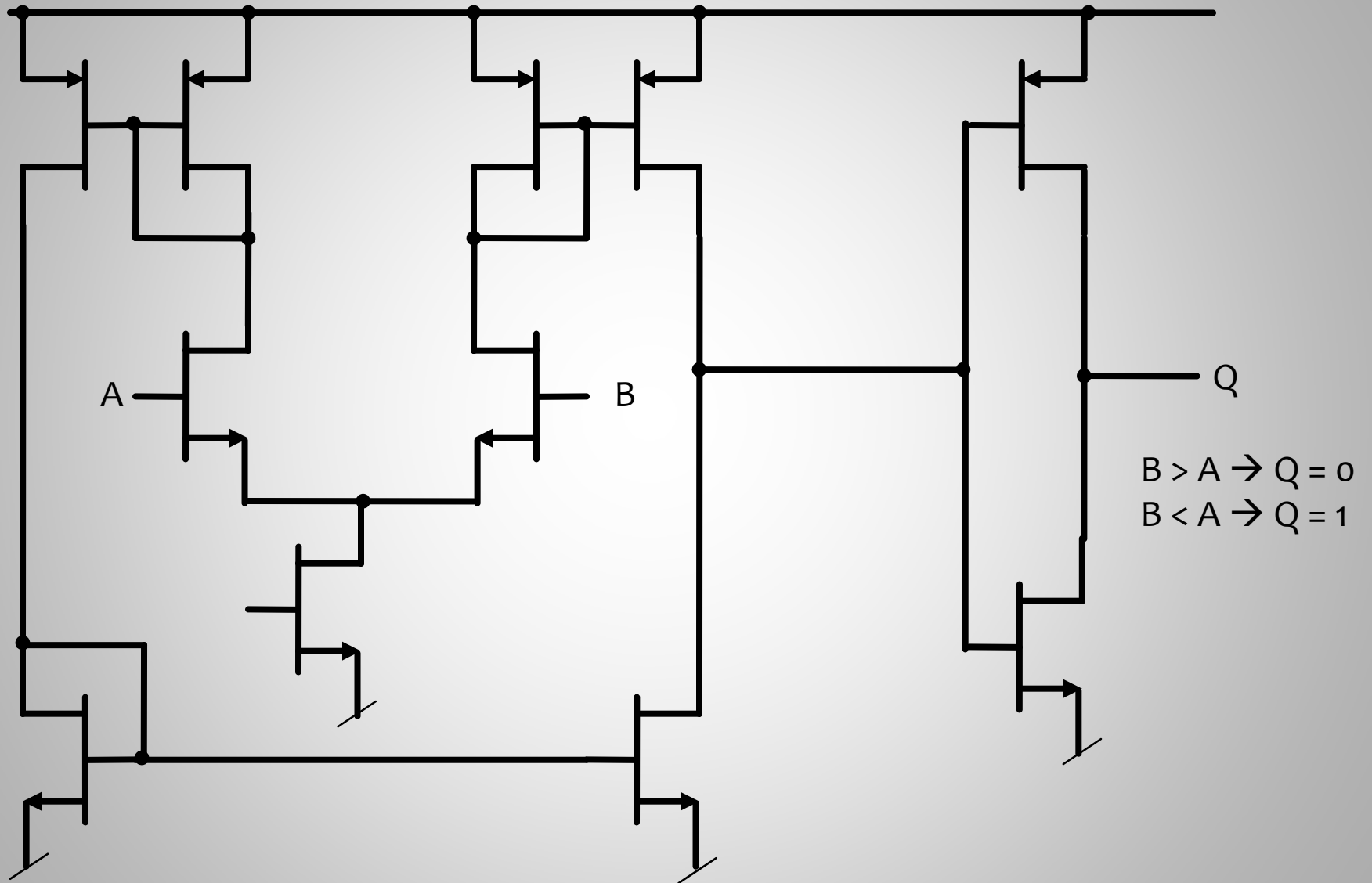

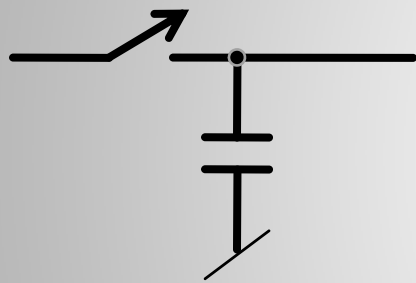
# Mixed-mode design


- ◆ The majority of “Front-end electronics for detectors and imagers”
- ◆ Switches are key components



Sample / hold  
(track / hold)

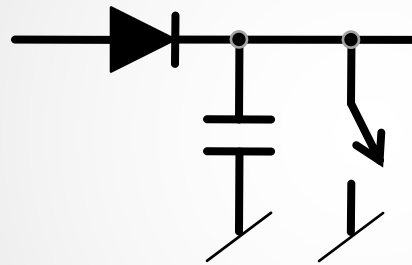

Peak detector

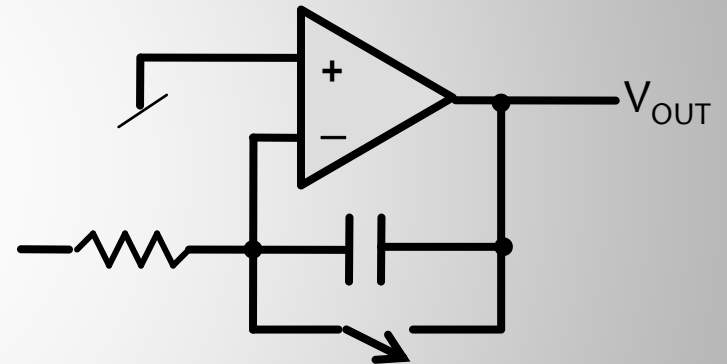


Gated integrator

# DAC

## R-2R ladder


Bipolar or CMOS

Laser trimming of R-2R ladder


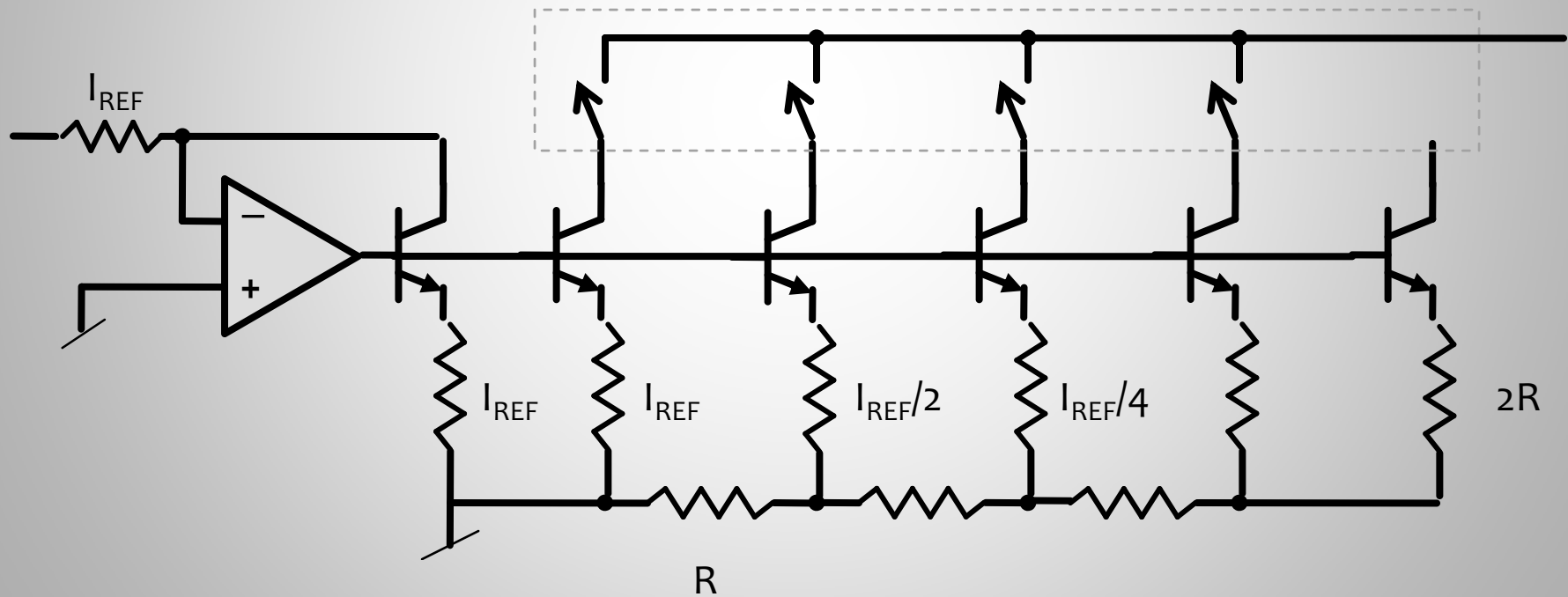


# Consider 3 examples which can be either "detectors" or "imagers"

Hybrid

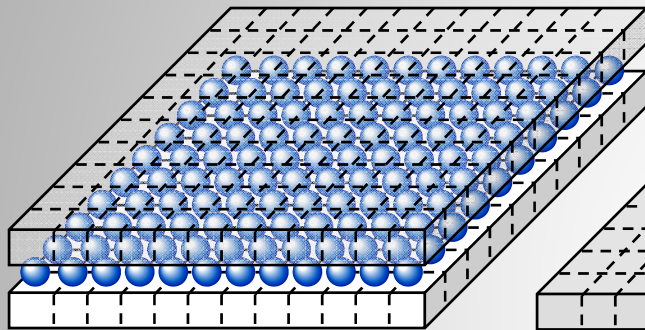

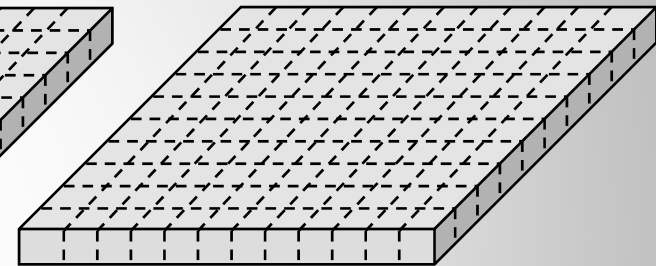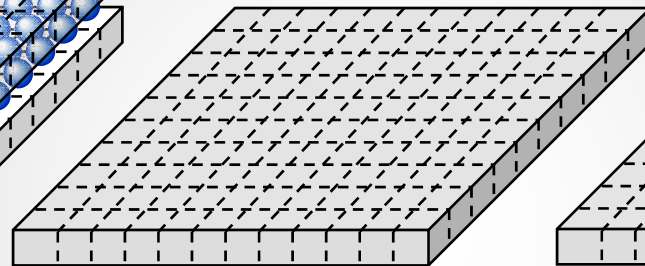Monolithic  
sensor+readout  
on same substrate



APS

CCD



Increasing complexity

- ◆ Particle tracking ( $x, y, t$ )
- ◆ Particle spectroscopy ( $x, y, E$ )
- ◆ Imaging  $N(x, y)$ 
  - Optical photons, x-rays, electrons, neutrons (with convertor)

# Scientific CCDs



Dumbbell nebula - LBNL CCD

Blue: H- $\alpha$  at 656 nm

Green: SIII at 955 nm


Red: 1.02  $\mu$ m



- ◆ CCD invented in 1969 by Boyle and Smith (Bell Labs) as alternative to magnetic bubble memory storage
- ◆ LST (“Large Space Telescope” – later Hubble) 1965 – how to image?
  - Film was obvious choice, but -  
It would “cloud” due to radiation damage in space  
Changing the film in the camera not so trivial
  - 1972 CCD proposed




# Integrated Circuit Elements

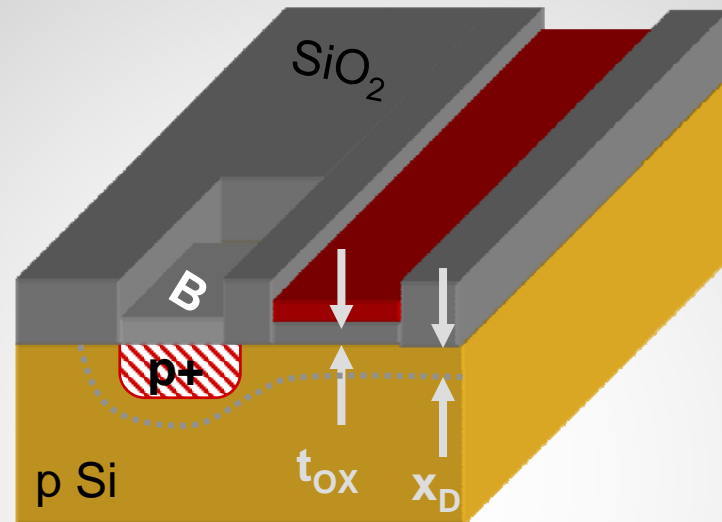


$$C = \frac{1}{\frac{1}{C_{OX}} + \frac{1}{C_{DEP}}}, \quad C_{OX} = \frac{\epsilon_{SiO_2}}{t_{OX}}, \quad C_{DEP} = \frac{\epsilon_{Si}}{x_D}$$

## MOS Capacitor


# Accumulate Charge

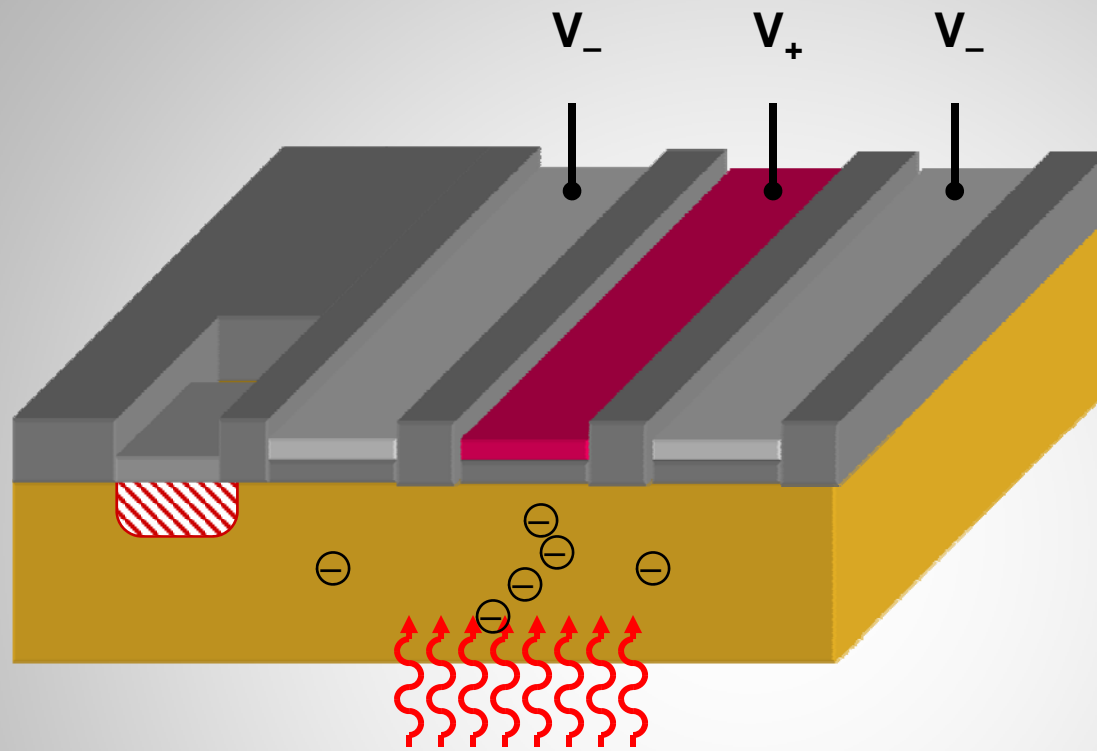

# Accumulate and Transfer Charge

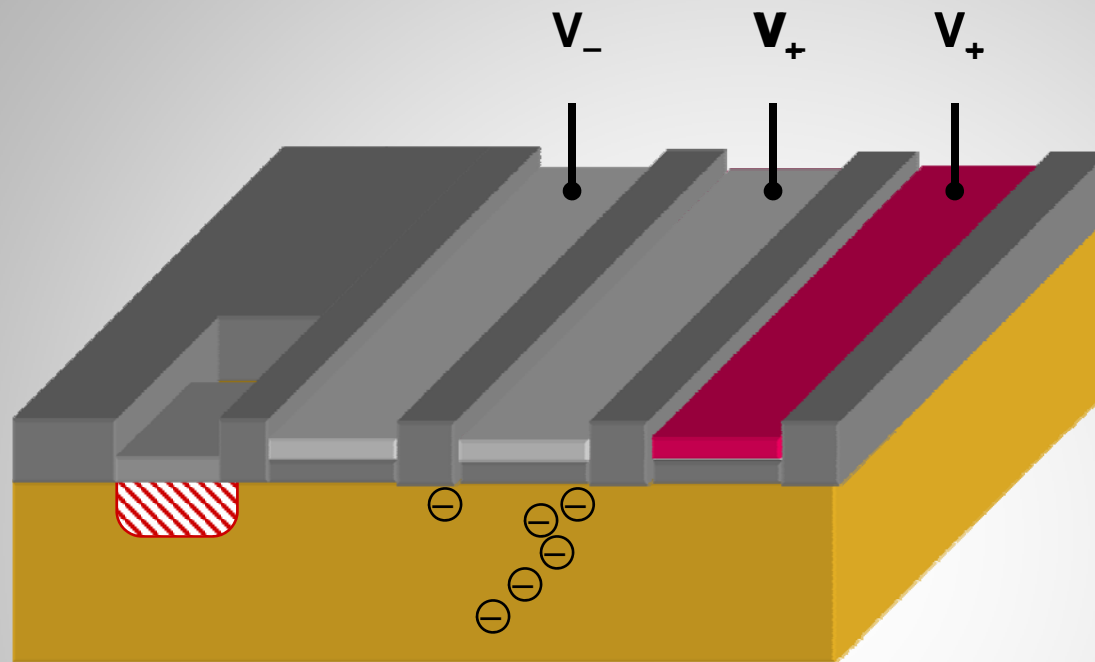


# Conventional 3-Phase CCD

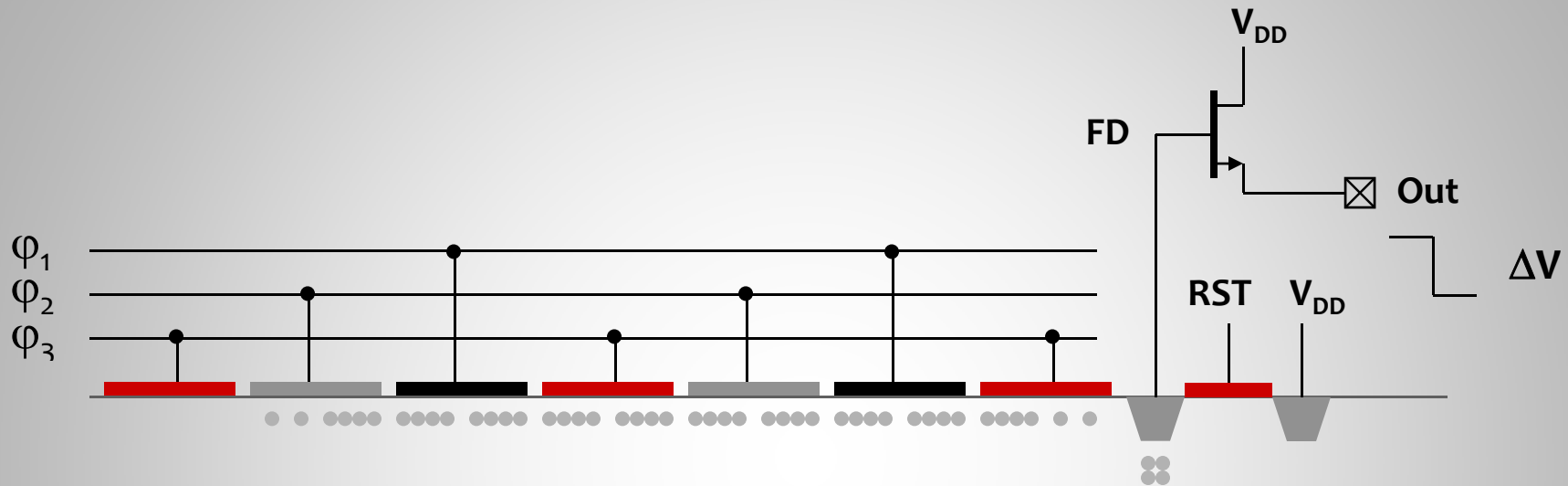


- ◆ Noiseless, ~lossless charge transfer
- ◆ High gain charge-to-voltage conversion  $\Delta V = q/C_{FD}$
- ◆ Output amplifier (source follower, or ...) on-chip

# Many ways to do this

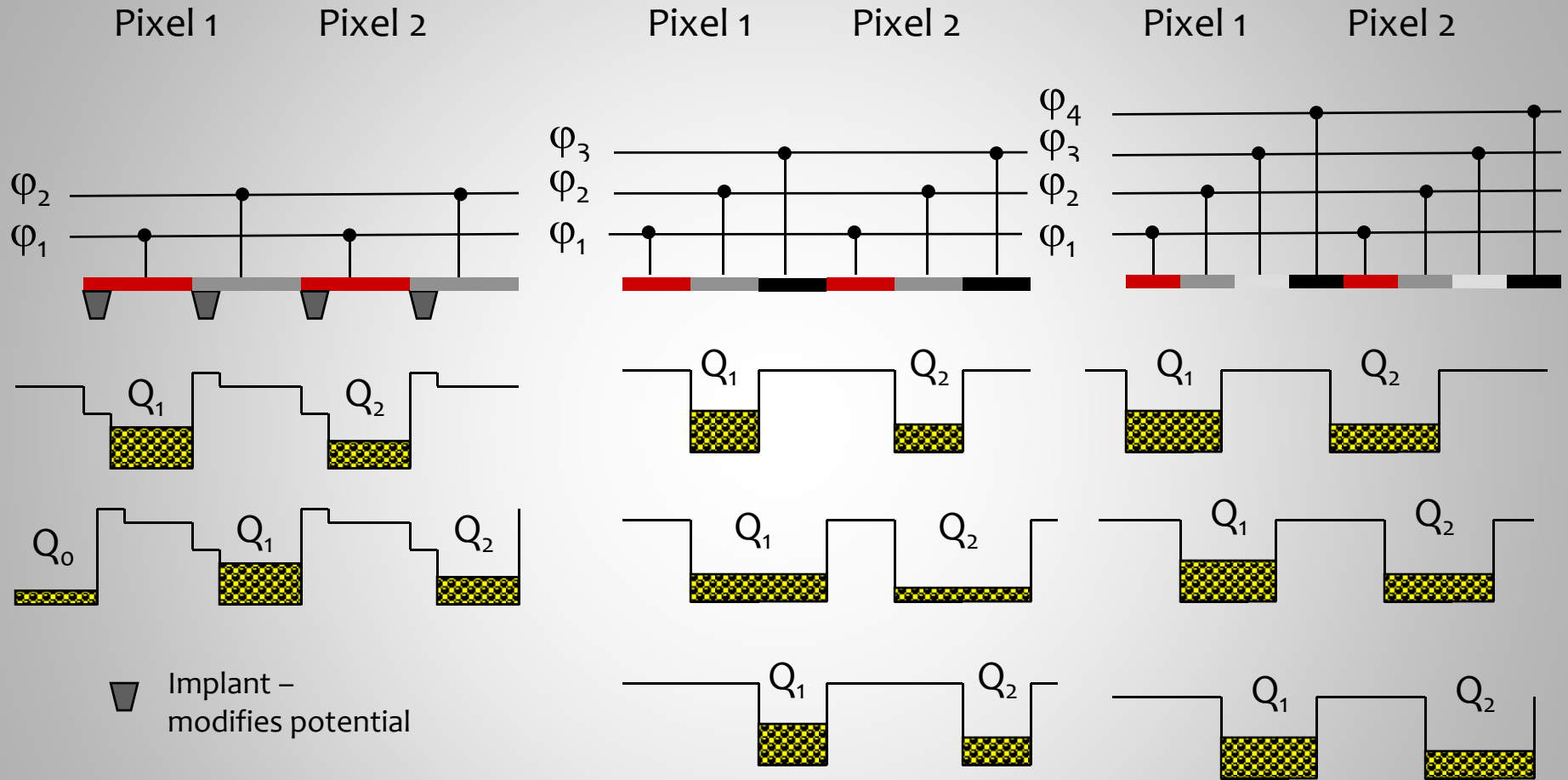


# Several architectures

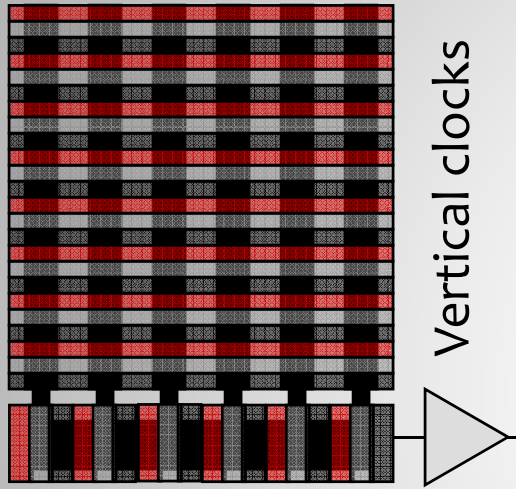


Horizontal clocks

Full frame

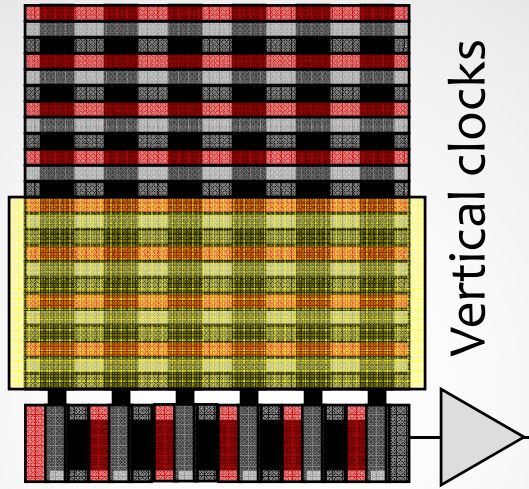

Horizontal clocks

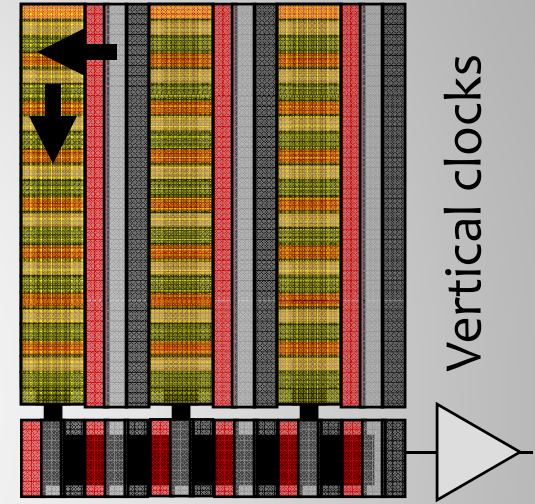Frame transfer  
Rapid shift from image  
to storage  
Slower readout of  
storage during integration




Horizontal clocks


Interline
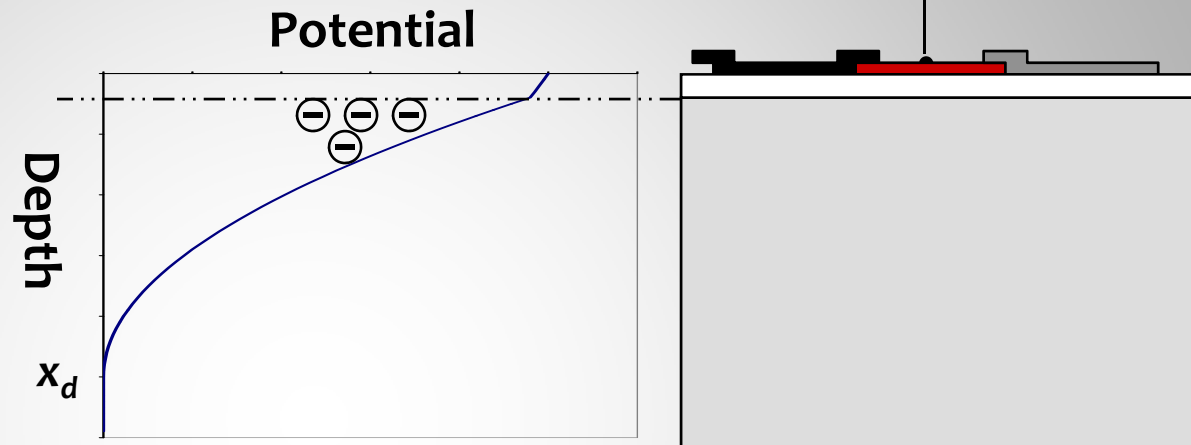
# Surface vs buried channel CCD


- ◆ MOS capacitor
- ◆ Potential maximum at Si – SiO<sub>2</sub> interface
  - CTE < 1 due to trapping at interface



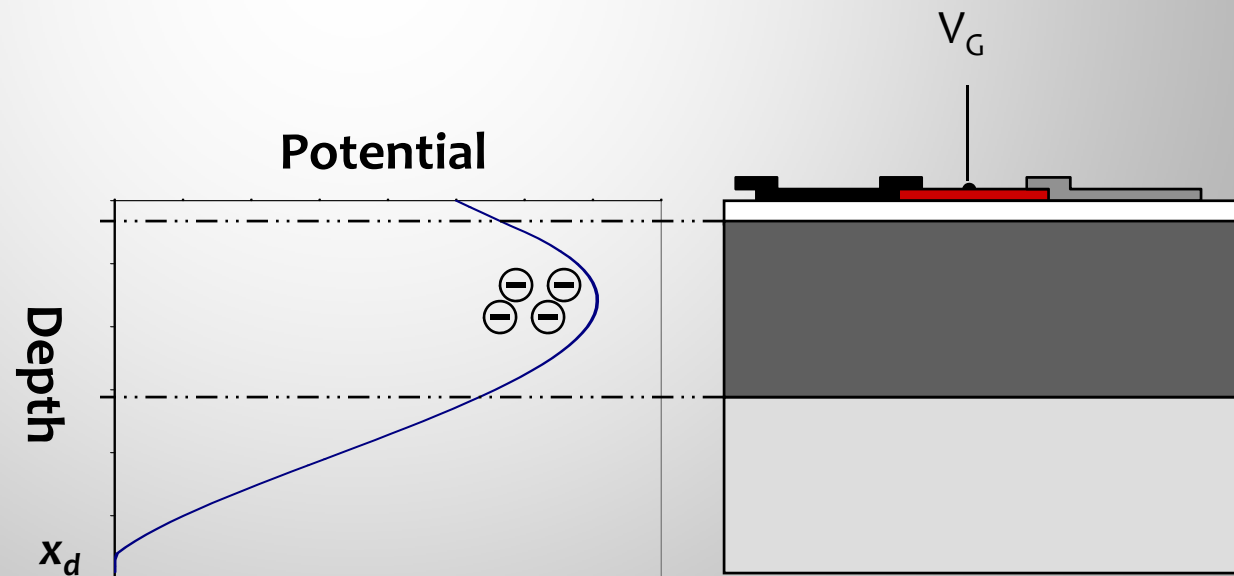- ◆ Potential maximum not at Si – SiO<sub>2</sub> interface
  - ◆ CTE typically > 99.9999%




# Frontside/Backside Illumination

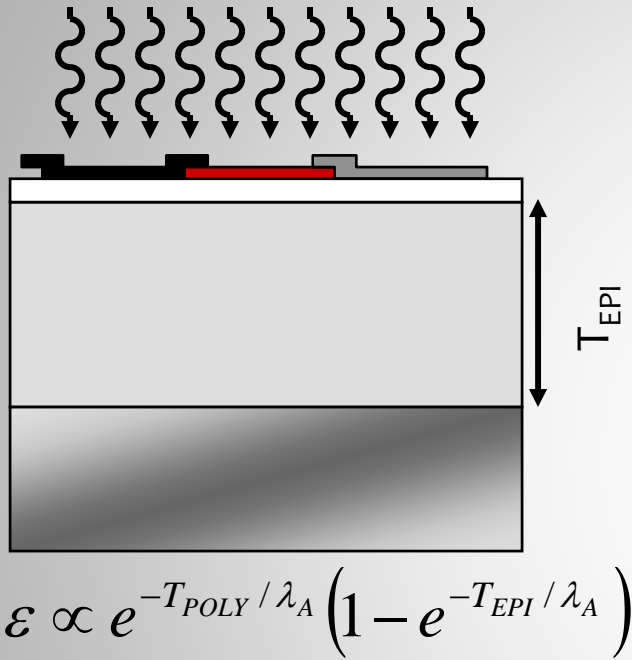


Fill factor < 1
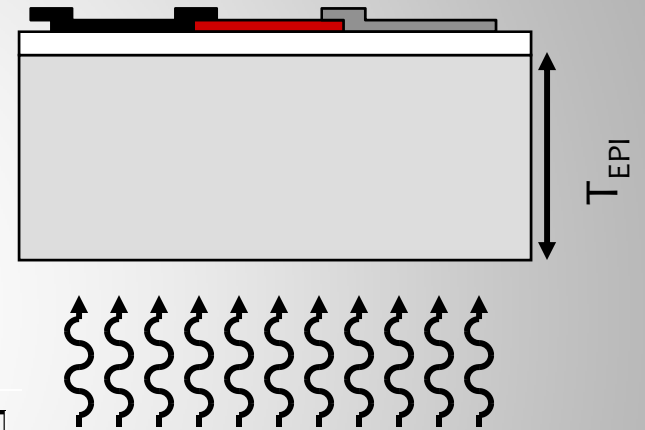
$$\varepsilon \propto (1 - e^{-T_{EPI}/\lambda_A})$$




Fill factor = 1

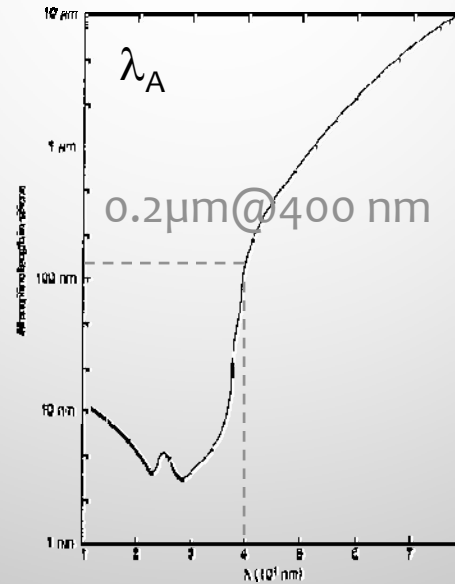




# Integrated Circuit Elements


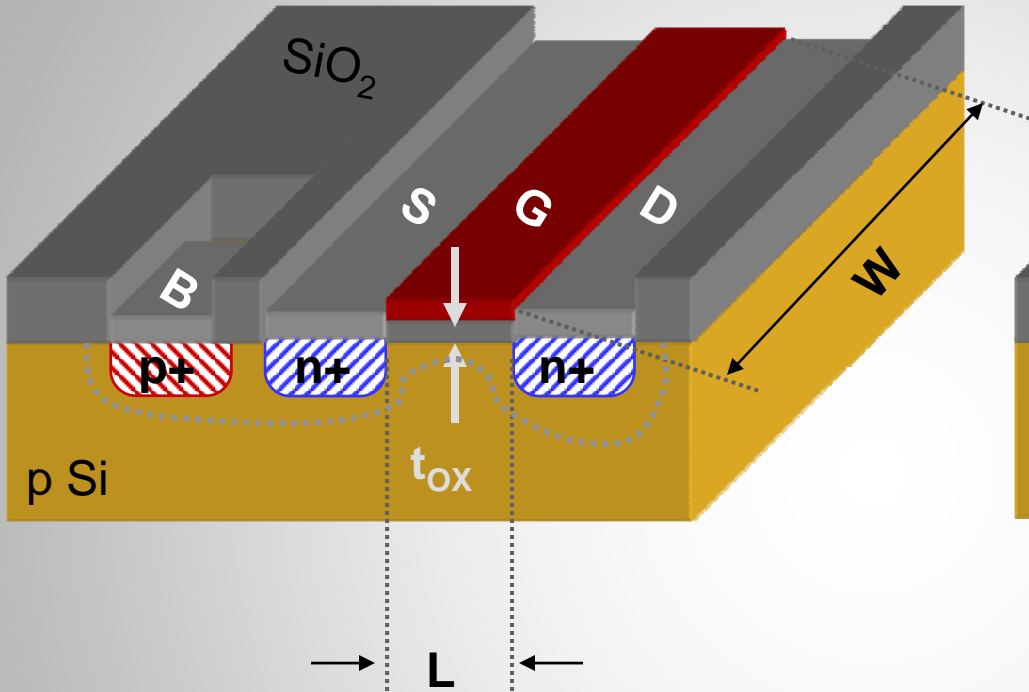


**MOS Transistor**

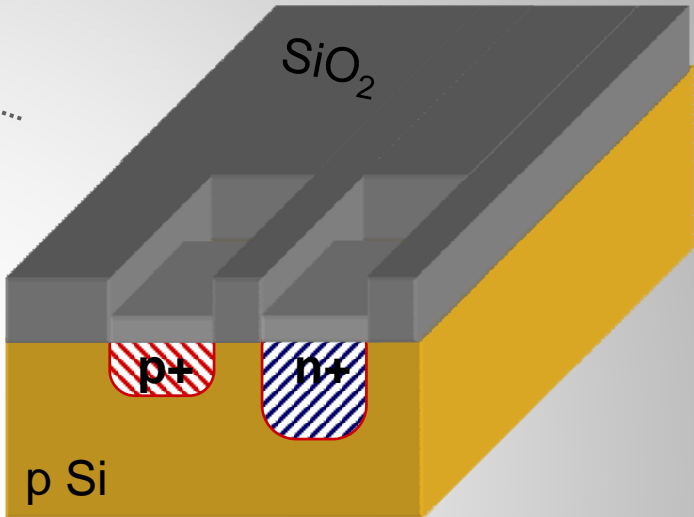



**pn Diode**

# Conventional Semiconductor Processing

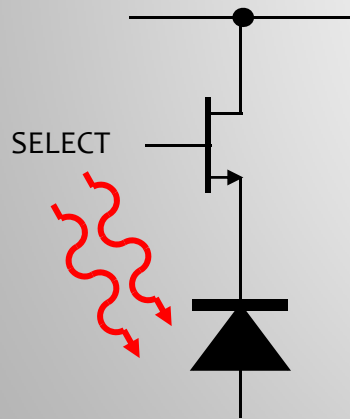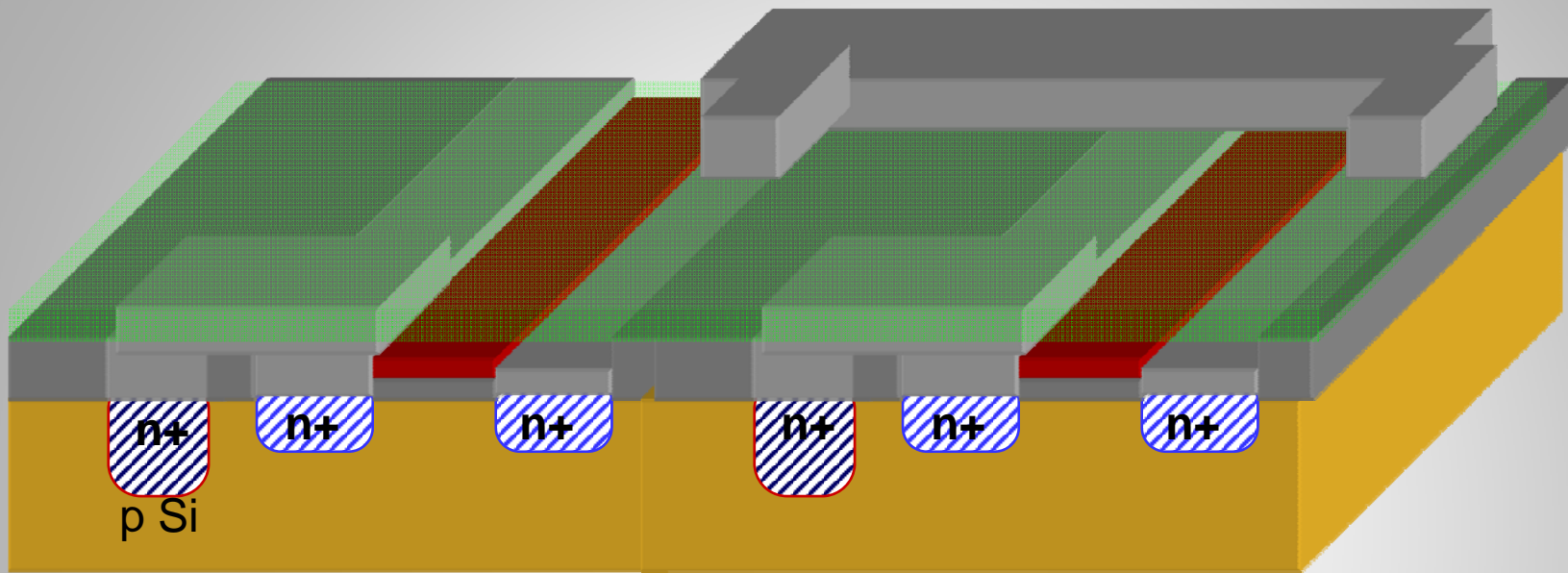

- ◆ Passive Pixel Sensor
- ◆ Proposed 1968
- ◆ No in-pixel reset
- ◆ Poor performance due to capacitive load (nothing buffers the photodiode)

# Active Pixel Sensor

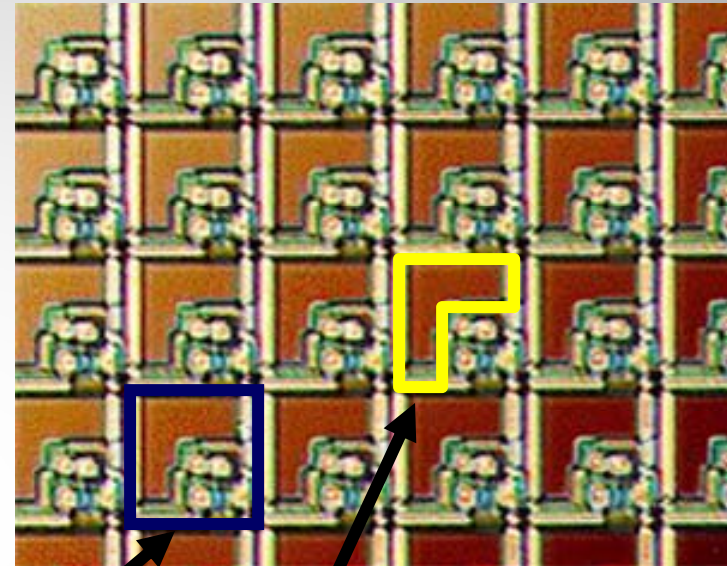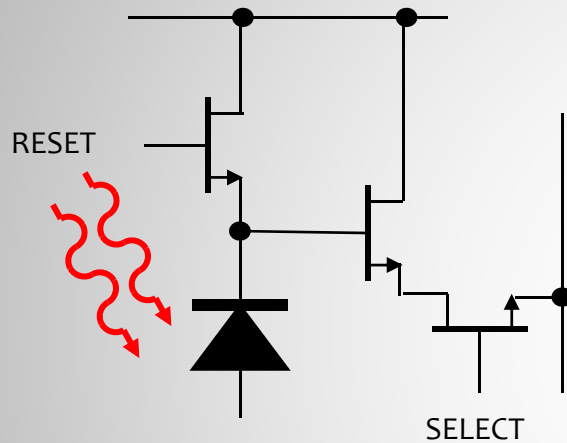



Pixel

Photosensitive region


- ◆ Active Pixel Sensor
- ◆ Also proposed 1968
- ◆ Many ways to make the photodiode

Fill factor =  $\frac{\text{Photosensitive region}}{\text{Pixel}}$

# How It Works

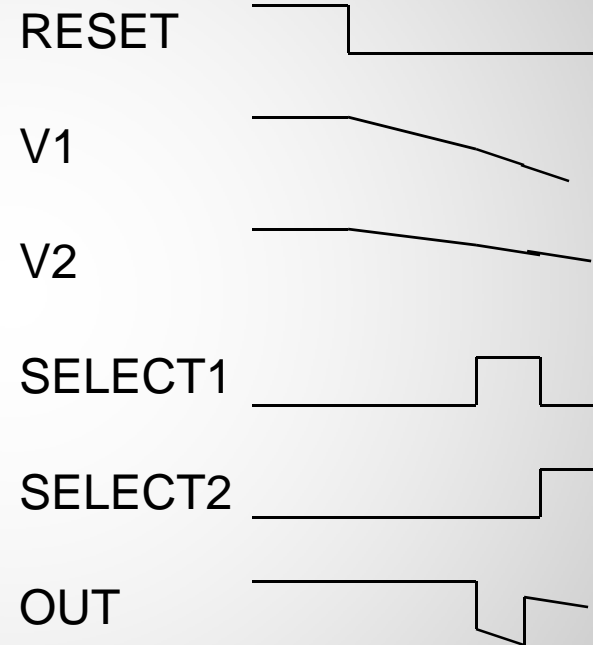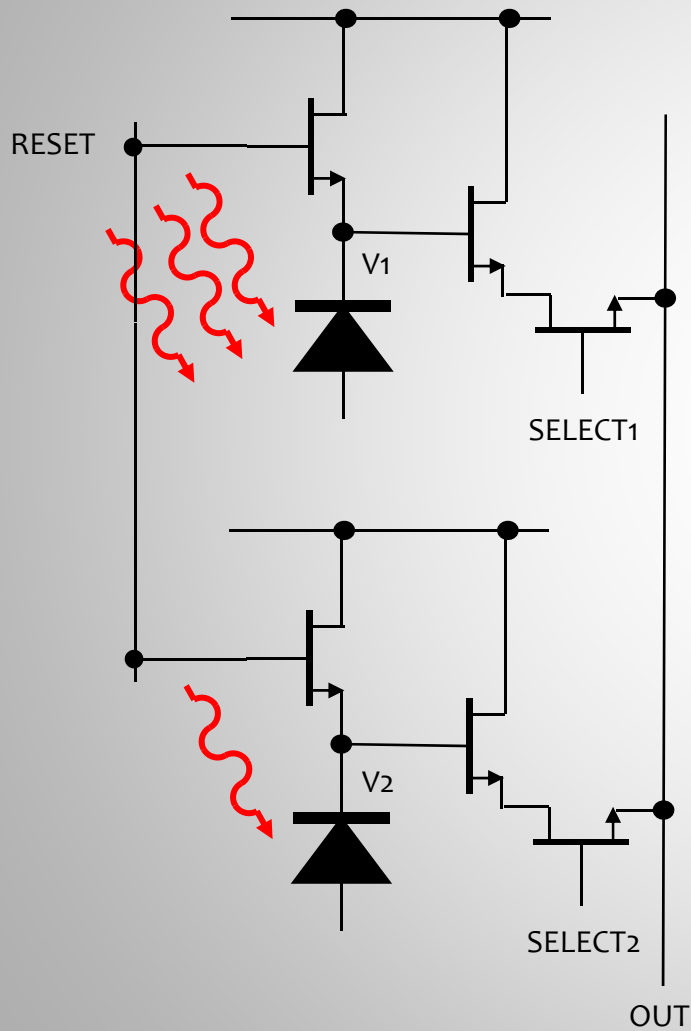


# Add Microlens and Color Filter

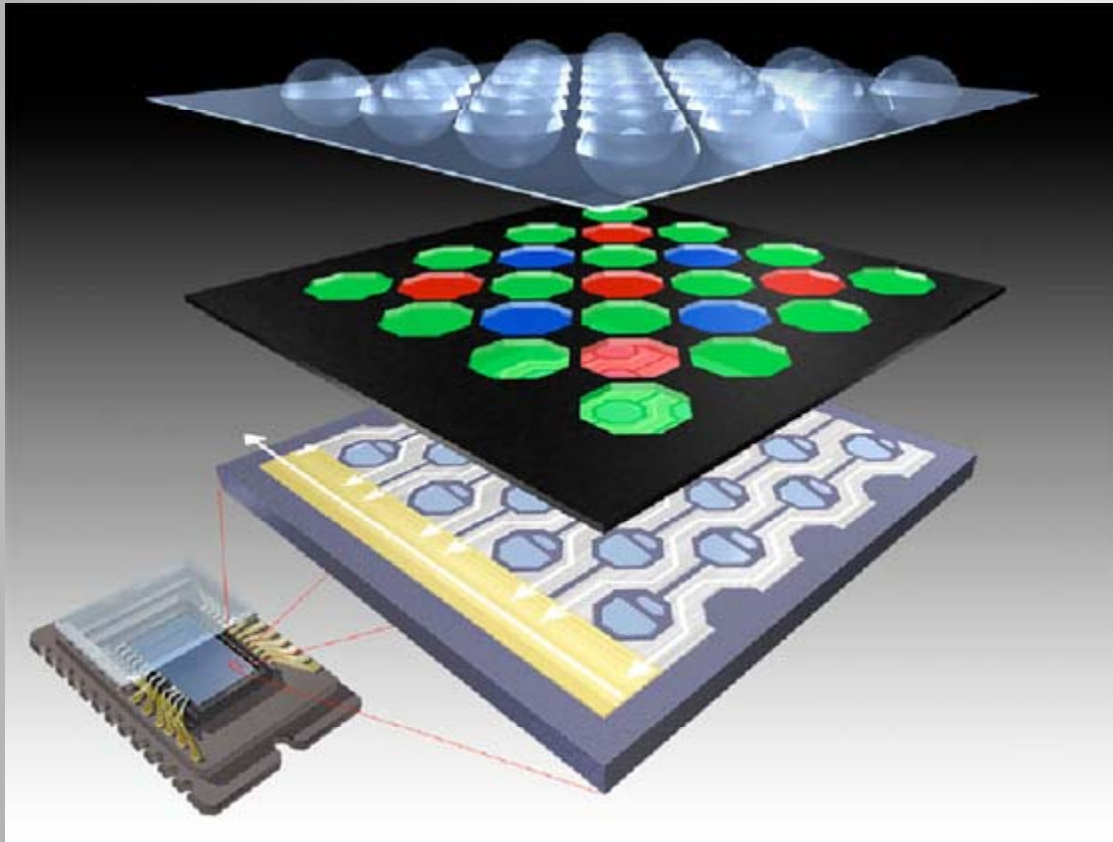

- ◆ Microlens array recovers some of the fill factor
- ◆ Opaque walls between cells reduces cross-talk
- ◆ Color pattern matched to algorithm


# CMOS, CMOS “opto” and CCD processes

CMOS driven by constant field scaling

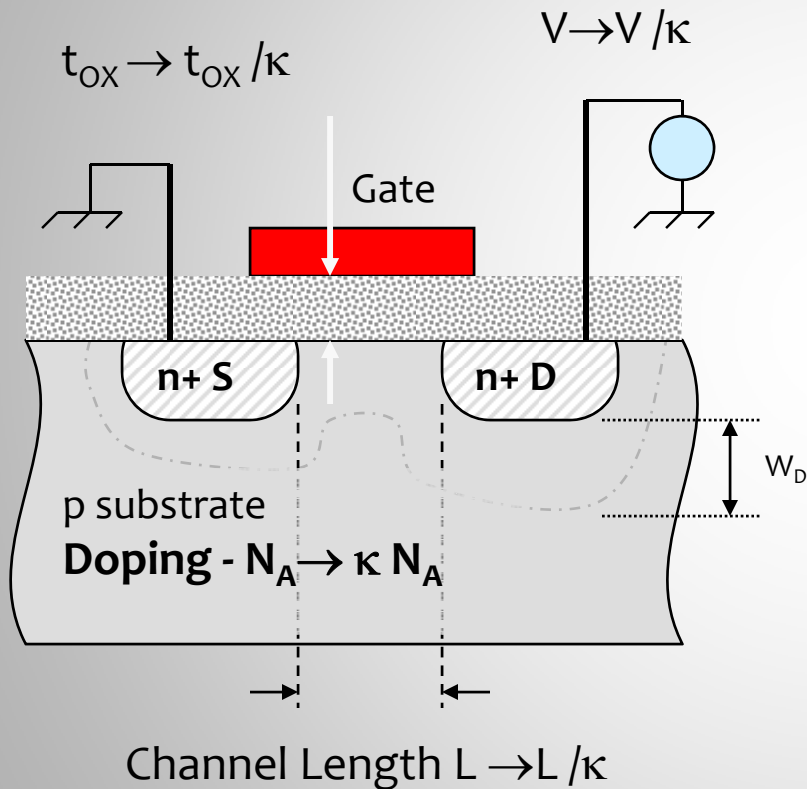

	CCD	CMOS
$t_{ox}$ (Å)	500 - 1000	50
Well depth (μm)	2.5	0.5 deeper for RF
Implant (μm)	~1 channel stop	0.1 S/D implants
V	≥10	<3.3 <2.5 <1.x ...
Poly layers	3 (2)	1 2 for analog
Subst. quality	Low leakage	Don't care Except opto

# Triple Poly CCD Process

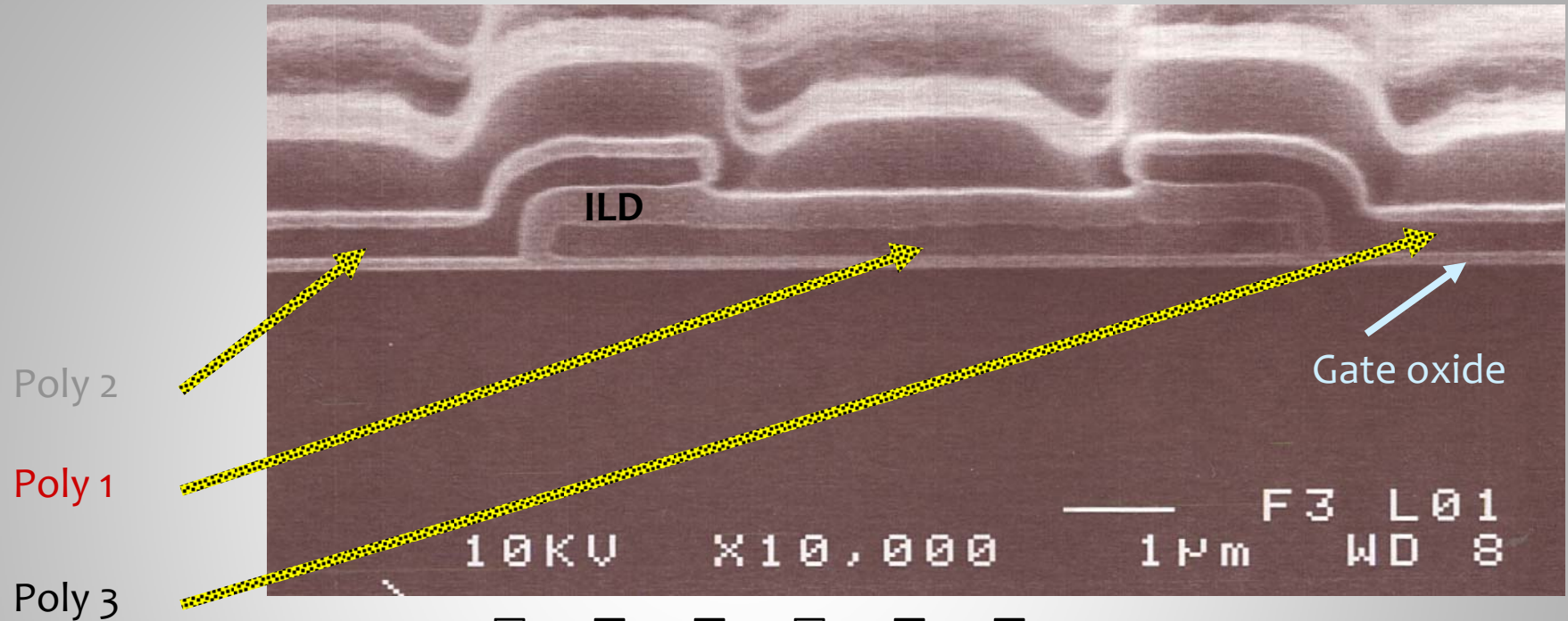

Poly 2

Poly 1


Poly 3

Gate oxide

ILD

10KV X10,000


1µm F3 L01  
WD 8

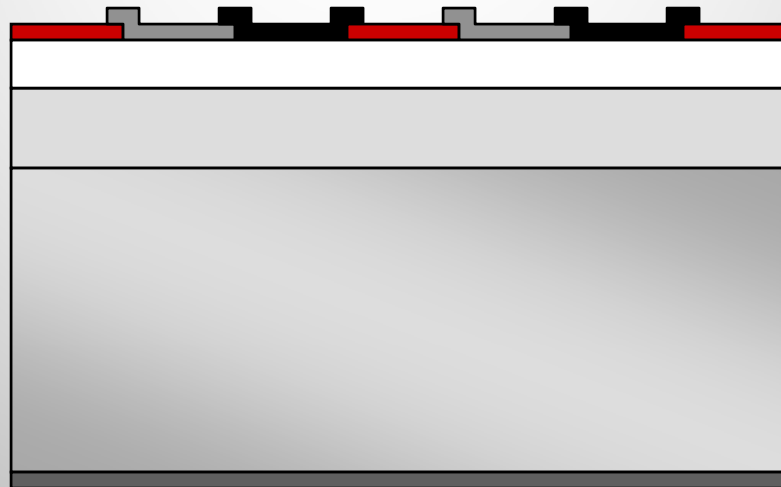

# Very Large Format CCDs (and CMOS imagers)

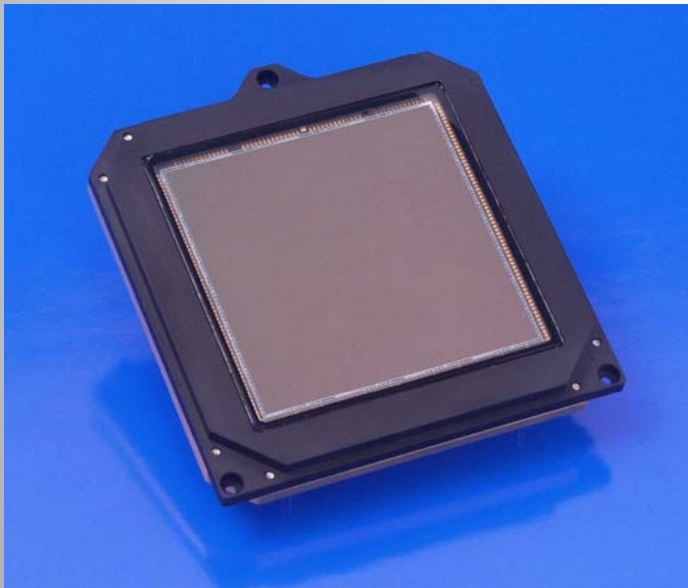
## ◆ Fairchild Wafer Scale Full Frame CCD

- 9216 x 9216 x 8.75  $\mu\text{m}$  pixel
- 80.64 x 80.64  $\text{mm}^2$  size CCD
- Eight 3-stage output amplifiers
- Readout noise < 30e- @ 2/fps


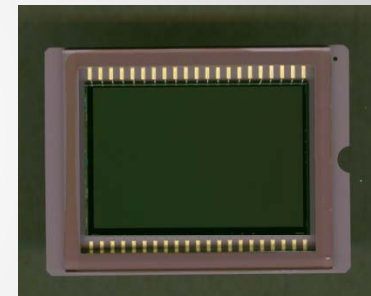
## ◆ Cypress CYIHDS9000

- 3710 x 2434 x 6.4  $\mu\text{m}$  pixel
- 23.3 x 15.5  $\text{mm}^2$  size APS
- 0.13  $\mu\text{m}$  imaging CMOS process



## ◆ Canon 16.7 MPix

- ◆ 36 x 24  $\text{mm}^2$  4992 x 3328

## ◆ Kodak 39 MPix

- ◆ 36 x 48  $\text{mm}^2$




# Electron-Multiplying CCDs

TC2858 PD-80

1004 x 1002 PIXEL IMPACTRON™ CCD IMAGE SENSOR

Sensor Topology diagram

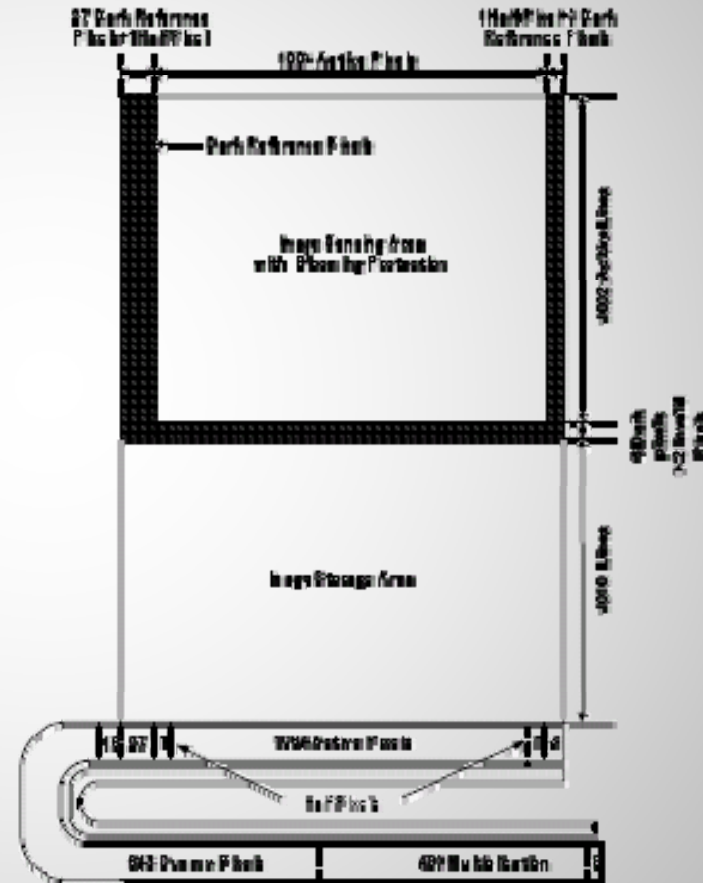


- ◆ Long serial register with avalanche multiplication pixels
- ◆ Gain  $(1+\epsilon)^N$   $\epsilon \sim 1\%$
- ◆ Good for single-photon sensitivity
- ◆ Nonetheless, current devices have limited ( $\leq 12$  bit) dynamic range
- ◆ Excess noise factor, F

# EM CCD

TI-TC285 1004x1002




e2v-97 512x512

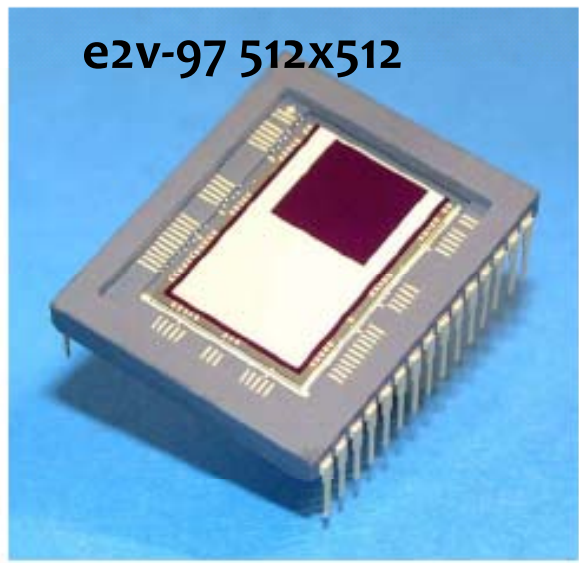

PARAMETER	MIN	TYP**	MAX	UNIT
Charge multiplication gain**	1	200	2000	-
Excess noise factor for typical CCM gain (Note 2)	1	1.4		-
Dynamic range without CCM gain		66		dB
Dynamic range with typical CCM gain (Note 3)		72	~12 bits	dB
Charge conversion gain without CCM gain (Note 4)		14		$\mu\text{V}/e$
$\tau$ Signal-response delay time (Note 5)		16		ns
Output resistance (Note 6)		320		$\Omega$
Amp. Noise-equivalent signal without CCM gain *		20		e
Amp. Noise-equivalent signal with typ. CCM gain *			1.0	e

PARAMETER	UNIT	MIN	TYPICAL	MAX
Output amplifier responsivity, HR amplifier (normal mode) (see note 1)	$\mu\text{V}/e^-$	-	5.3	-
Output amplifier responsivity, LS amplifier (normal mode) (see note 1)	$\mu\text{V}/e^-$	-	1.1	-
Multiplication register gain, LS amplifier (high gain mode) (see notes 2, 3 and 4)		1	-	1000
Peak signal - 2-phase IMO	$e^-/\text{pixel}$	90k	130k	-
Charge handling capacity of multiplication register (see note 5)	$e^-/\text{pixel}$	-	800k	-
Readout noise at 50 kHz with CDS, HR amplifier (normal mode) (see note 6)	$e^- \text{ rms}$	-	2.2	-
Readout noise at 1 MHz with CDS, HR amplifier (normal mode) (see note 6)	$e^- \text{ rms}$	-	5.4	-
Amplifier reset noise (without CDS), HR amplifier (normal mode) (see note 6)	$e^- \text{ rms}$	-	50	-
Readout noise at 50 kHz with CDS, LS amplifier (normal mode) (see note 6)	$e^- \text{ rms}$	-	6	-
Readout noise at 1 MHz with CDS, LS amplifier (normal mode) (see note 6)	$e^- \text{ rms}$	-	14	-
Amplifier reset noise (without CDS), LS amplifier (normal mode) (see note 6)	$e^- \text{ rms}$	-	120	-
Readout noise at 1 MHz (high gain mode) (see note 6)	$e^- \text{ rms}$	-	<1	-
Maximum frequency (settling to 1%), HR amplifier (see notes 6 and 7)	MHz	-	-	3
Maximum frequency (settling to 5%), HR amplifier (see notes 6 and 7)	MHz	-	-	4.5
Maximum frequency (settling to 1%), LS amplifier (see notes 6 and 7)	MHz	-	-	9
Maximum frequency (settling to 5%), LS amplifier (see notes 6 and 7)	MHz	-	-	15
Maximum parallel transfer frequency (see note 1)	MHz	-	1.6	-
Dark signal at 293 K (see note 8)	$e^-/\text{pixel}/s$	-	400	800
Dark signal non-uniformity (DSNU) at 293 K (see note 9)	$e^-/\text{pixel}/s$	-	60	-
Excess noise factor (see note 10)		-	$\sqrt{2}$	-



# Particle physics example

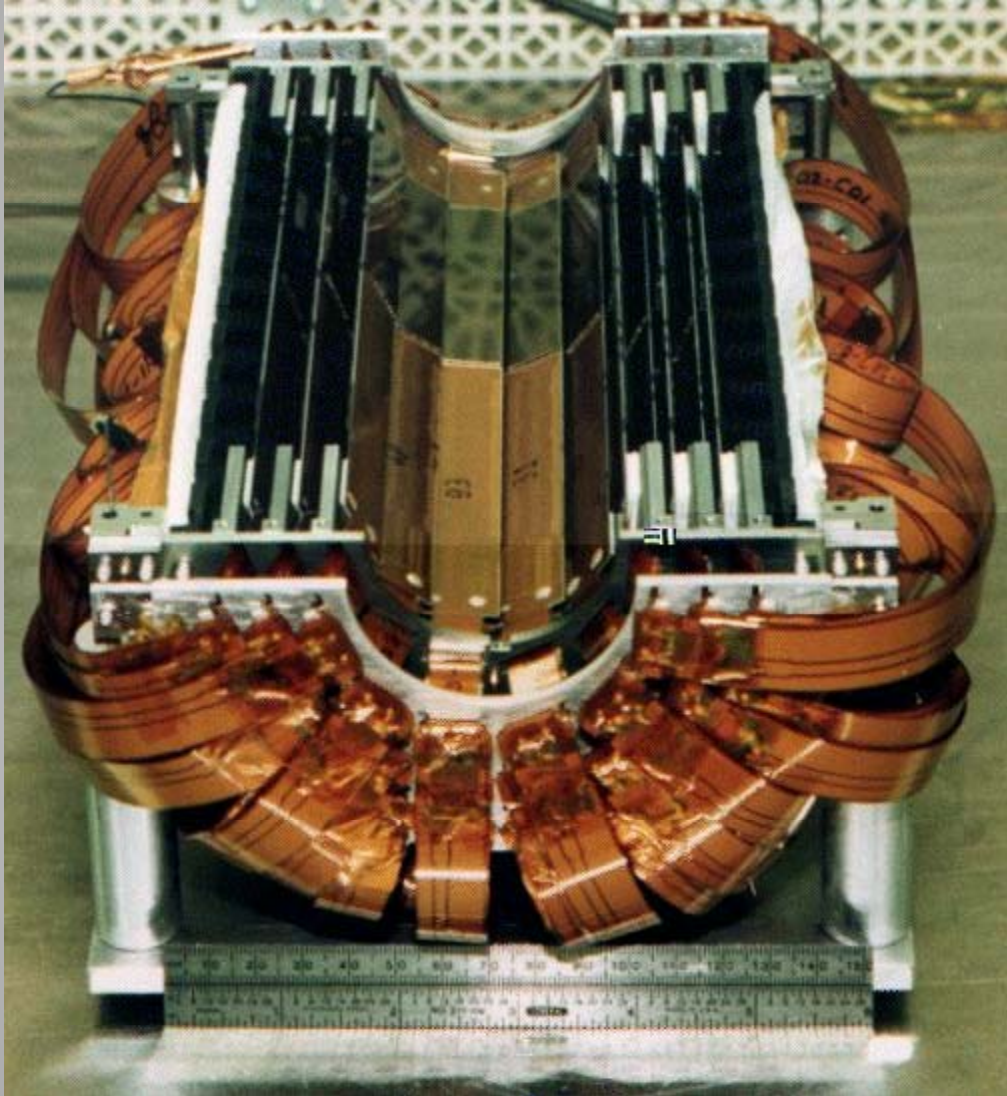


- ◆ 1996 - SLD Vertex Detector
- ◆  $3 \times 10^8$  pixels
- ◆  $96 \times 3.2$  MPix  $\times 20 \mu\text{m}$  CCD

# Reading out CCDs

CCD Output Stage

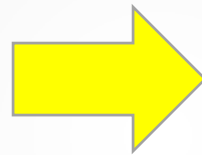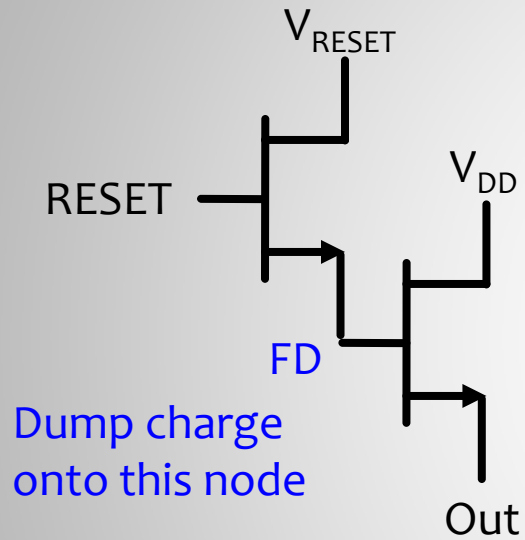


CCD Output Stage

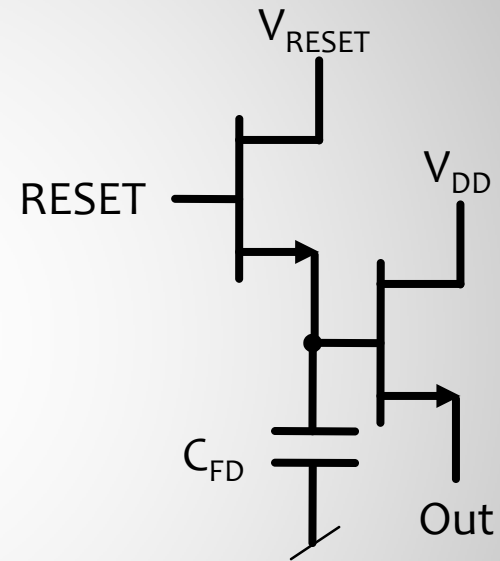


**Each transistor is a noise source**

$C_{FD}$  “converts” the charge into a voltage:  $V = Q / C_{FD}$

# kT/C noise

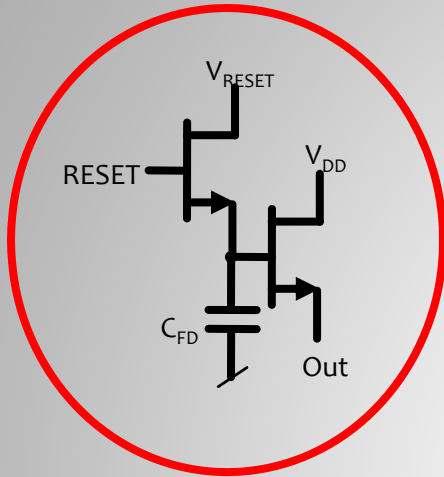

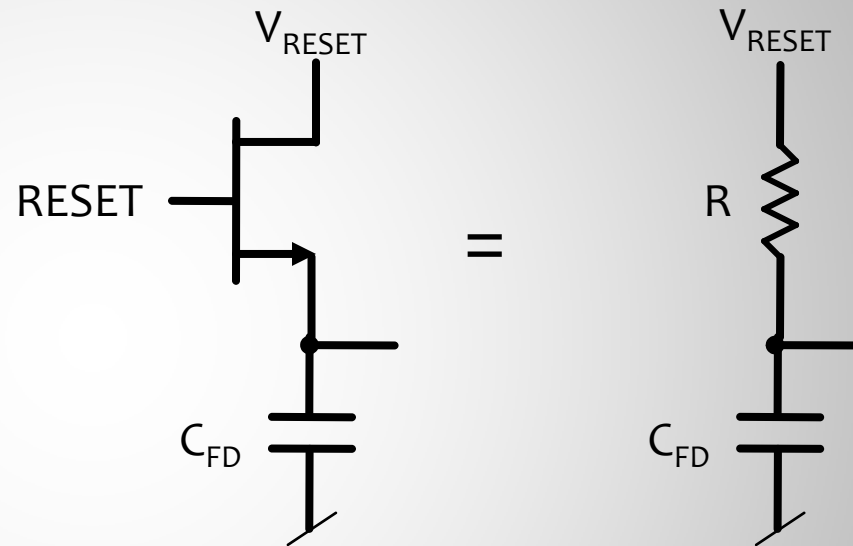Reset transistor is a switch whose resistance is a function of the gate voltage




$$\text{Voltage noise} = \sqrt{4kTR \times BW}$$

$$\text{Bandwidth} \propto 1/\tau, \tau = RC \rightarrow \text{Voltage noise} = \sqrt{4kT/C}$$

$$V = Q/C_{FD} \rightarrow \text{e.n.c.} = \sqrt{4kTC}$$

# Correlated double sampling

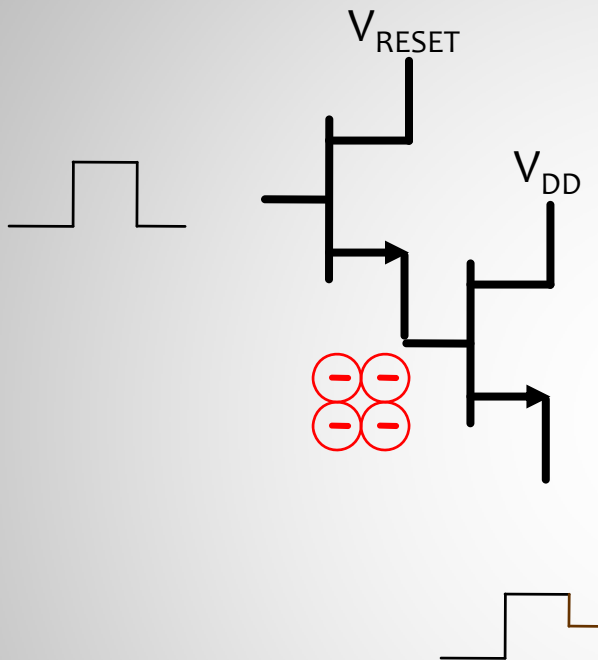


1. Turn on RESET
2. Measure
3. Turn off RESET
4. Dump charge on to FD
5. Measure

Signal = difference

Cancels  $kT/C$  noise


Helps to remove low frequency ( $1/f$ ) noise

# A practical example

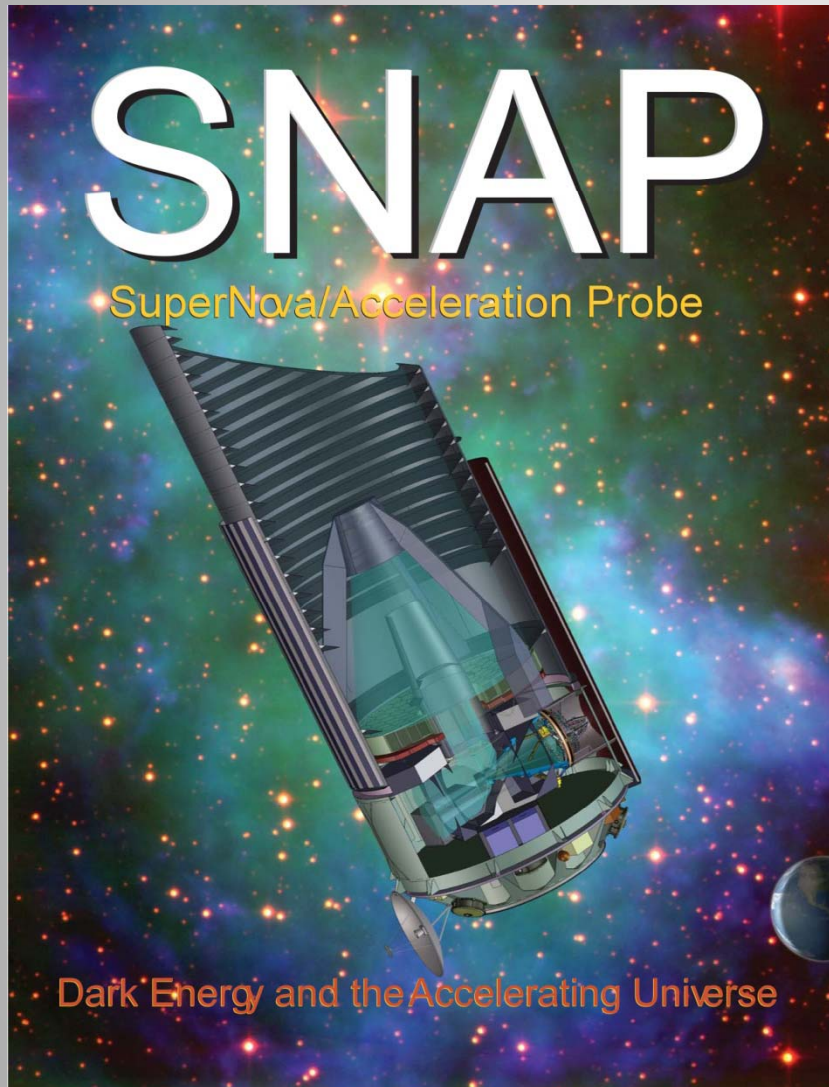



- ◆ Satellite experiment to look at supernovae
  - Uses CCDs in the focal plane
- ◆ SNAP requirements
  - 16 bit dynamic range at 100 kHz
  - 4 channels per chip
  - low power
  - space qualified

# Floating point readout

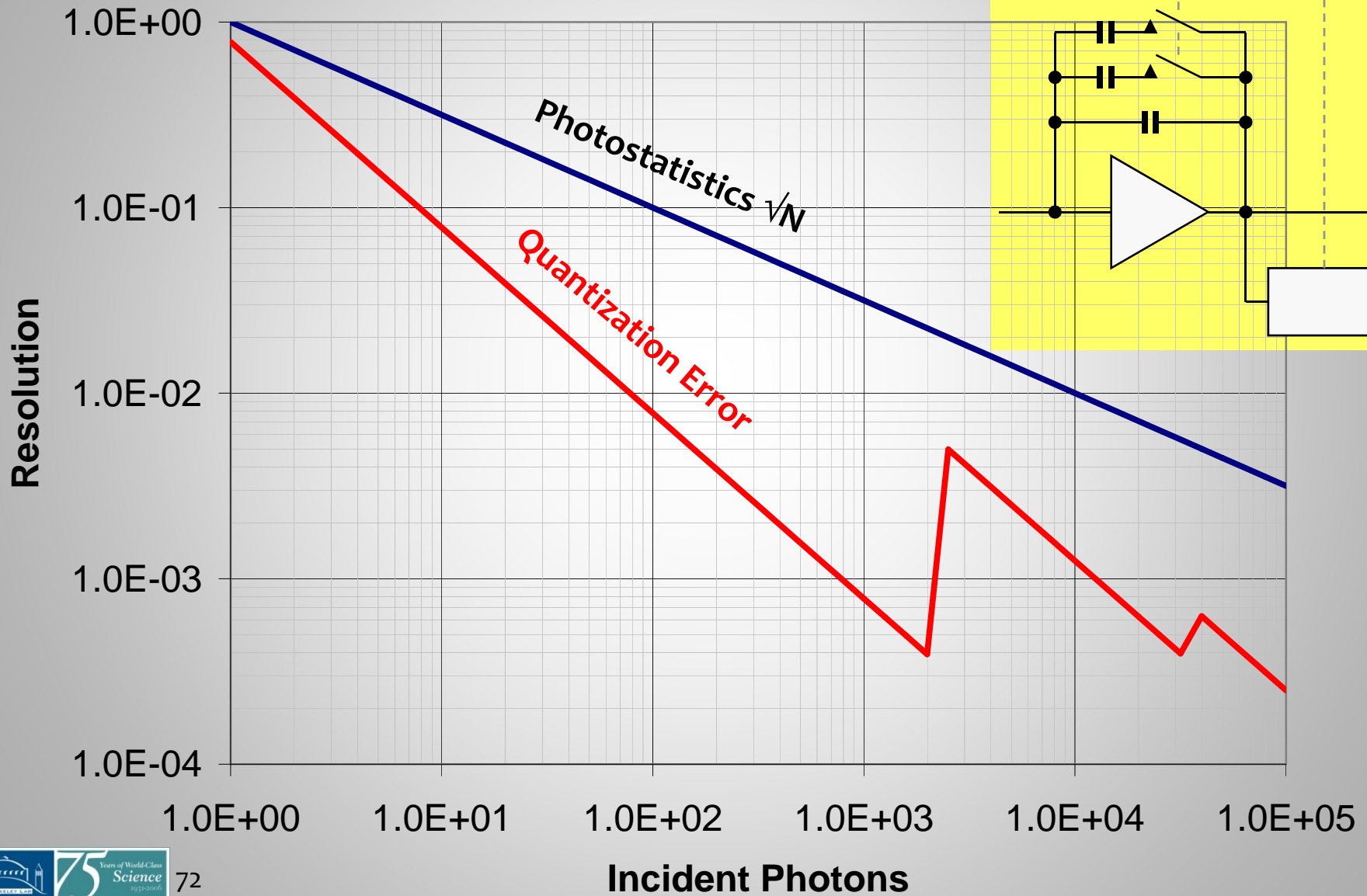




# Digitize cycle

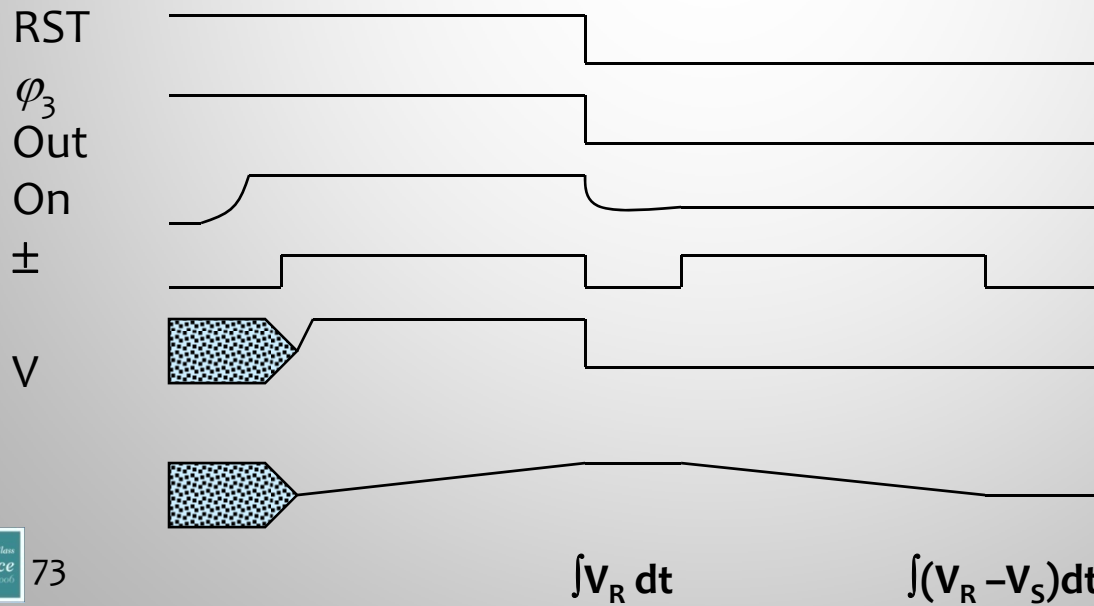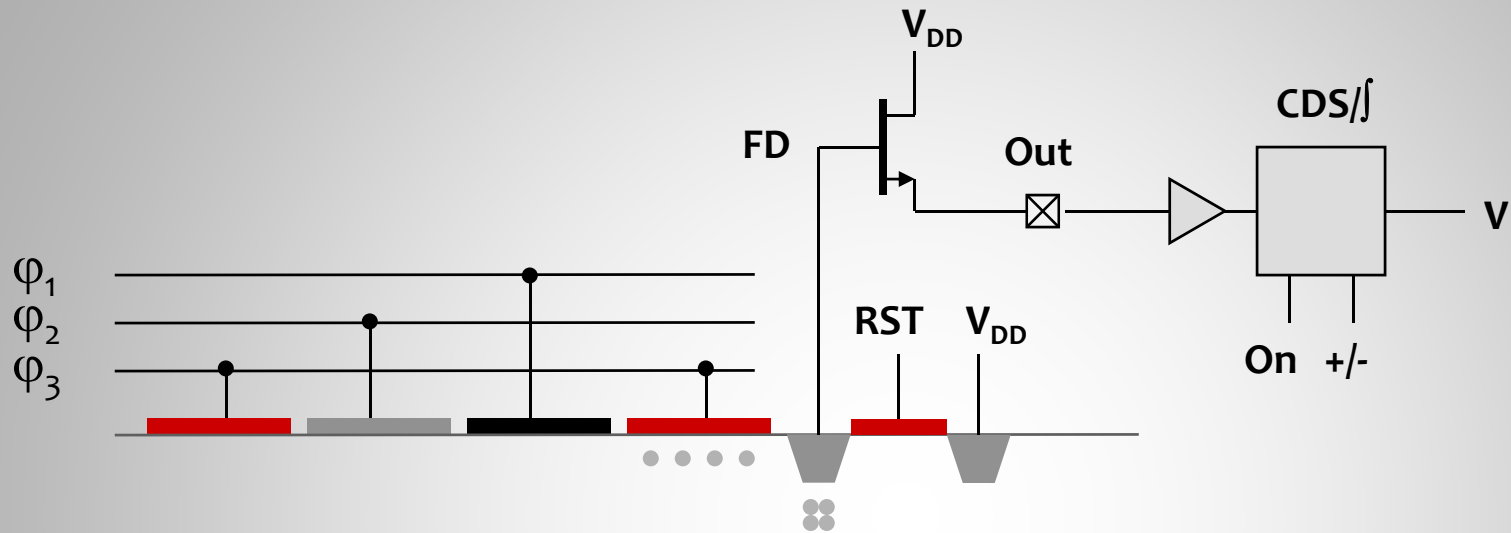


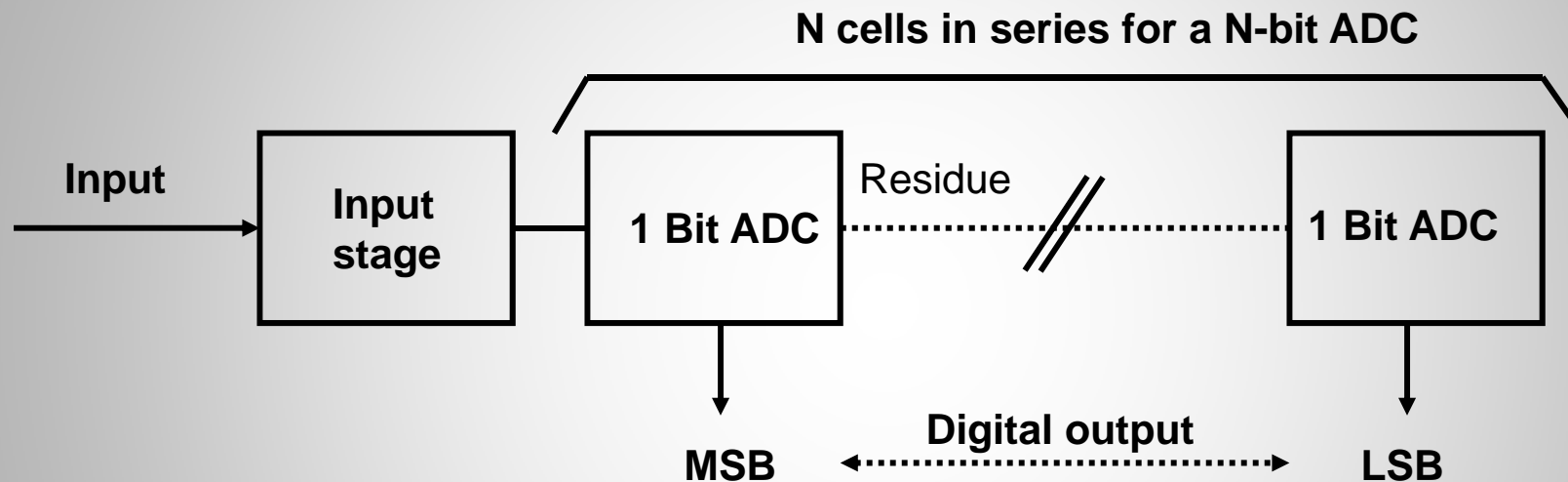
# Pipelined ADC

*Helmuth mentioned the pipelined ADC – here's a practical implementation*



- ◆ **Sub ranging architecture: Each stage determines one bit.**
- ◆ **The first stage residue is digitized by a (N-1) bit ADC and so on...**
- ◆ **Digitization rate = ADC clock frequency**
- ◆ **Latency = Digitization rate x number of bits / 2**

# 1-Bit Cell

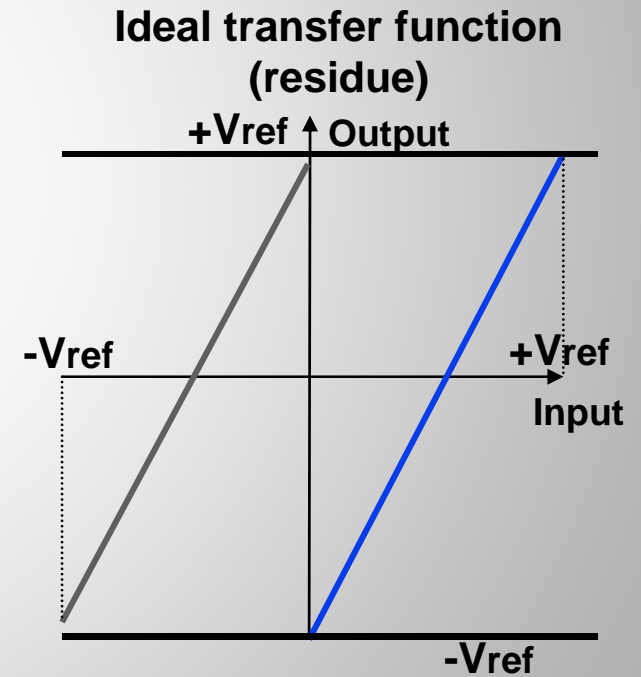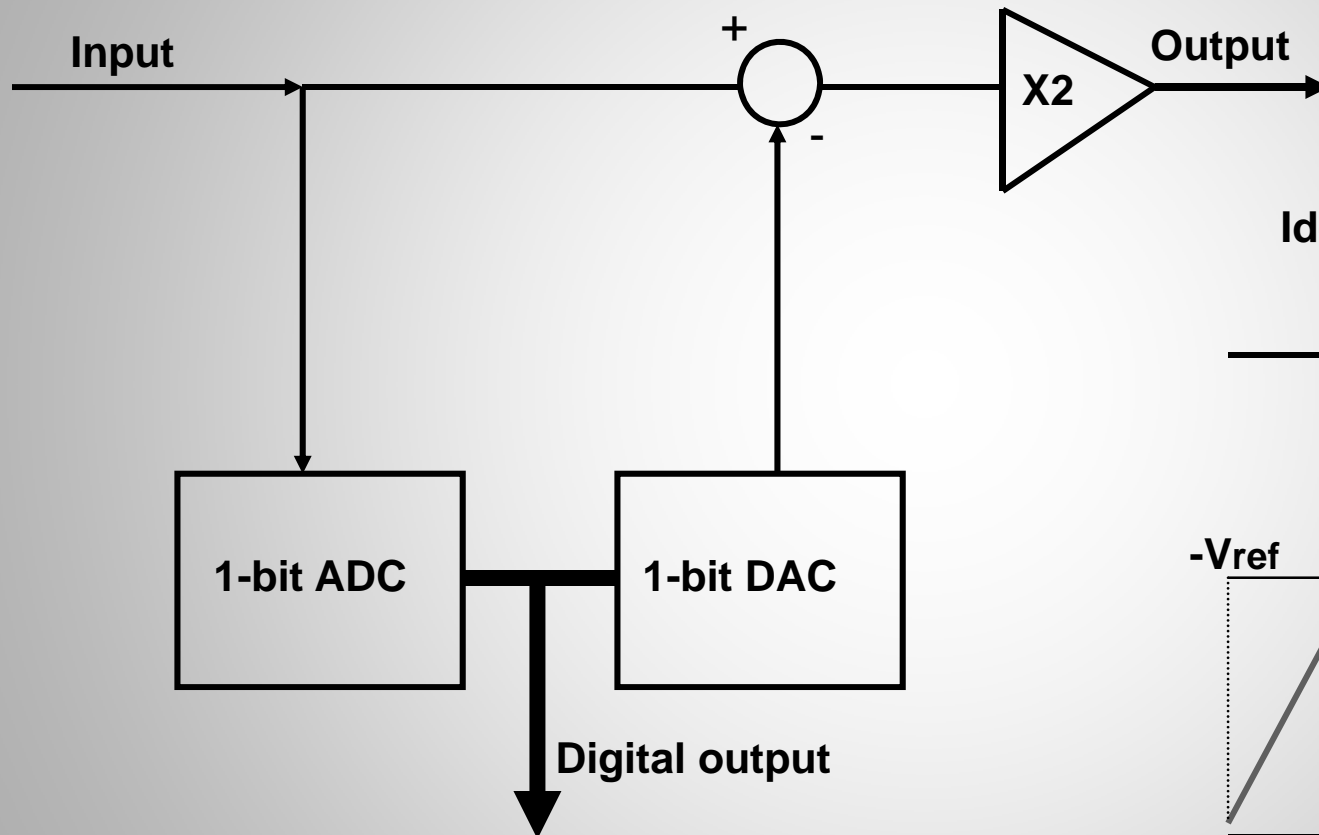

D0

0



1

→

$$V_{out} = 2xV_{in} + V_{ref}$$

$$V_{out} = 2xV_{in} - V_{ref}$$

# Limitation of the 1-Bit Cell

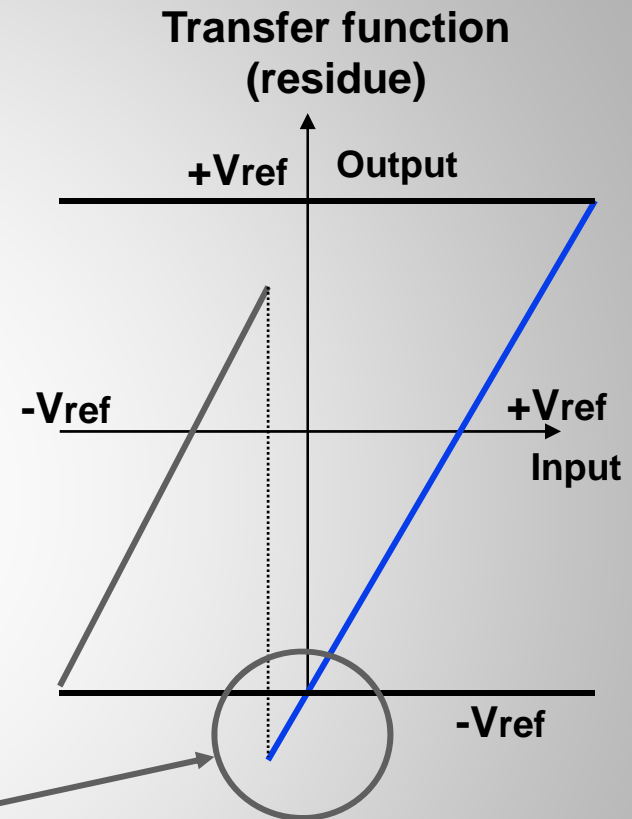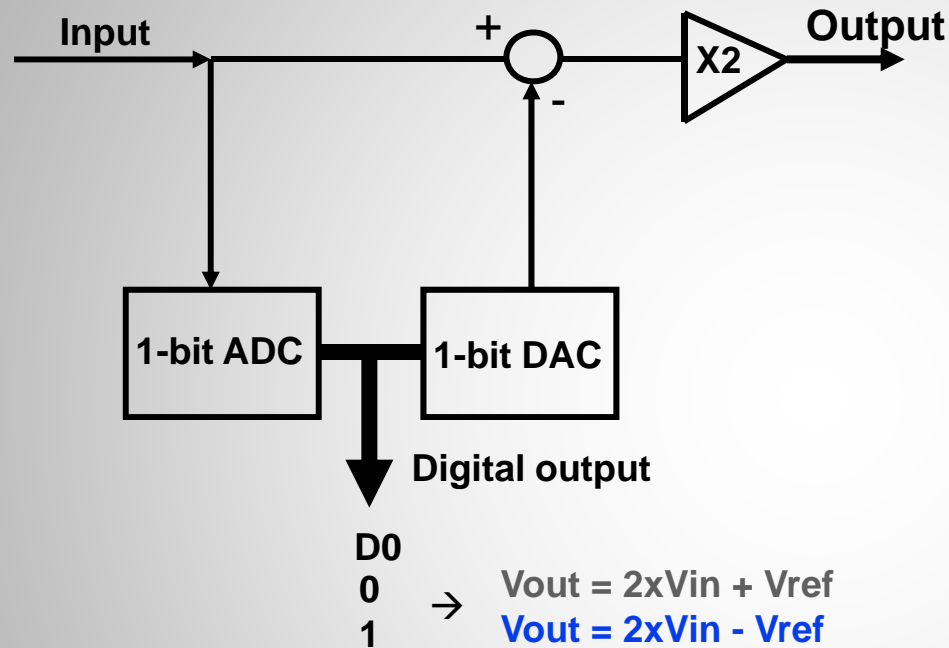


Missing codes due to comparator offset for example

Loss of information when the larger residues saturate the next stage. It could come from charge injection, capacitance mismatch or comparator offset.

Errors can be corrected by digital correction if the conversion range of the next stage is increased to handle the larger residues.

# 1.5-Bit Cell

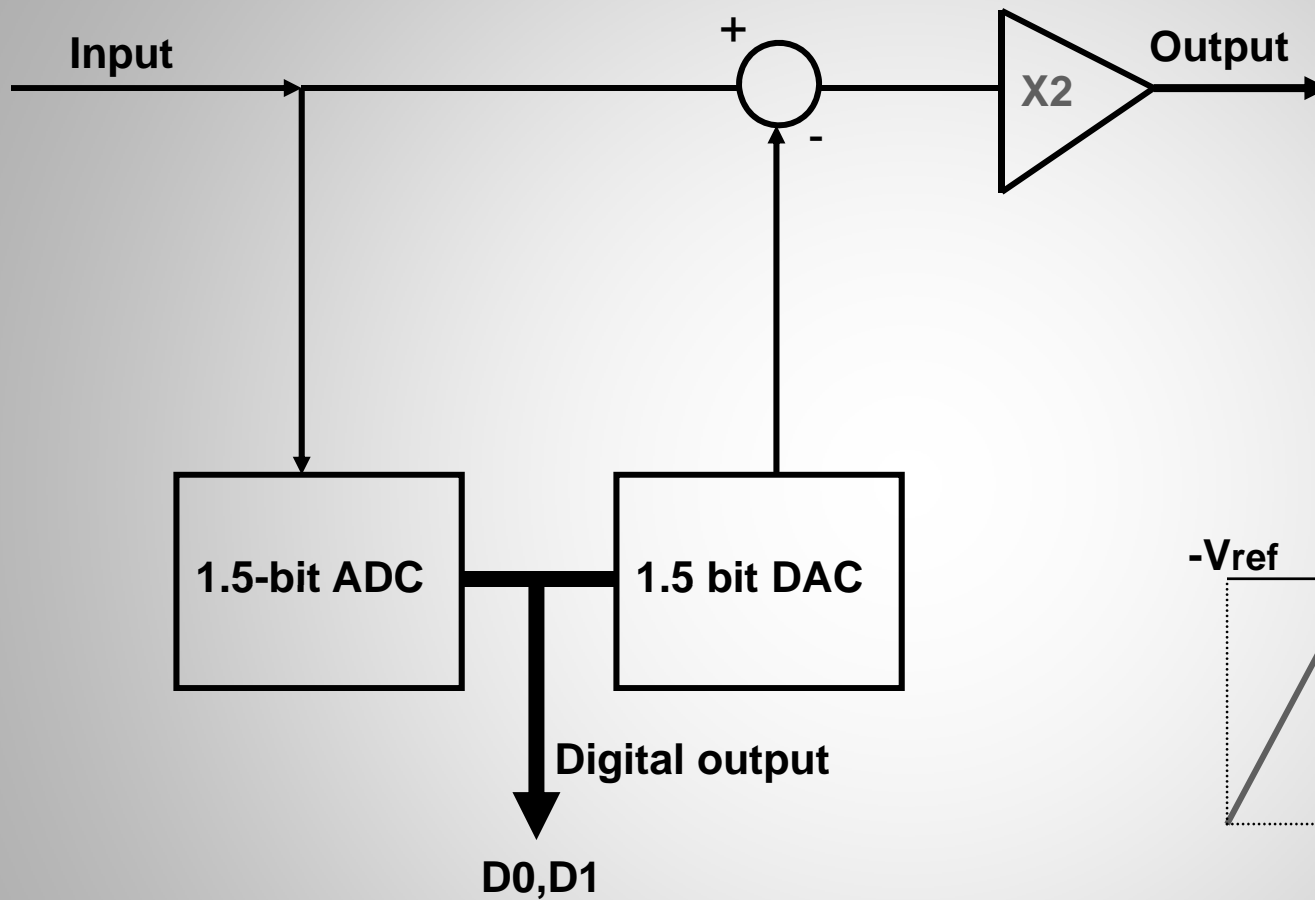


Digital output  
D0, D1

00  
01  
11


→
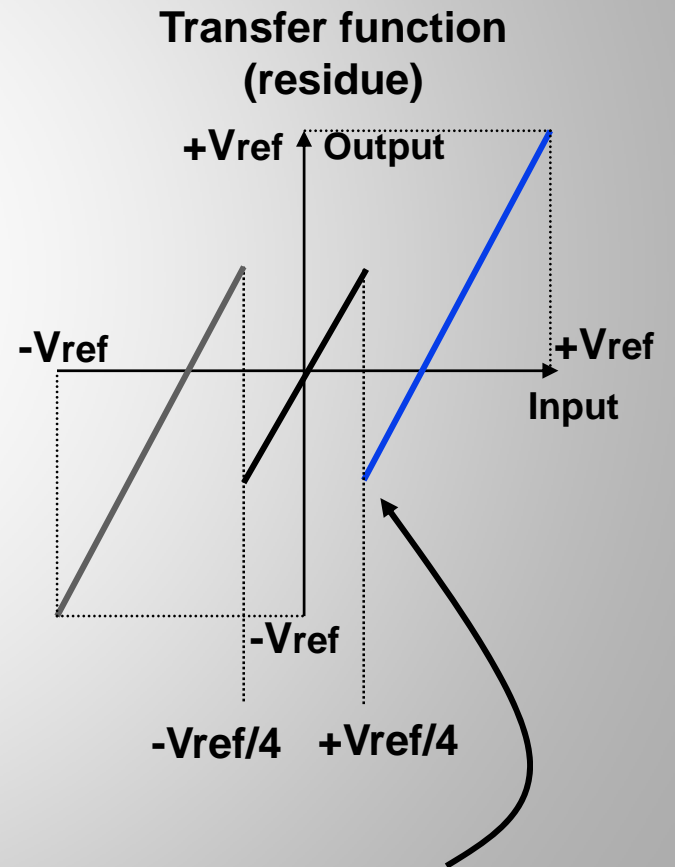
$$\begin{aligned} V_{out} &= 2xV_{in} + V_{ref} \\ V_{out} &= 2xV_{in} + 0 \\ V_{out} &= 2xV_{in} - V_{ref} \end{aligned}$$




No saturation if  $\pm V_{ref}/4$  is moving

# 1.5-Bit Cell Implementation

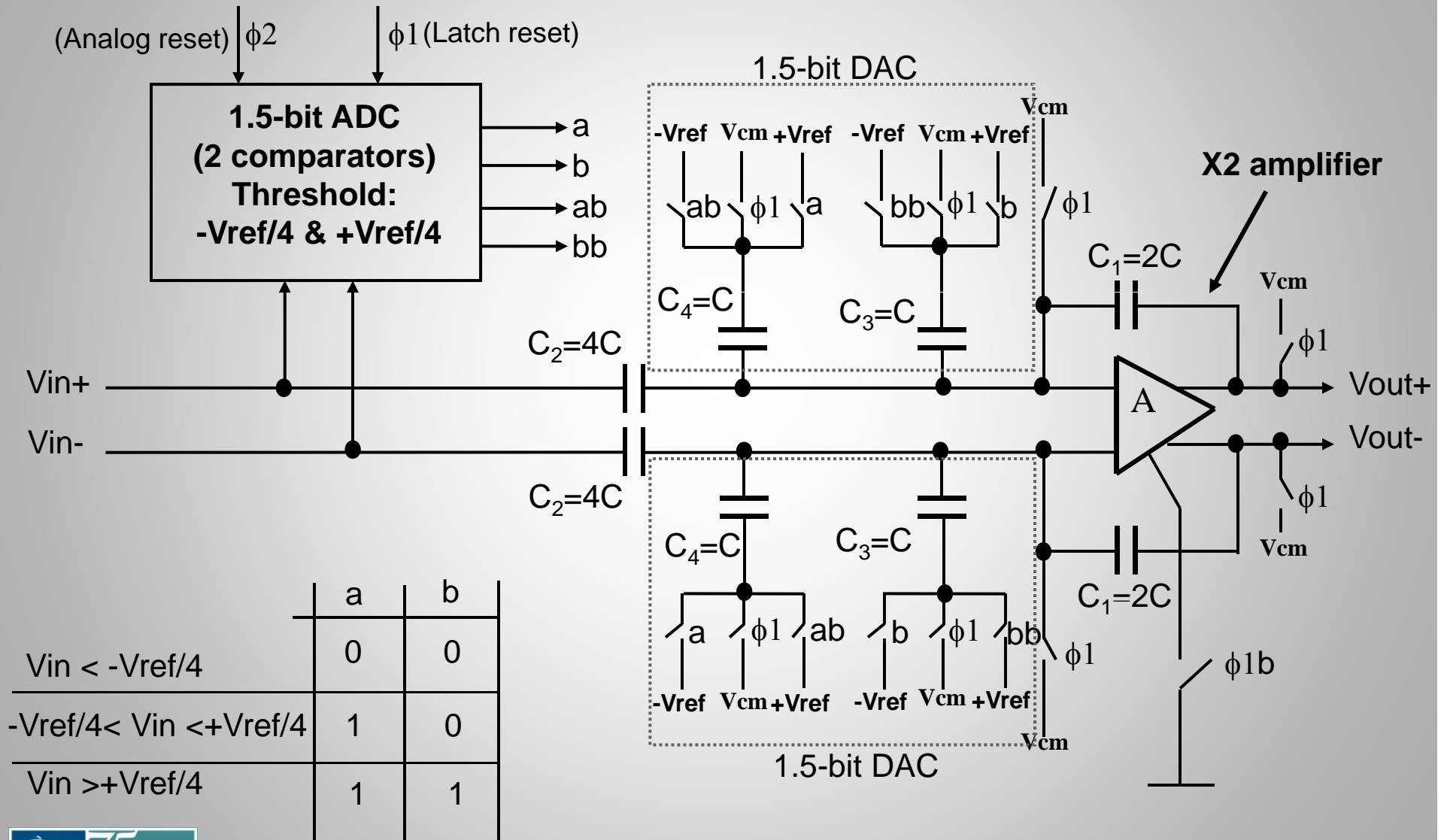


# Sampling Phase

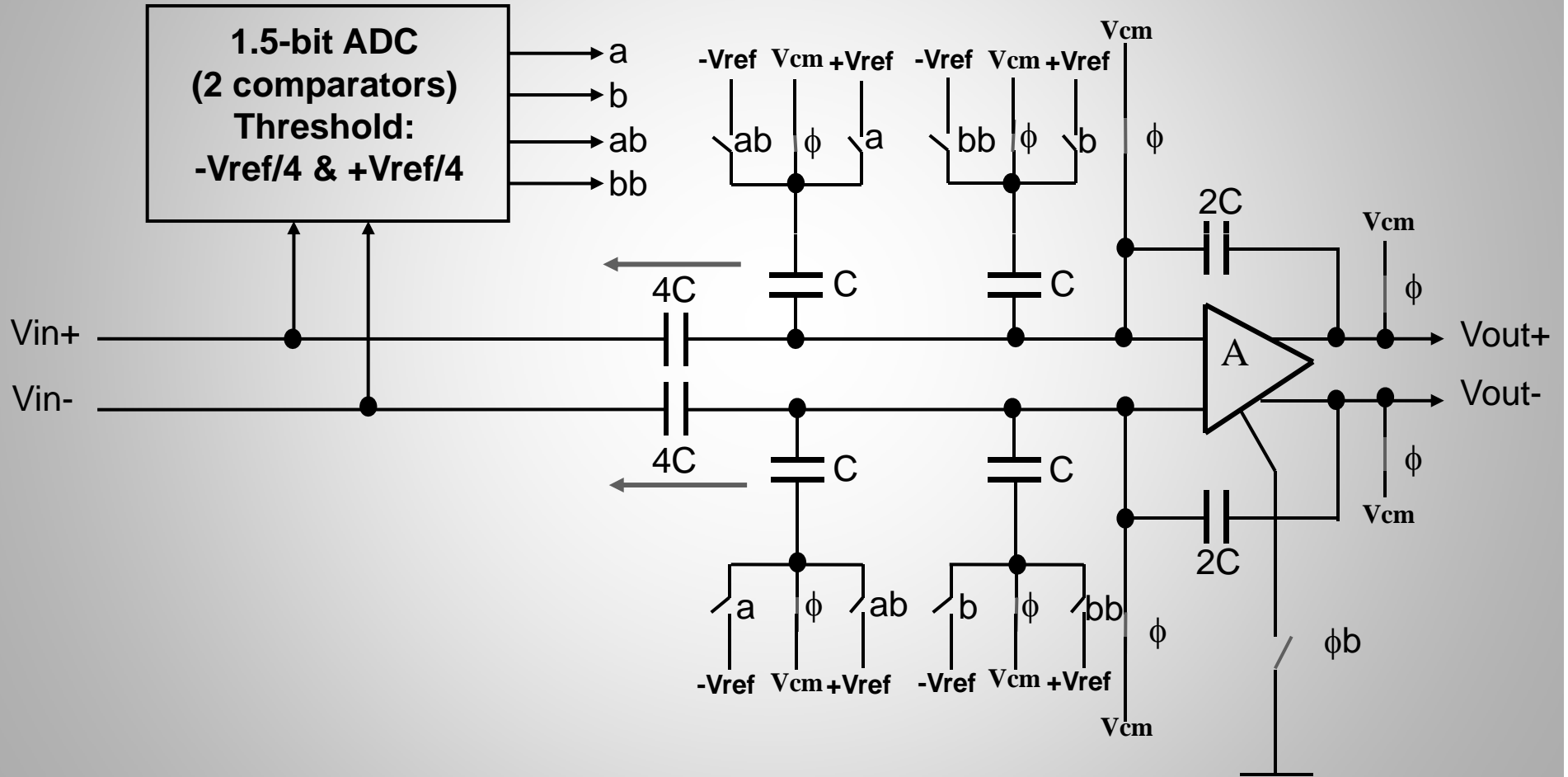

**Input signal sampled on  $4C$**

# Amplification Phase

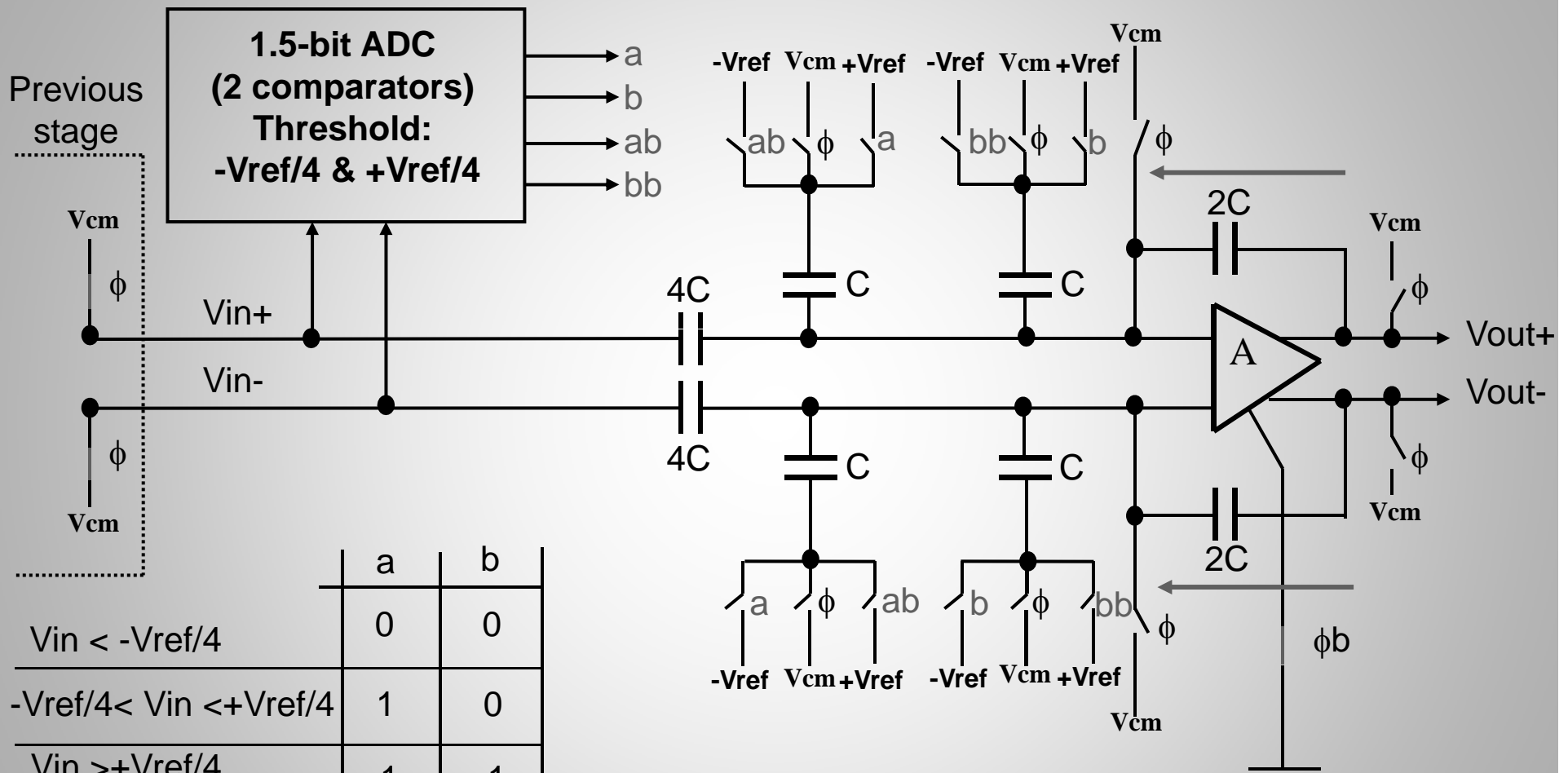


	a	b
$V_{in} < -V_{ref}/4$	0	0
$-V_{ref}/4 < V_{in} < +V_{ref}/4$	1	0
$V_{in} > +V_{ref}/4$	1	1

**$V_{out} = 2xV_{in} \pm V_{ref}/2 \pm V_{ref}/2$**   
 (DC gain infinite)




# Optical active pixel

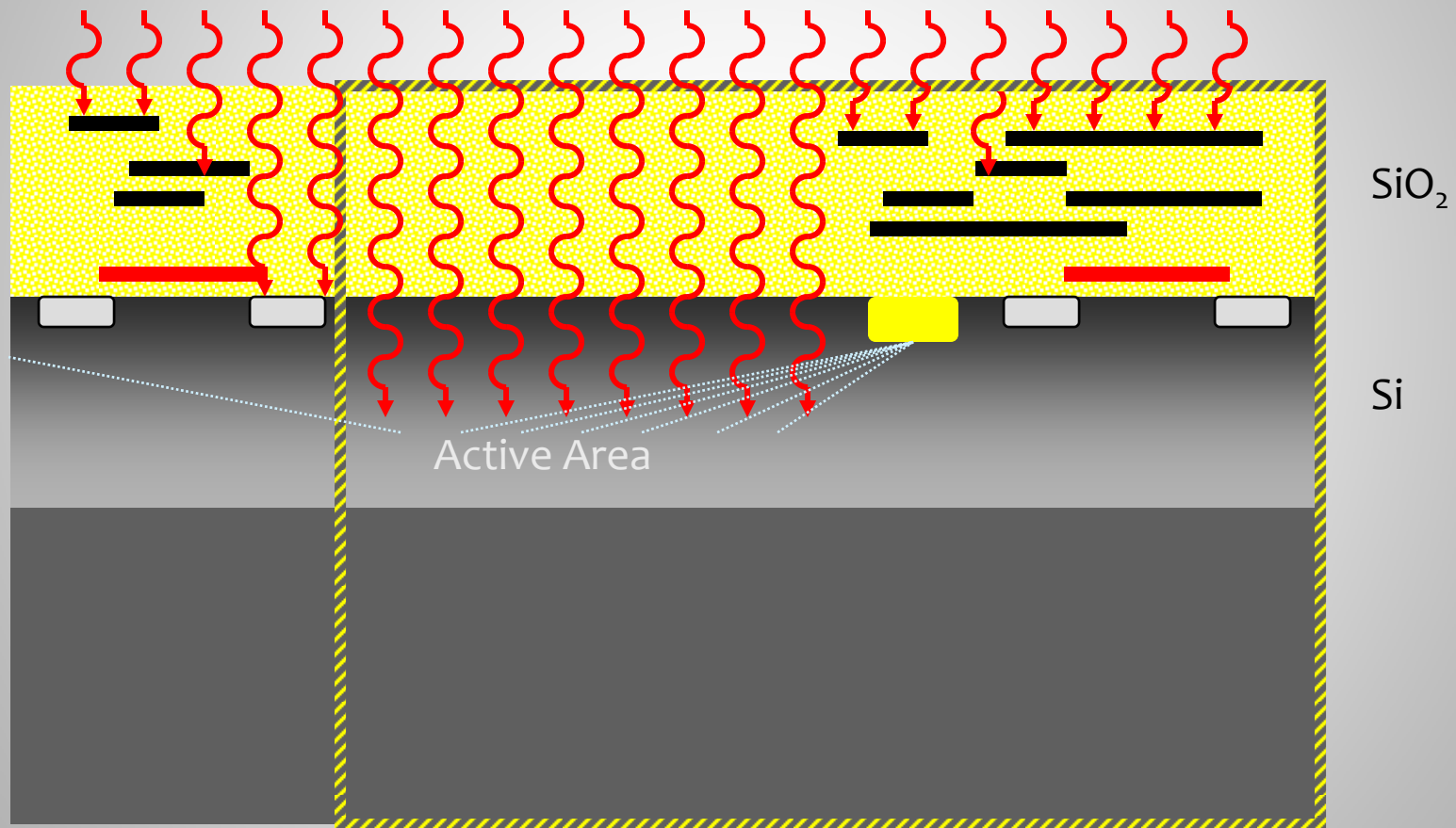

$$\text{Fill Factor} = \text{Active} / \text{Total area}$$


# Charged particle active pixel

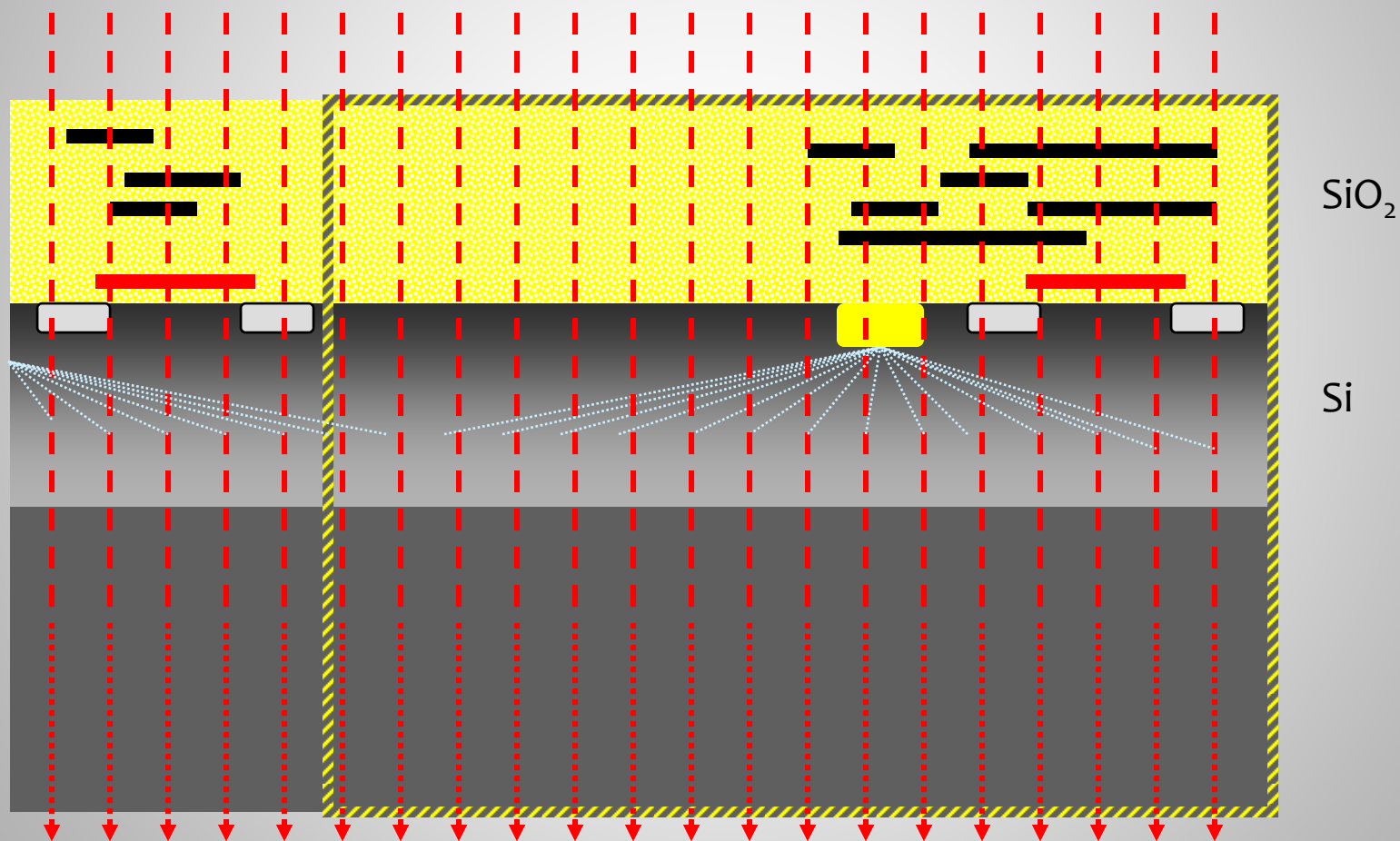


Fill Factor = 100%
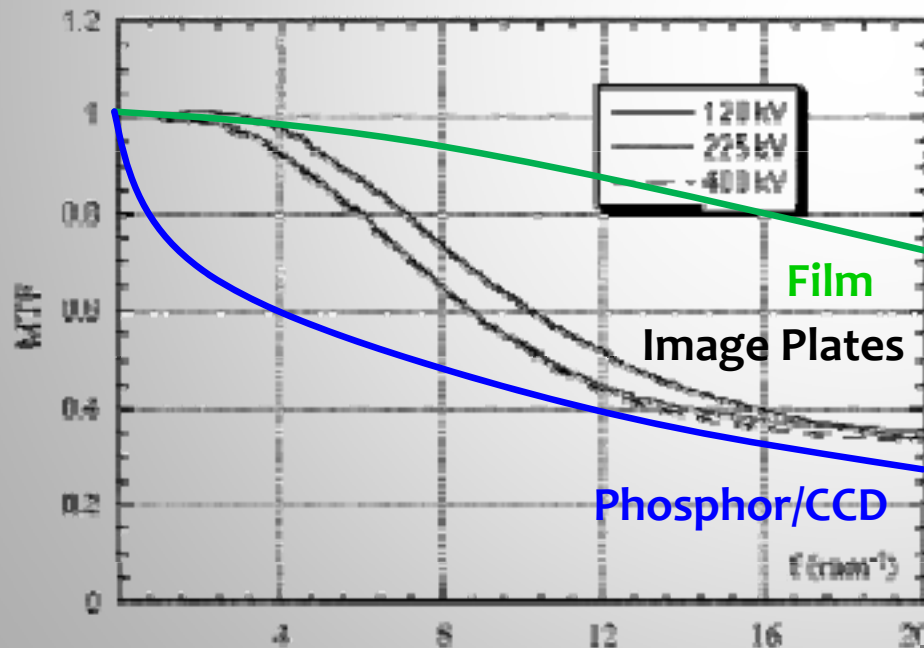
# Example: Transmission Electron Microscopy

- ◆ Film:  $\Delta t$ (exposure-to-image) – minutes-hours-days  
Good MTF (very small grains), less aliasing (random grain sizer)  
Non-linear, low (local) dynamic range
- ◆ Image plates:  $\Delta t$ (exposure-to-image) – minutes-hours-days  
Moderate MTF  
Wide dynamic range
- ◆ Phosphor/CCD:  $\Delta t$ (exposure-to-image) – seconds  
Poorer MTF  
Wide dynamic range



## “Digital” EM (and xray) detector



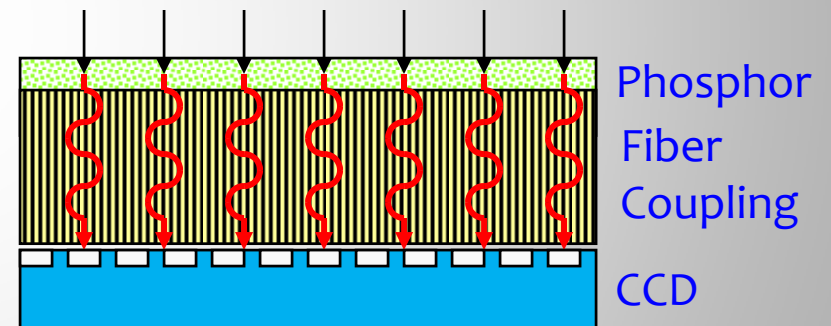


Yet, film has better MTF

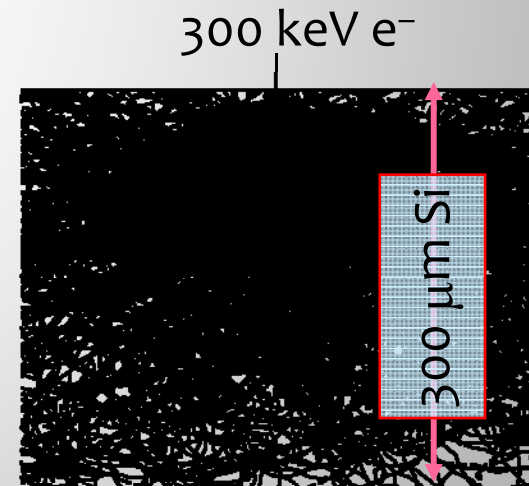
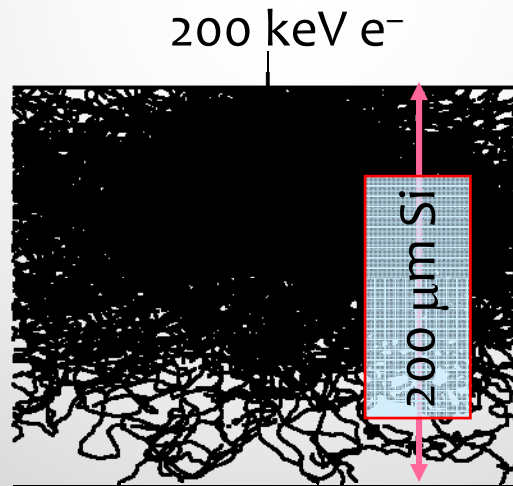
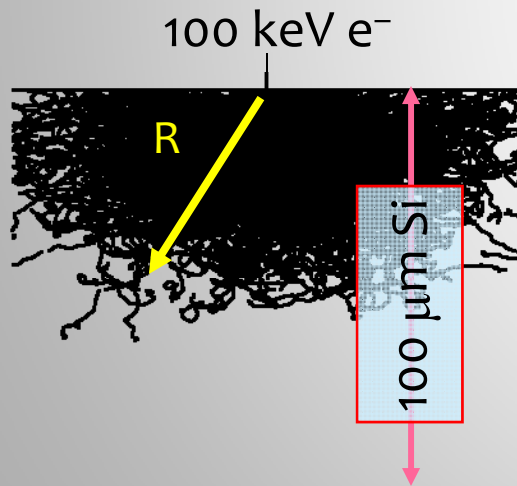
# EM Detector Challenge

“At energies of interest for electron microscopy, electrons scatter a lot!”

$$\left. \begin{array}{l} R [\mu\text{m}] \sim E [\text{keV}] \\ dE/dx \sim 1/E \end{array} \right\} \text{Astronomical Precision}$$




# Charged particle active pixel

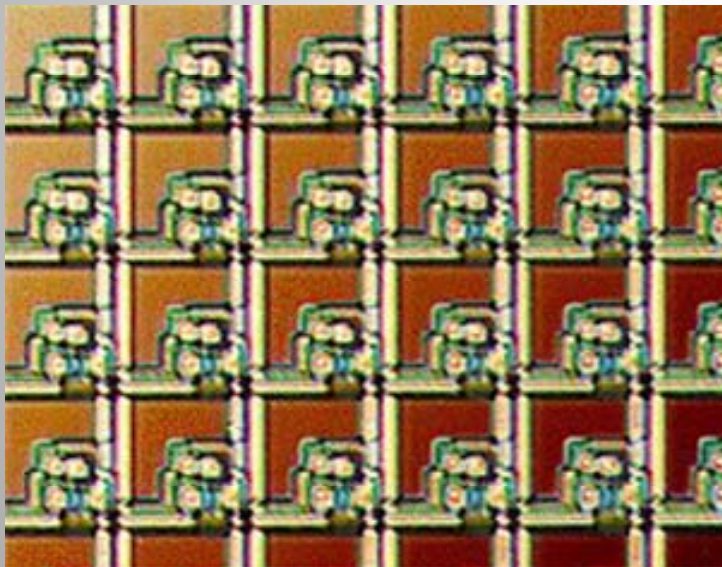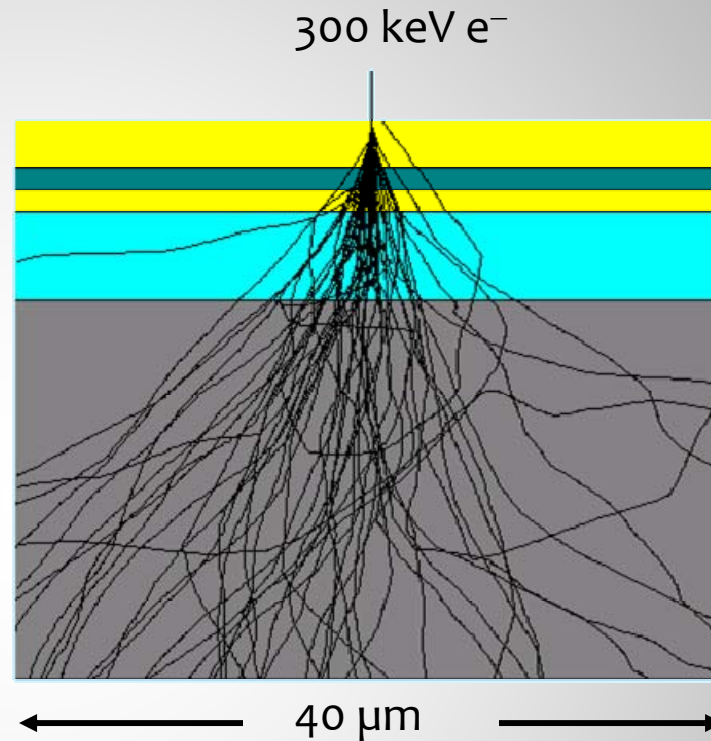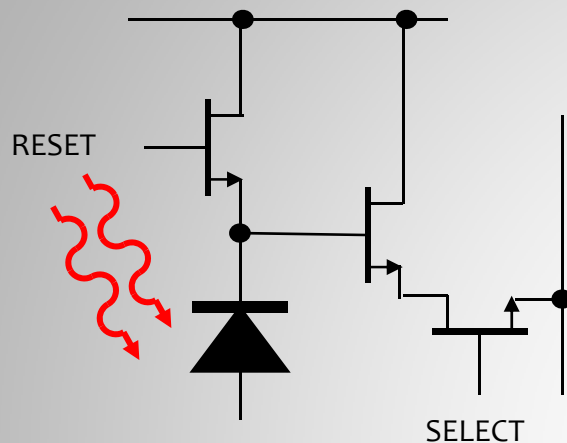

- ◆ Essentially all charge collected from thin region
- ◆ Detector can be thinned
- ◆ Higher energy  $\rightarrow$  better PSF, lower S/N
- ◆ Rivals film MTF

## Film vs. Silicon

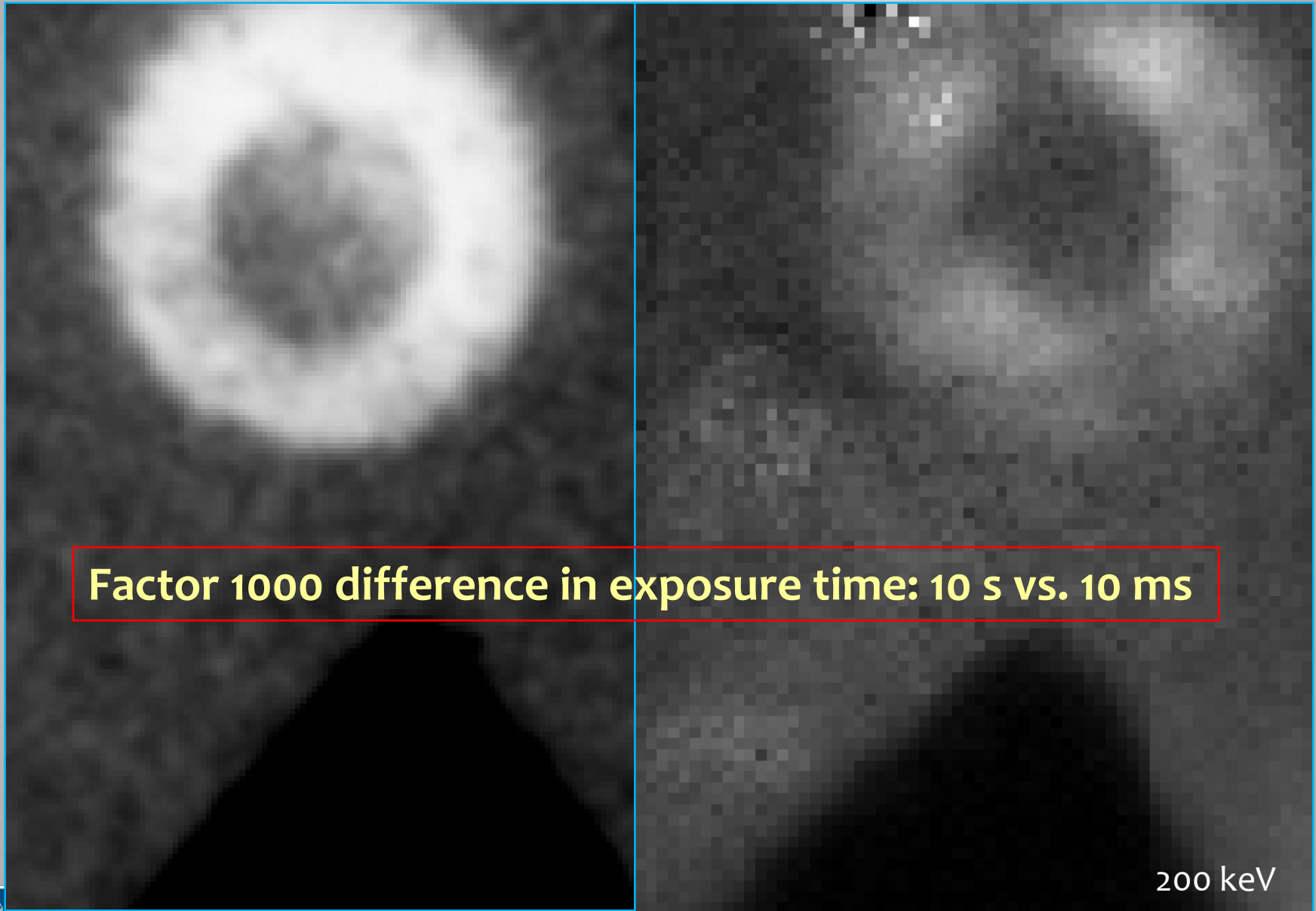


Factor 1000 difference in exposure time: 10 s vs. 10 ms

200 keV

# An example of another kind of ADC

*Charged particle tracker*

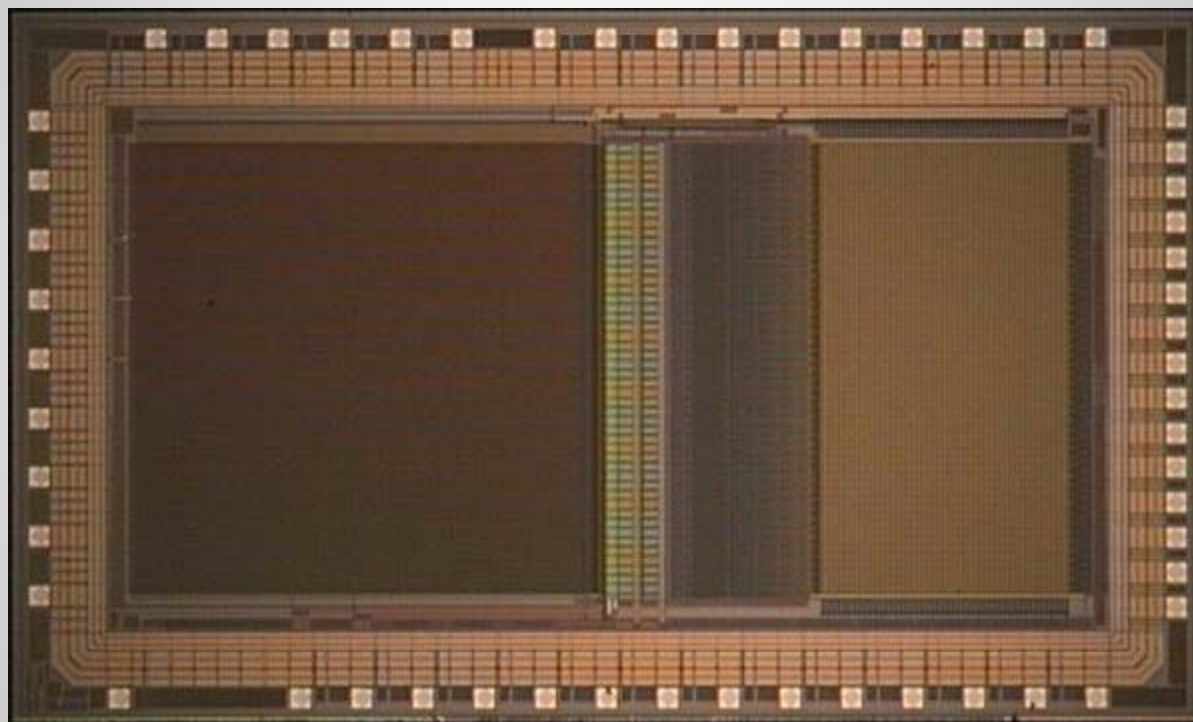

Sensor


ADC

Memory

5-bit differential charge redistribution ADC


# Capacitive charge redistribution ADC

*A form of successive approximation ADC*

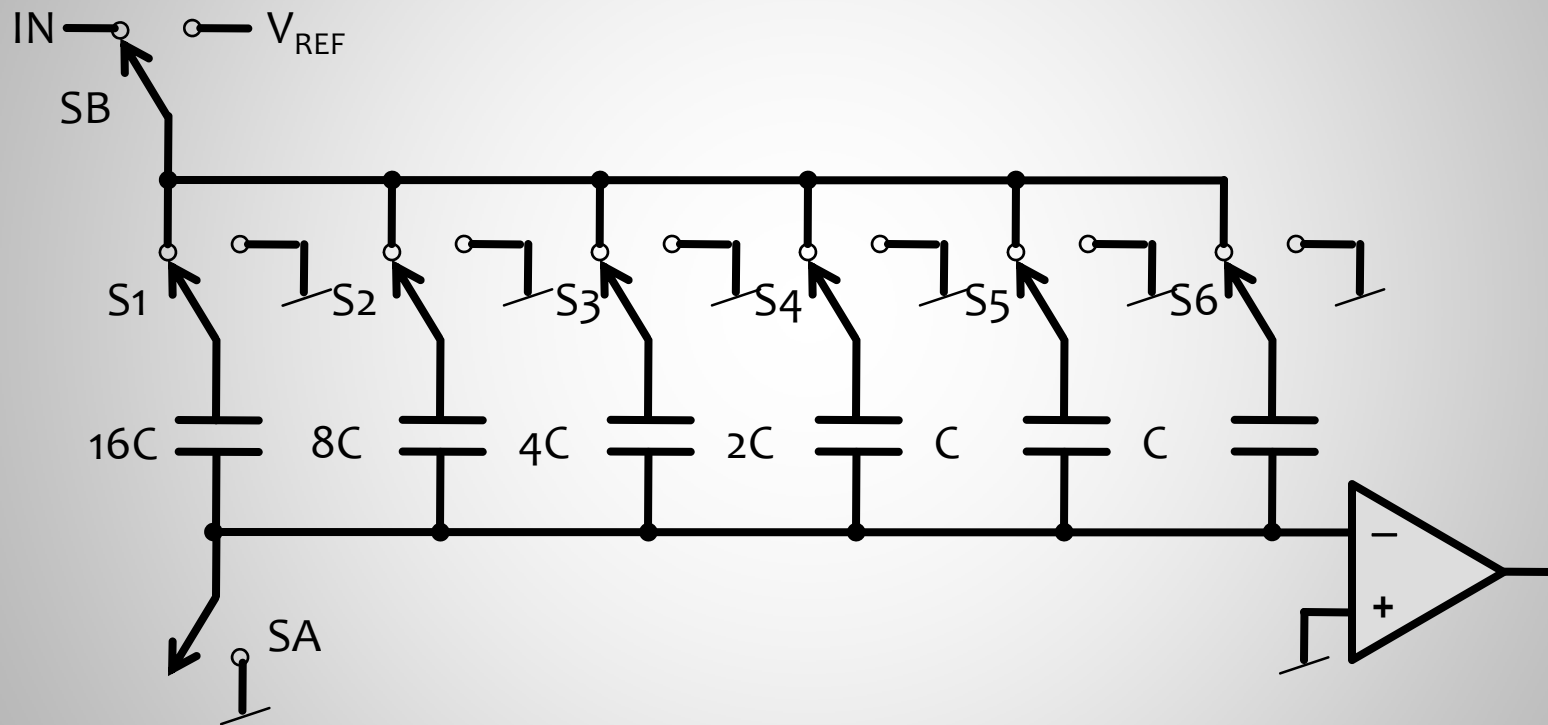




# Sample input

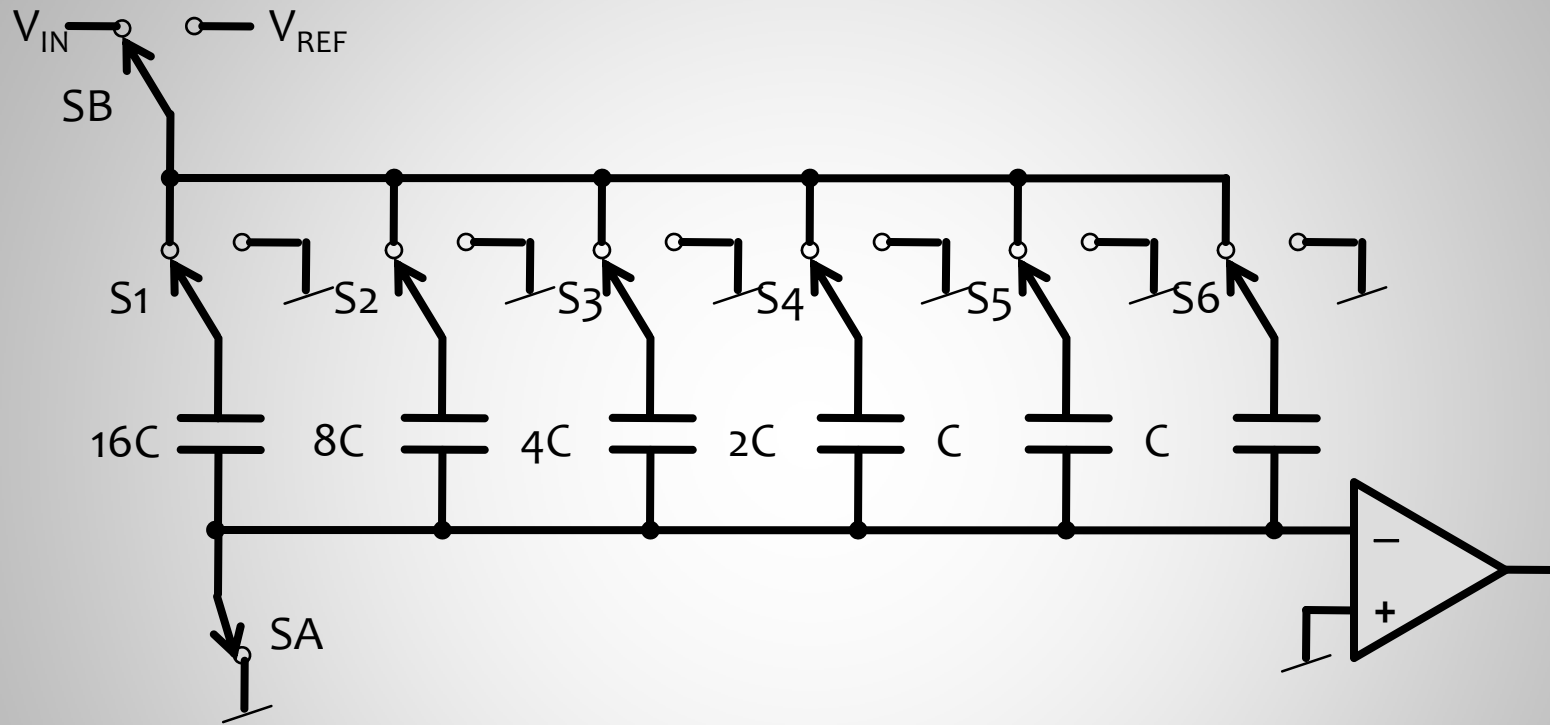


Charge stored on capacitors:  $Q = 32C \times V_{IN}$

$V_- = 0$

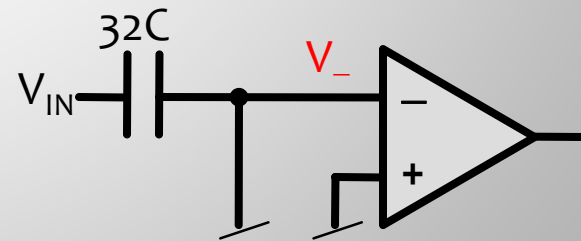


# Hold – do nothing

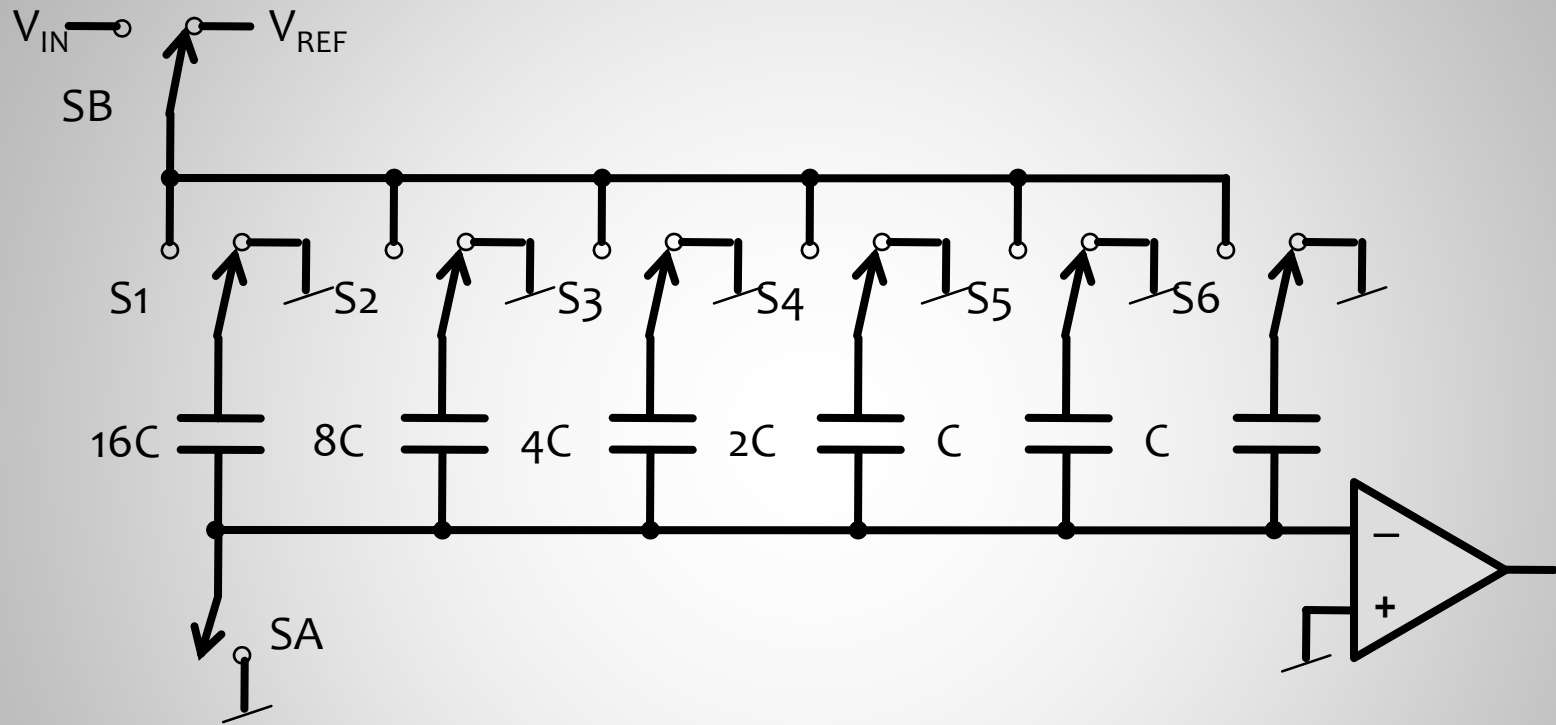


Charge stored on capacitors:  $Q = 32C \times V_{IN}$

$$V_- = -V_{IN}$$

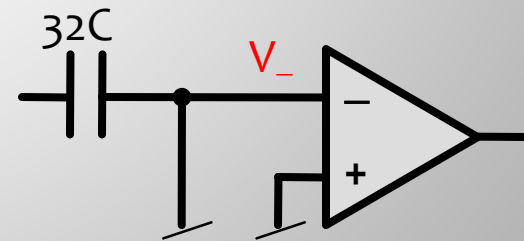




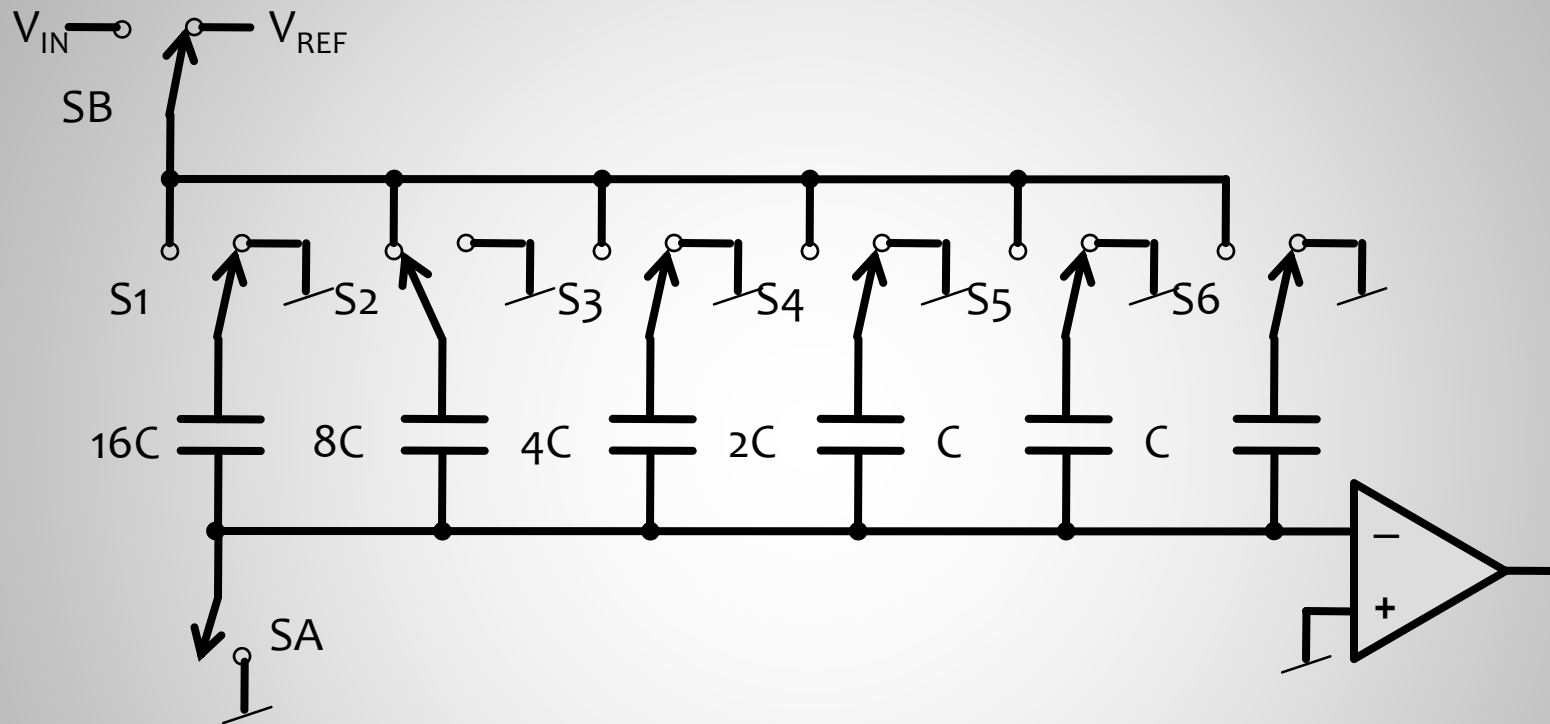
If comparator fired (MSB = 1)  $V_{IN} < V_{REF}/2$




$$V_- = V_{REF}/4 - V_{IN}$$

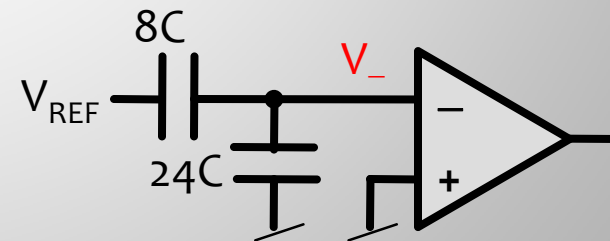

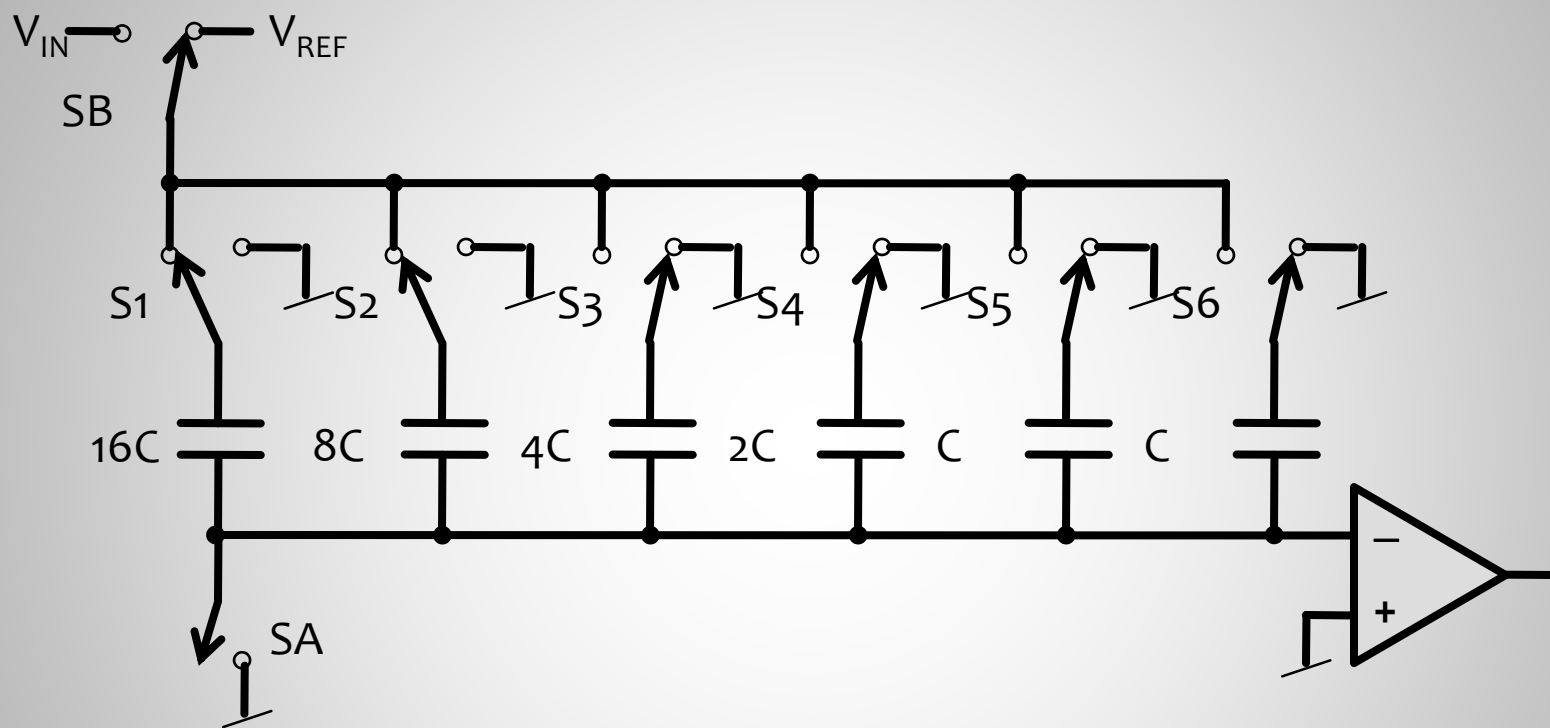If comparator did not fire (MSB = 0)  $V_{IN} > V_{REF}/2$



$$V_- = 3 \times V_{REF} / 4 - V_{IN}$$

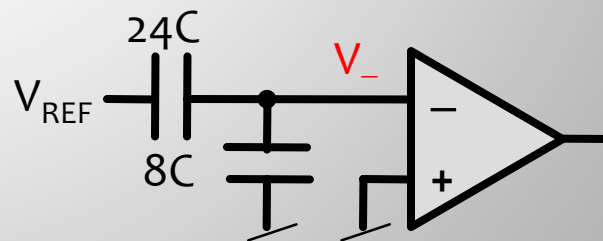

# CCD vs. APS

## ◆ Consumer market


- APS – “system on a chip” (cell phone cameras)
- CCD – high end digital camera, but overtaken by APS (again, system on a chip)

## ◆ Scientific market

- Still CCD (more sensitive, bigger – easier to make “wafer scale”)
  - Ubiquitous x-ray and electron detector is a phosphor fiber-coupled to a CCD
- APS a growing interest for charged particles
- CCD lends itself naturally to CDS
  - But modern optical APS do too
- Back-illuminated CCDs have 100% optical fill factor


# Who Wins?

Silicon

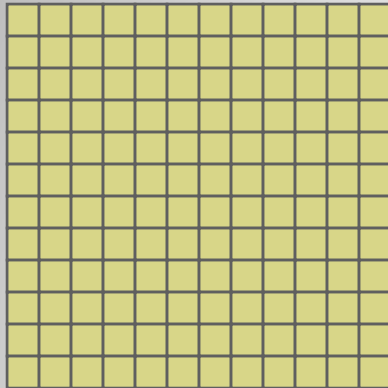




Regular array of pixels  
pitch  $p$

Film

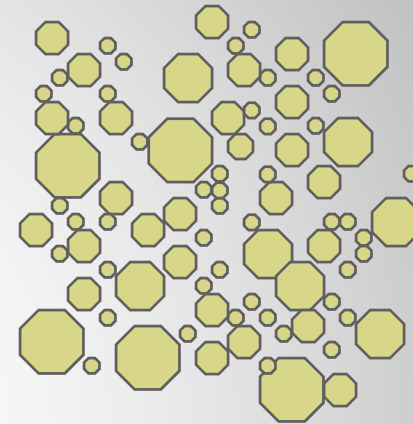

Random collection of  
different grain sizes

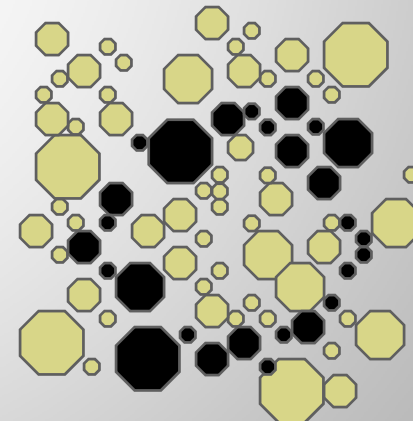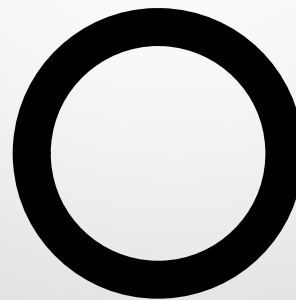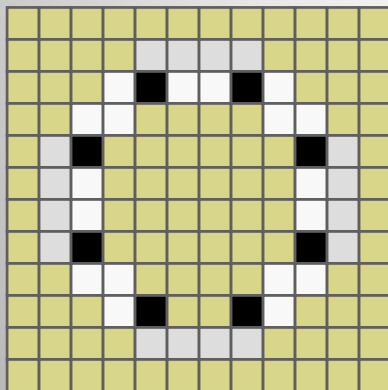*For now film grains smaller than silicon pixels*



Analog

Digital

# Pros and Cons


	Silicon	Film
◆ Processing	Electronic	Chemical
◆ Linearity	“ideal” $n(e^-) = QE \times n(\gamma)$	non-linear – $n \gamma$ required to flip a grain; thermal fluctuations vs grain size
◆ Resolution	Larger pixels	Smaller grains
◆ Dynamic range	CCDs – 16 bits	Locally, ~4 bits
◆ Integration time	Ultra-high quality process – minutes; opto process – seconds; normal process – ms	“long” (also thermally limited)
◆ MTF	Regular pattern – aliasing	Given by smallest grains, no aliasing
◆ MTF x S/N	Better	Worse



# Marketplace has decided


## Camera Sales Million units

■ Analog cameras ■ Digital cameras

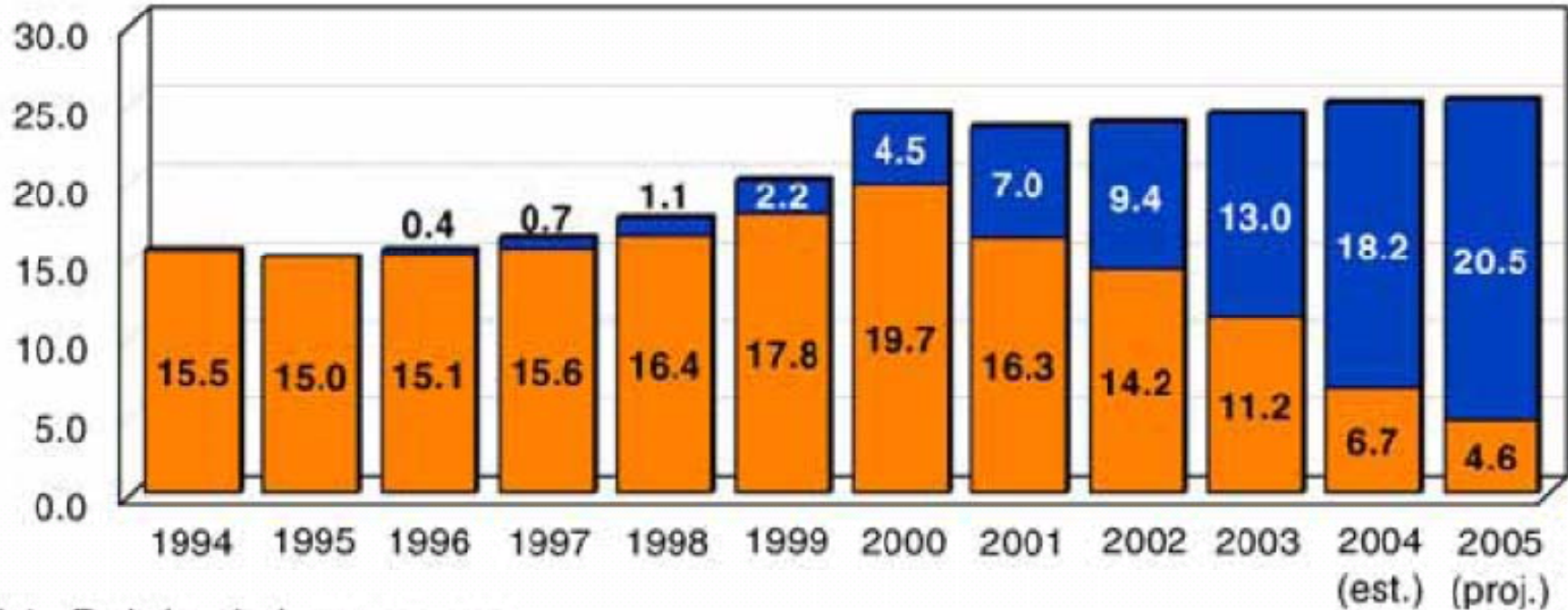

Note: Excludes single-use cameras  
Source: PMA Marketing Research

# Hybrid Pixels




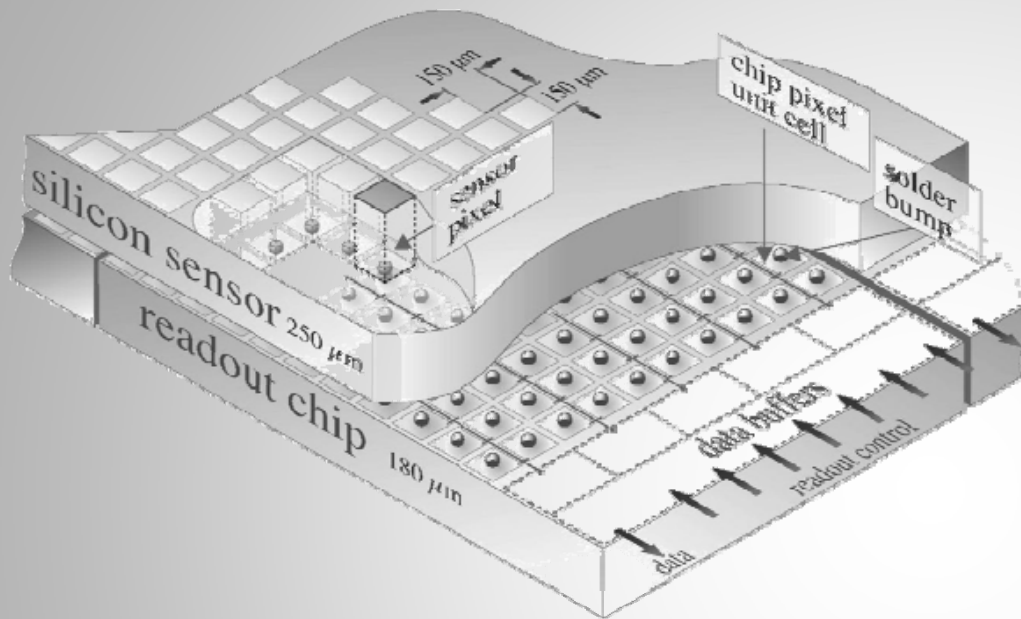


- ◆ Thick sensor
- ◆ Large pixels (due to bump bonding)
- ◆ Bump bonding
- ◆ Size limitations (due to IC)
- ◆ Lots of electronics in a pixel (large pixel)


- ◆ Pixilated sensor on high-resistivity silicon
  - Fully depleted
    - Fully depleted devices collect charge by drift (little diffusion)
    - Partially depleted devices (APS, many CCDs) collect charge by diffusion
- ◆ Bonded to readout IC
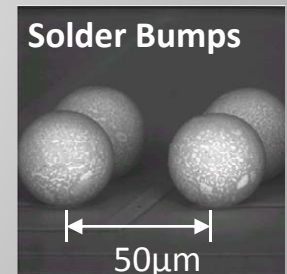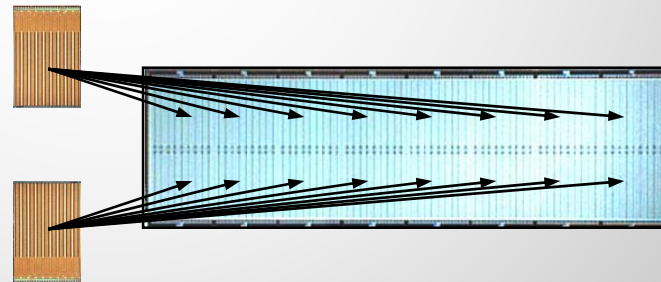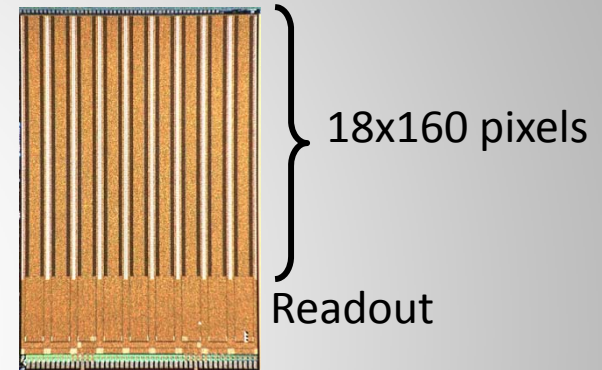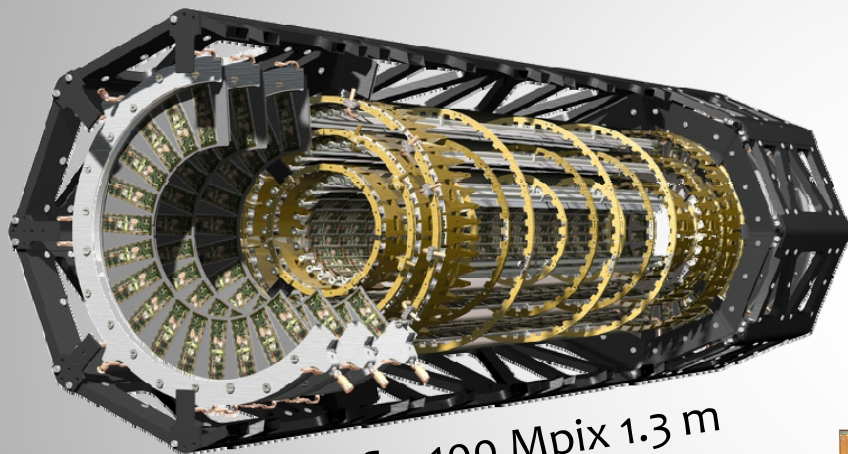
# ATLAS pixel


Massive (~\$200M) development for Large Hadron Collider at CERN  
ATLAS (LBNL and others), CMS (PSI and others)  
CERN spinoff → “Medipix”



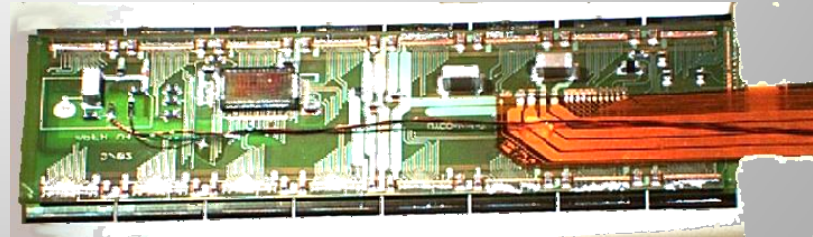A “module” is 1 sensor with  
2x8 bump-bonded chips



# Requirements

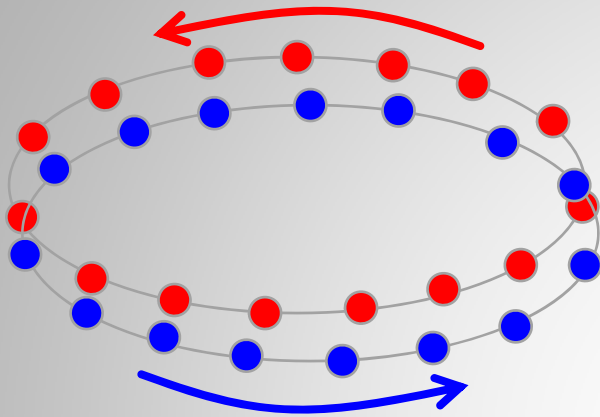


- ◆ LHC – counter-rotating proton beams
- ◆ Bunch crossings every 25 ns
- ◆ Much longer to decide if event from  $BC_i$  is interesting

- ◆ Detect hits in the pixel
- ◆ Tag them to the specific bunch crossing they came from
- ◆ Trigger (request to provide data corresponding to  $BC_i$ ) will come later
  - Provide data for  $BC_i$
  - Flush out other data
- ◆ Radiation hardness

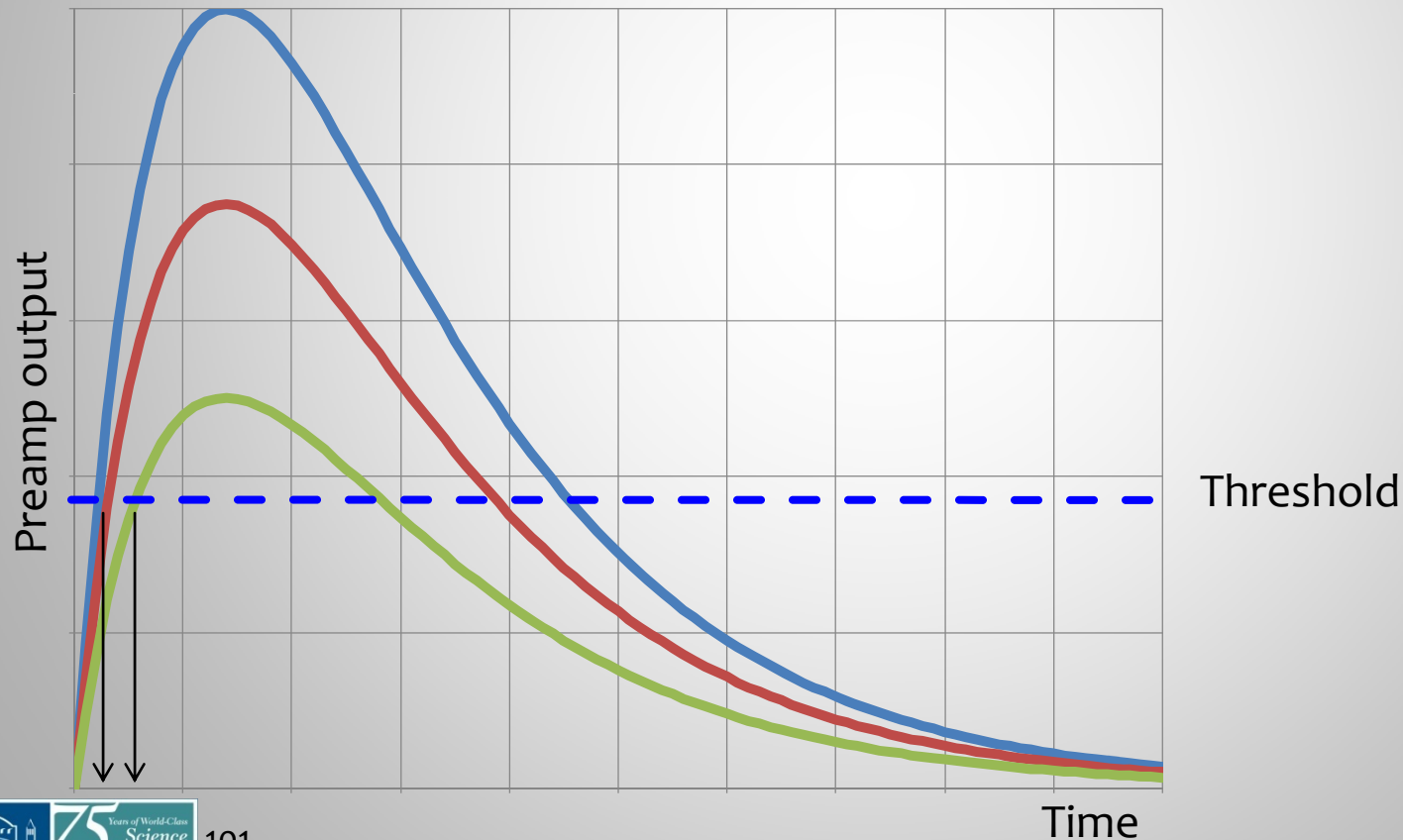
# Solution

- ◆ Folded cascode preamp + comparator
- ◆ Linear discharge feedback
  - Noise  $\sim BW^{1/2}$  - reduce noise by making preamp slower
  - Introduces “timewalk” problem




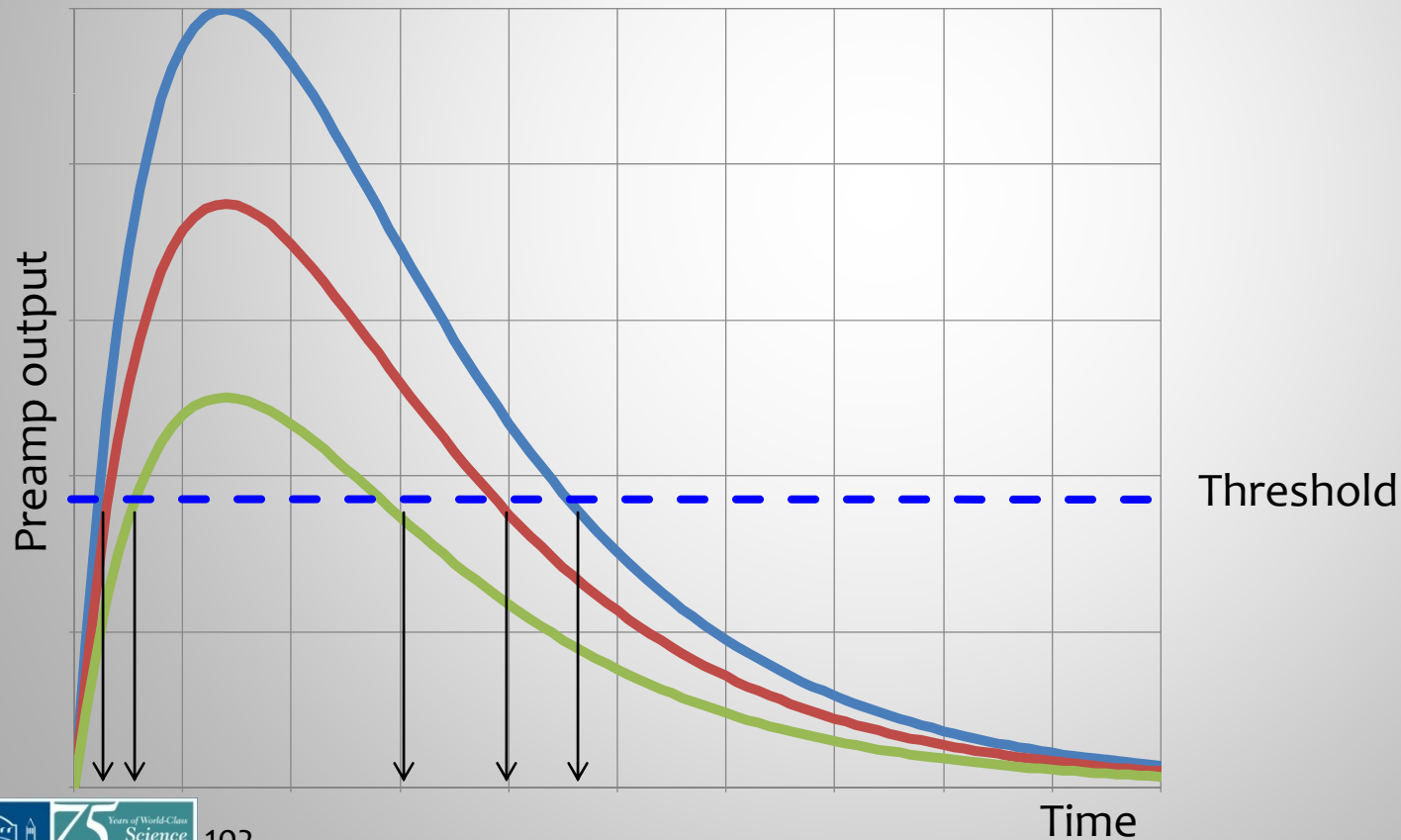
# TOT


- ◆ Measuring “time over threshold” measures charge, and can be used to correct timewalk
- ◆ Variant of Wilkinson ADC



# In a pixel

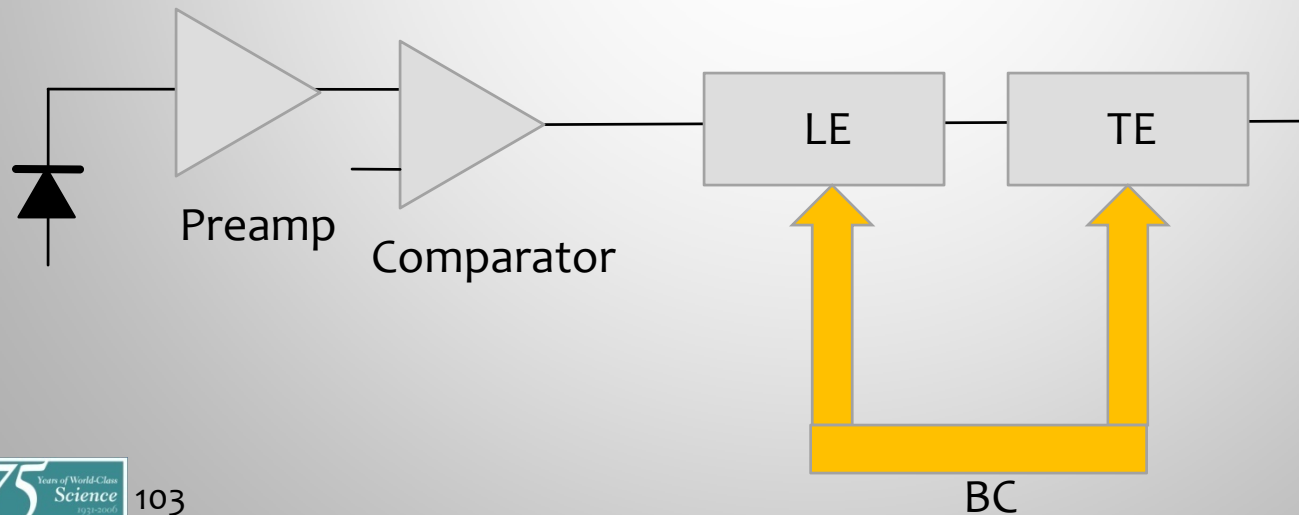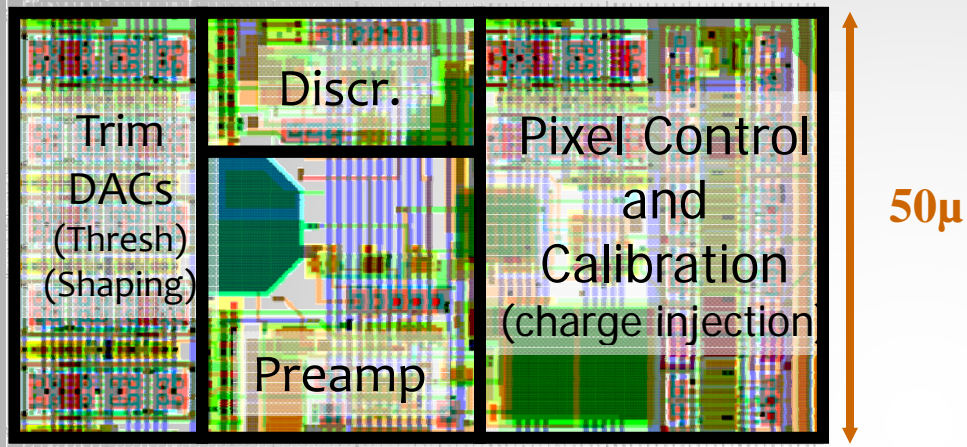


# In a column

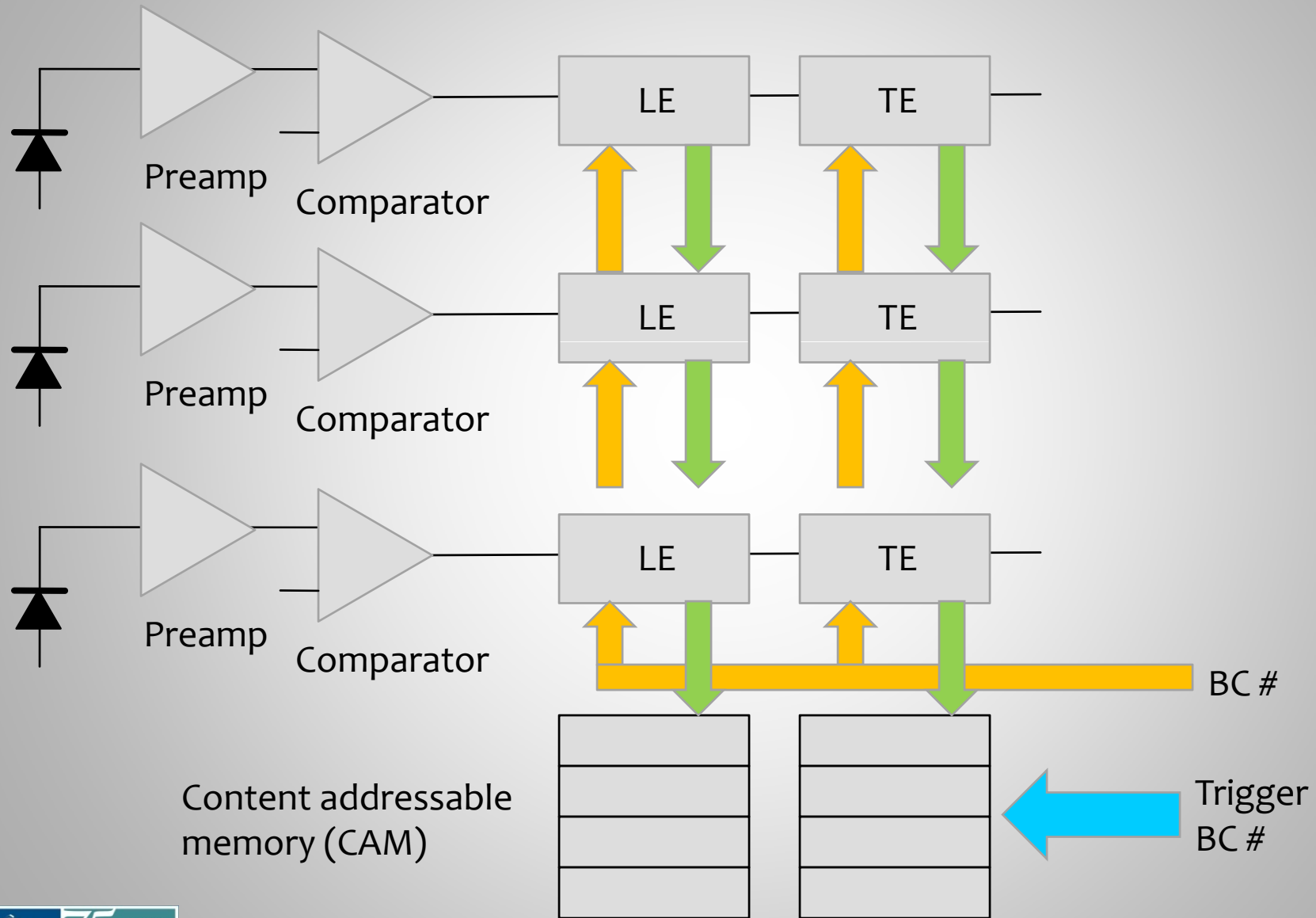



# In a chip

A D

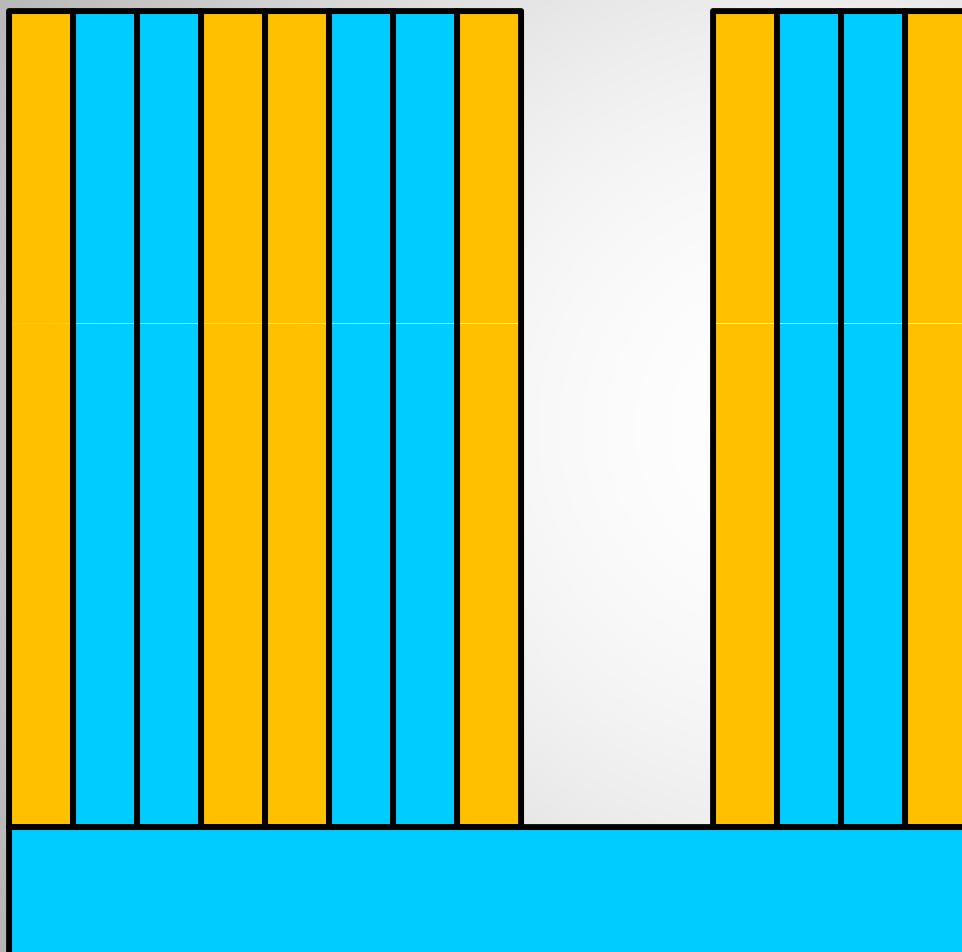


“Column pairs”

BOC
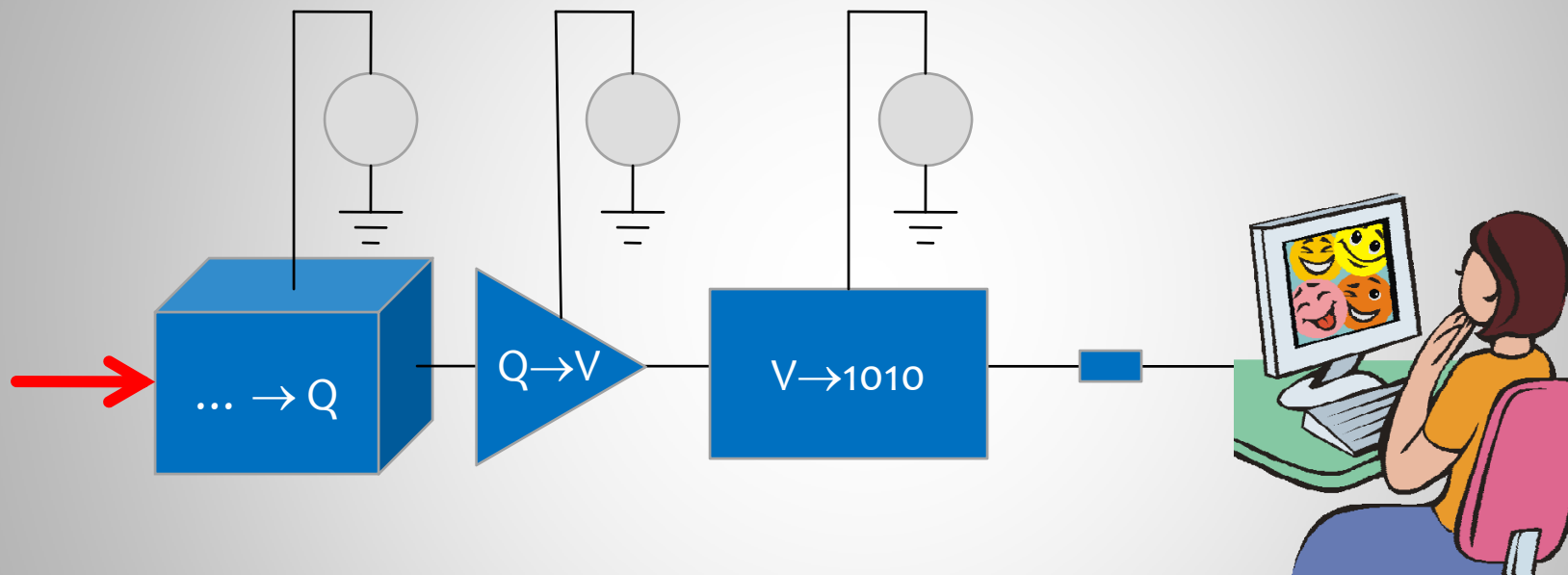
# Caveat Emptor


*Helmuth will warn you about the pitfalls*




- ◆ Analog and Digital blocks
- ◆ Analog and digital power (and detector bias)
- ◆ Digital communications interface

**Not discussed,  
but significant!**

## Rule #1 – Follow the current


- ◆ 99% of “unexpected problems” are due to
  - $V = IR$  (parasitic resistance, improper grounding, ...)
  - $dV/dt = I/C$  (parasitic capacitance)
  - $V = L di/dt$  (parasitic inductance)
- ◆ Mixed-mode systems have digital “spikes” and quiet analog inputs
- ◆ Grounding is not “magic”
- ◆ Power is ground 

# PMOS version of folded cascode preamp

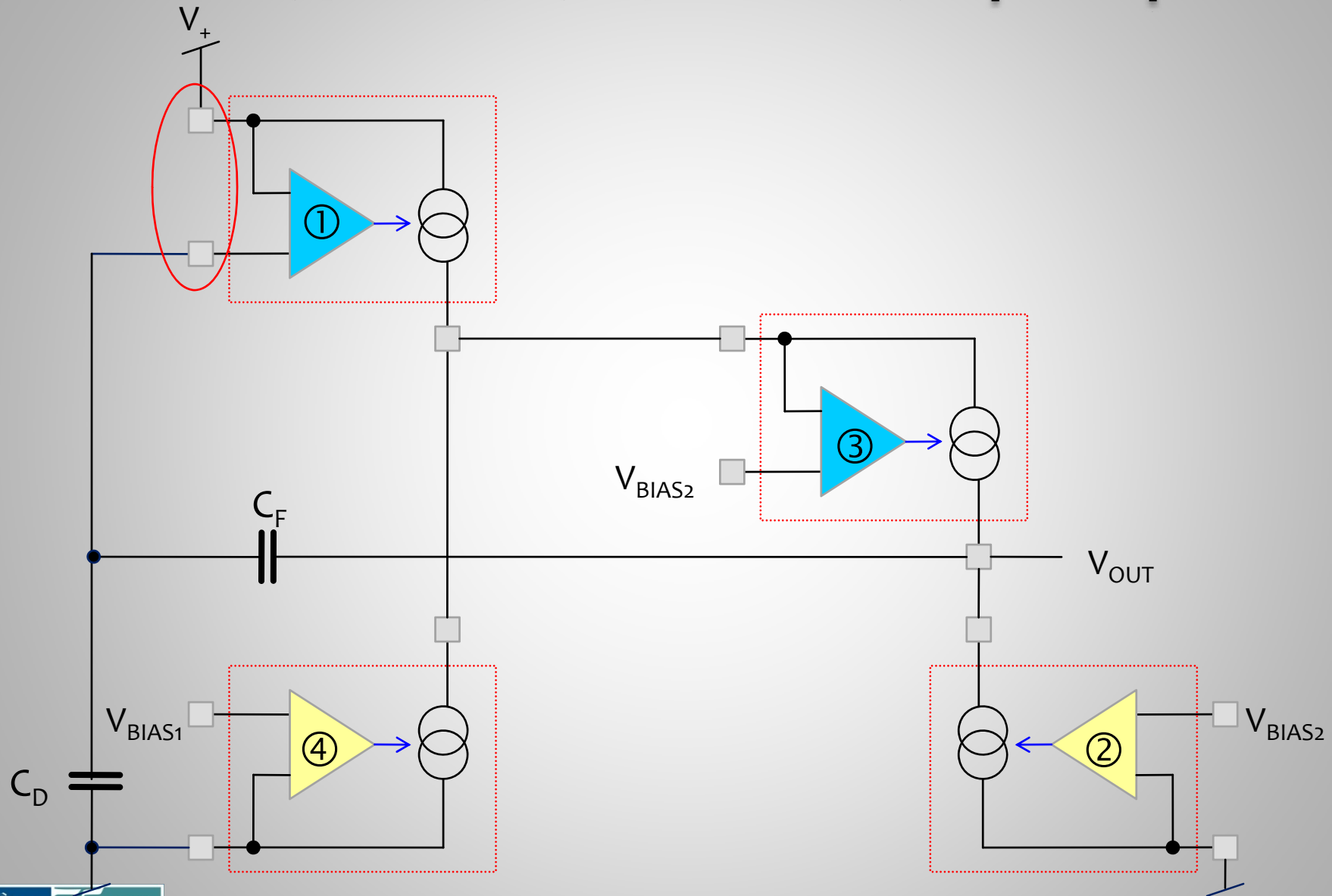
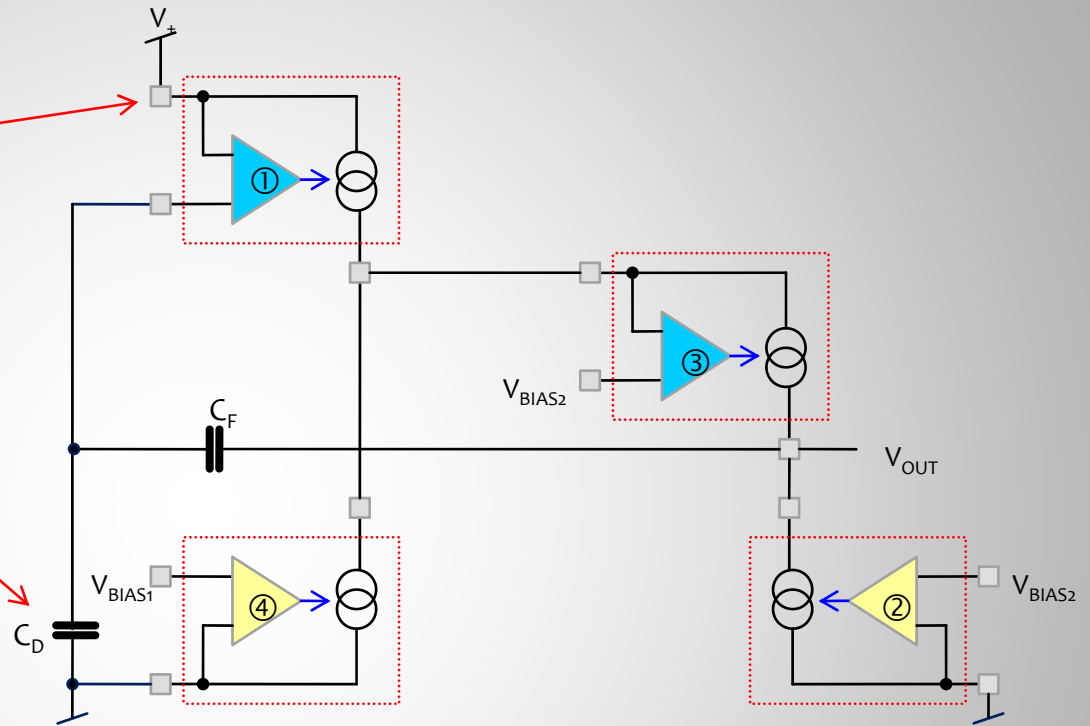
# Follow the current

Two inputs  
The power supply  
The detector



Power Supply Rejection Ratio  $\frac{\partial V_{OUT}}{\partial V_+}$

# Front-End Electronics Systems for Particle Detection and Imaging

- ◆ Quantize charge
- ◆ Electronic detectors *approach* film (but have obvious advantages – particularly speed)
- ◆ Practically, each solution is determined by the  $dE/dx$  of the particle being looked at
- ◆ Electronically, the challenges are noise ( $e^-$  from single photons) and dynamic range
  - Ultimately, radiation hardness