

V.2. Signal Acquisition

- Determine energy deposited in detector
- Detector signal generally a short current pulse

Typical durations

Thin silicon detector (10 ... 300 μm thick):	100 ps – 30 ns
Thick ($\sim\text{cm}$) Si or Ge detector:	1 – 10 μs
Proportional chamber (gas):	10 ns – 10 μs
Gas microstrip or microgap chamber:	10 – 50 ns
Scintillator + PMT/APD:	100 ps – 10 μs


The total charge Q_s contained in the detector current pulse is $i_s(t)$ proportional to the energy deposited in the detector

$$E \propto Q_s = \int i_s(t) dt$$

- Necessary to integrate the detector signal current.

- Possibilities:
1. Integrate charge on input capacitance
 2. Use integrating (“charge sensitive”) preamplifier
 3. Amplify current pulse and use integrating (“charge sensing”) ADC

Signal integration on Input Capacitance

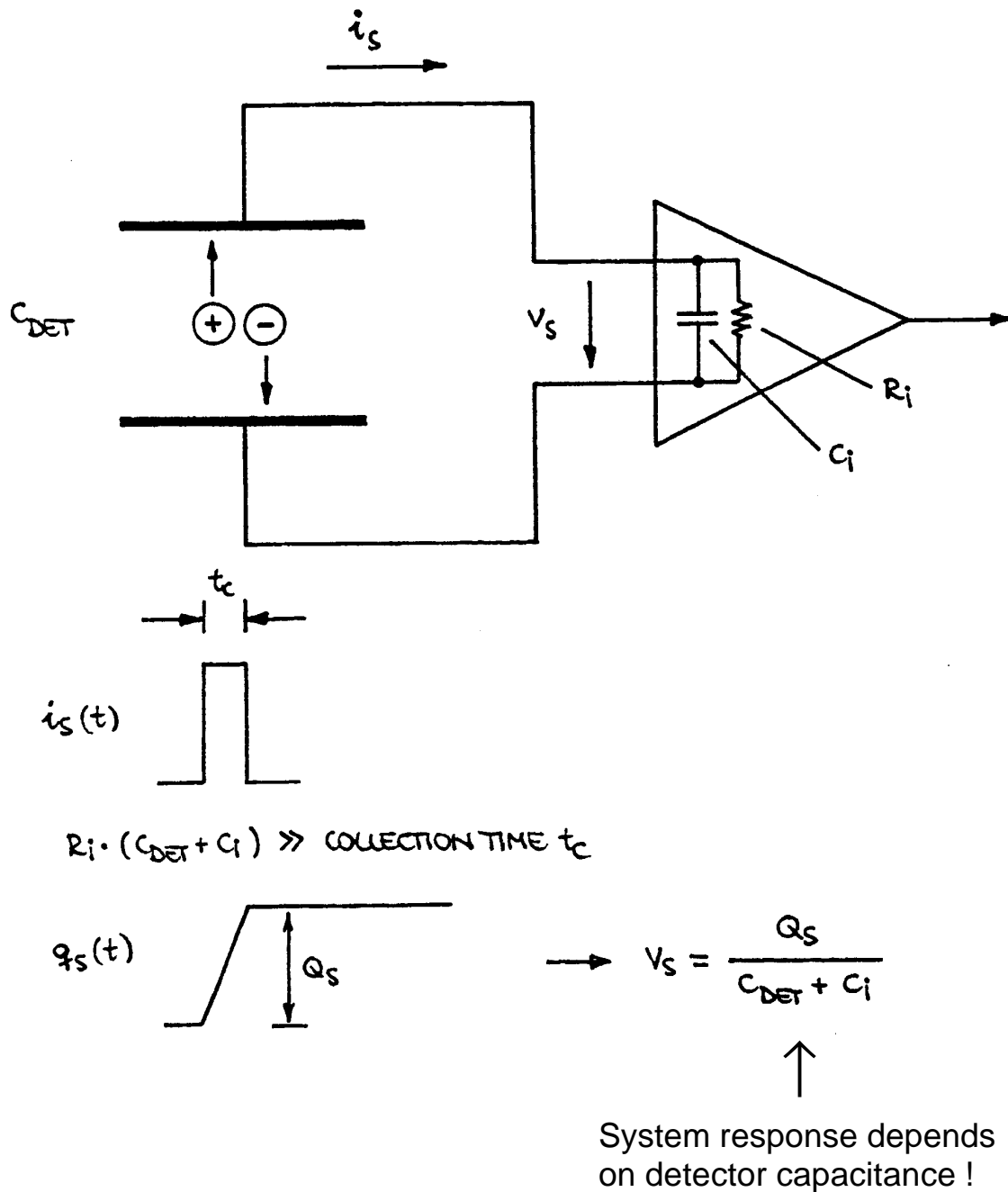

Detector capacitance may vary within a system or change with bias voltage (partially depleted semiconductor diode).

⇒ make system whose gain (dV_{out}/dQ_s) is independent of detector capacitance.


Active Integrator (“charge-sensitive amplifier”)

Start with inverting voltage amplifier

Voltage gain $dV_o/dV_i = -A \Rightarrow v_o = -A v_i$

Input impedance = ∞ (i.e. no signal current flows into amplifier input)

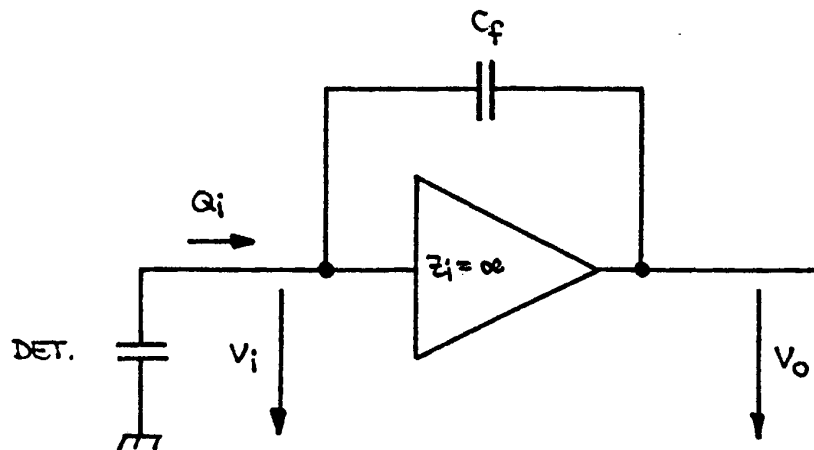Connect feedback capacitor C_f between output and input.



Voltage difference across C_f : $v_f = (A+1) v_i$

\Rightarrow Charge deposited on C_f : $Q_f = C_f v_f = C_f (A+1) v_i$

$Q_i = Q_f$ (since $Z_i = \infty$)

\Rightarrow Effective input capacitance

$$C_i = \frac{Q_i}{v_i} = C_f (A+1)$$

(“dynamic” input capacitance)

Gain

$$A_Q = \frac{dV_o}{dQ_i} = \frac{A \cdot v_i}{C_i \cdot v_i} = \frac{A}{C_i} = \frac{A}{A+1} \cdot \frac{1}{C_f} \approx \frac{1}{C_f} \quad (A \gg 1)$$

Q_i is the charge flowing into the preamplifier

but some charge remains on C_{det} .

What fraction of the signal charge is measured?

$$\frac{Q_i}{Q_s} = \frac{C_i v_i}{Q_{det} + Q_i} = \frac{C_i}{Q_s} \cdot \frac{Q_s}{C_i + C_{det}}$$

$$= \frac{1}{1 + \frac{C_{det}}{C_i}} \approx 1 \quad (\text{if } C_i \gg C_{det})$$

Example:

$$A = 10^3$$

$$C_f = 1 \text{ pF} \quad \Rightarrow \quad C_i = 1 \text{ nF}$$

$$C_{det} = 10 \text{ pF}: \quad Q_i/Q_s = 0.99$$

$$C_{det} = 500 \text{ pF}: \quad Q_i/Q_s = 0.67$$




Si Det.: 50 μm thick
500 mm^2 area

Note: Input coupling capacitor must be $\gg C_i$ for high charge transfer efficiency.

Calibration

Inject specific quantity of charge - measure system response

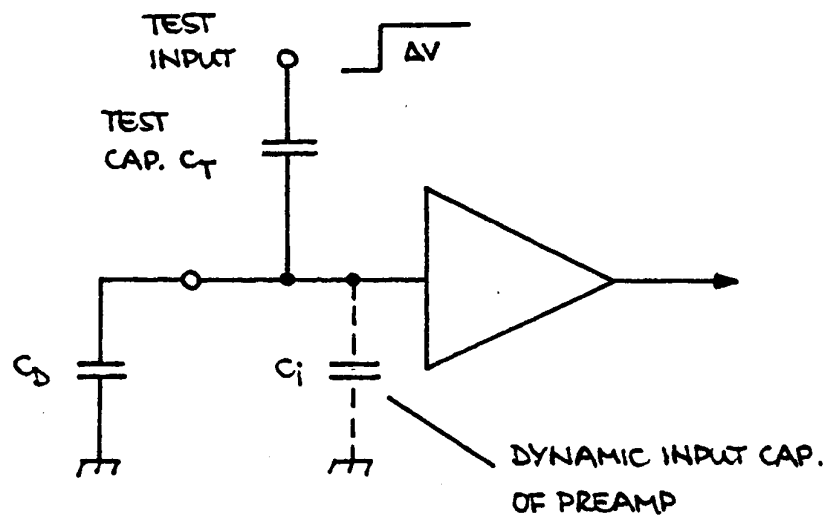Use voltage pulse (can be measured conveniently with oscilloscope)



$C_i \gg C_T \Rightarrow$ Voltage step applied to test input develops over C_T .

$$\Rightarrow Q_T = \Delta V \cdot C_T$$


Accurate expression:

$$Q_T = \frac{C_T}{1 + \frac{C_T}{C_i}} \cdot \Delta V \approx C_T \left(1 - \frac{C_T}{C_i} \right) \Delta V$$

Typically: $C_T/C_i = 10^{-3} - 10^{-4}$

Summary of Amplifier Types

1. Simple Amplifiers

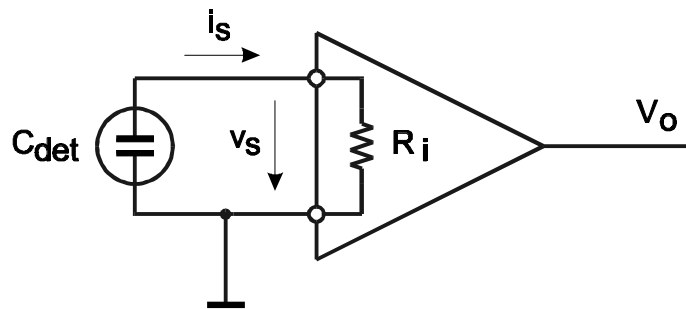

Output voltage $V_o =$ voltage gain $A_v \times$ input voltage v_s .

Operating mode depends on charge collection time t_{coll} and the input time constant $R_i C_{det}$:

a) $R_i C_{det} \ll t_{coll}$ detector capacitance discharges rapidly

$$\Rightarrow V_o \propto i_s(t)$$

current sensitive amplifier

b) $R_i C_{det} \gg t_{coll}$ detector capacitance discharges slowly

$$\Rightarrow V_o \propto \int i_s(t) dt$$

voltage sensitive amplifier


In both cases the output signal voltage is determined directly by the input voltage.

2. Feedback Amplifiers

Basic amplifier as used above.

High input resistance: $R_i C_{det} \gg t_{coll}$

Add feedback capacitance C_f

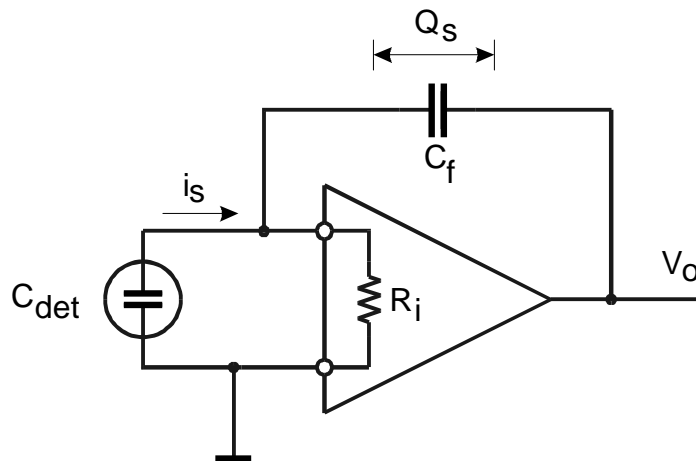

Signal current i_s is integrated on feedback capacitor C_f :

$$V_o \propto Q_s / C_f$$

Amplifier output directly determined by signal charge,
insensitive to detector capacitance


⇒ charge-sensitive amplifier

Realistic Charge-Sensitive Preamplifiers

The preceding discussion assumed idealized amplifiers with infinite speed.

- How do “real” amplifiers affect charge response?
- How does the detector affect amplifier response?

A Simple Amplifier

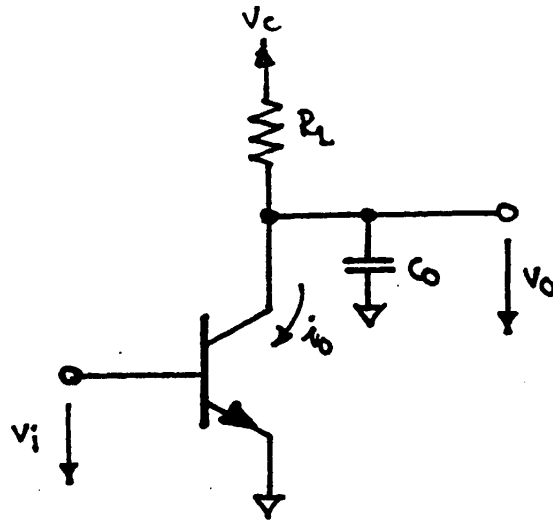

Voltage gain:


$$A_V = \frac{dv_o}{dv_i} = \frac{di_o}{dv_i} \cdot Z_L \equiv g_m Z_L$$

$g_m \equiv$ transconductance

$$Z_L = R_L // C_o$$

$$\frac{1}{Z_L} = \frac{1}{R_L} + i\omega C_o \quad \Rightarrow \quad A_V = g_m \left(\frac{1}{R_L} + i\omega C_o \right)^{-1}$$

\uparrow low freq. \uparrow high freq.

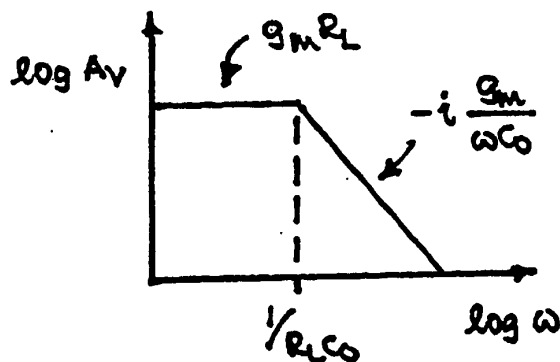


\uparrow upper cutoff frequency $2\pi f_u$

Pulse Response of the Simple Amplifier

A voltage step $v_i(t)$ at the input causes a current step $i_o(t)$ at the output of the transistor.

For the output voltage to change, the stray capacitance C_o must first charge up.

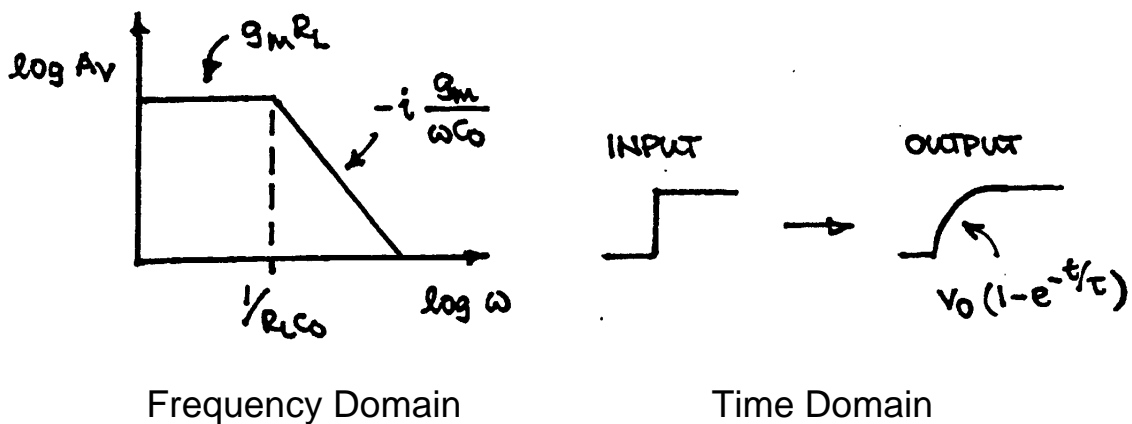⇒ The output voltage changes with a time constant $\tau = R_L C_o$




Note that τ is the inverse upper cutoff frequency $1/(2\pi f_u)$

Input Impedance of a Charge-Sensitive Amplifier

Input impedance

$$Z_i = \frac{Z_f}{A+1} \approx \frac{Z_f}{A} \quad (A \gg 1)$$

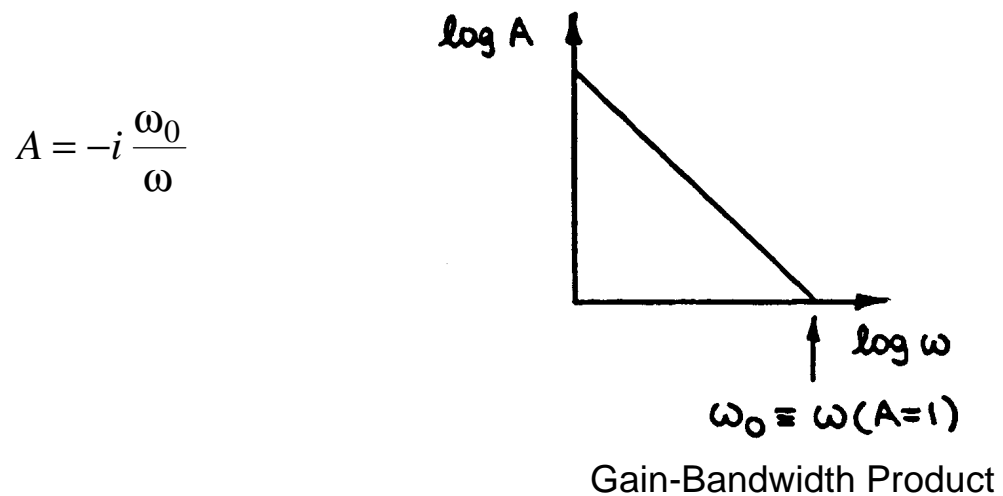Amplifier gain vs. frequency beyond the upper cutoff frequency



Feedback Impedance

$$Z_f = -i \frac{1}{\omega C_f}$$

⇒ Input Impedance

$$Z_i = -\frac{i}{\omega C_f} \cdot \frac{1}{-i \frac{\omega_0}{\omega}}$$

$$Z_i = \frac{1}{\omega_0 C_f}$$


Imaginary component vanishes ⇒ *Resistance: $Z_i \rightarrow R_i$*

Time Response of a Charge-Sensitive Amplifier

Closed Loop Gain

$$A_f = \frac{C_D + C_f}{C_f} \quad (A_f \ll A_0)$$
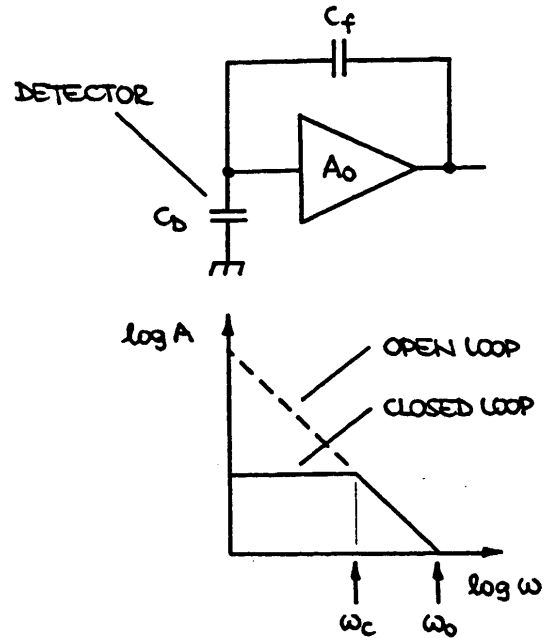
$$A_f \approx \frac{C_D}{C_f} \quad (C_D \gg C_f)$$



Closed Loop Bandwidth

$$\omega_c A_f = \omega_0$$

Response Time

$$\tau_{amp} = \frac{1}{\omega_c} = C_D \frac{1}{\omega_0 C_f}$$

Alternative Picture: Input Time Constant

$$\tau_i = R_i C_D$$

$$\tau_i = \frac{1}{\omega_0 C_f} \cdot C_D = \tau_{amp}$$

Same result as from conventional feedback theory.